


the built-in amplifier performance in HV-CMOS CHES1

Vitaliy Fadeyev, Zach Galloway , Herve Grabas
Alexander Grillo , Zhijun Liang , Abe Seiden
Jennifer Volk, Forest Martinez-Mckinney

University of California, Santa Cruz

CHESS1 bonded for testing


CHESS1 chip Mount on daughter board

 

Thanks to Jaya John and Oxford group to design daughter board for CHESS1 chip


CHESS1 amplifier

 A low noise built-in amplifier **into** the CHESS1 chip to improve the signal to noise ratio.




Bias	Description	Config (V)
VNBias	Bias for the NWELL	0.4
Casc	Cascode voltage	2.6
VPLoad	Pmos Load voltage	2.1
iN	Amplifier bias current	1.0
iNSF	Source Follower Bias	0.49
iFB	Feedback current	2.664

Isolated amplifier test Setup

 


Pulse shape


Before irradiation

 


After 3Mrad gamma irradiation

 

Response curve

 

Rise time

 

Summary

- The gain increased after radiation
- Rise time and deadtime(pulse width) increased after radiation