

Readout Adapter Details

- Readout Adapter's purpose is to convert 112-bit-wide data coming from L0L1 to 12-bit-wide "cluster" format required by the readout block
- Readout Adapter is implemented with a FIFO and a latch
- A state machine reads out the 112 bits sequentially into 11-bit chunks (the 12th bit is the "last cluster" bit)
- We can actually drop the Data Valid bit at this point because the number of cluster packets uniquely identifies the number of valid data packets
- 1 hit on CHESS II translates to 2 cluster packets, 8 hits to 10 cluster packets



1.00us


Re-launch

Objects


Simulation Objects for ReadoutA...

Object Name	Value
cluster_we	0
cluster[11:0]	000000000000
BC	0
rstb	1
in_we	0
data_in[11:0]	000000000000
Xoff	0

Name	Value
cluster_we	1
cluster[11:0]	111111111110
[11]	1
[10]	1
[9]	1
[8]	1
[7]	1
[6]	1
[5]	1
[4]	1
[3]	1
[2]	1
[1]	1
[0]	0
BC	1
rstb	1
in_we	0
data_in[11:0]	000000000000
Xoff	0

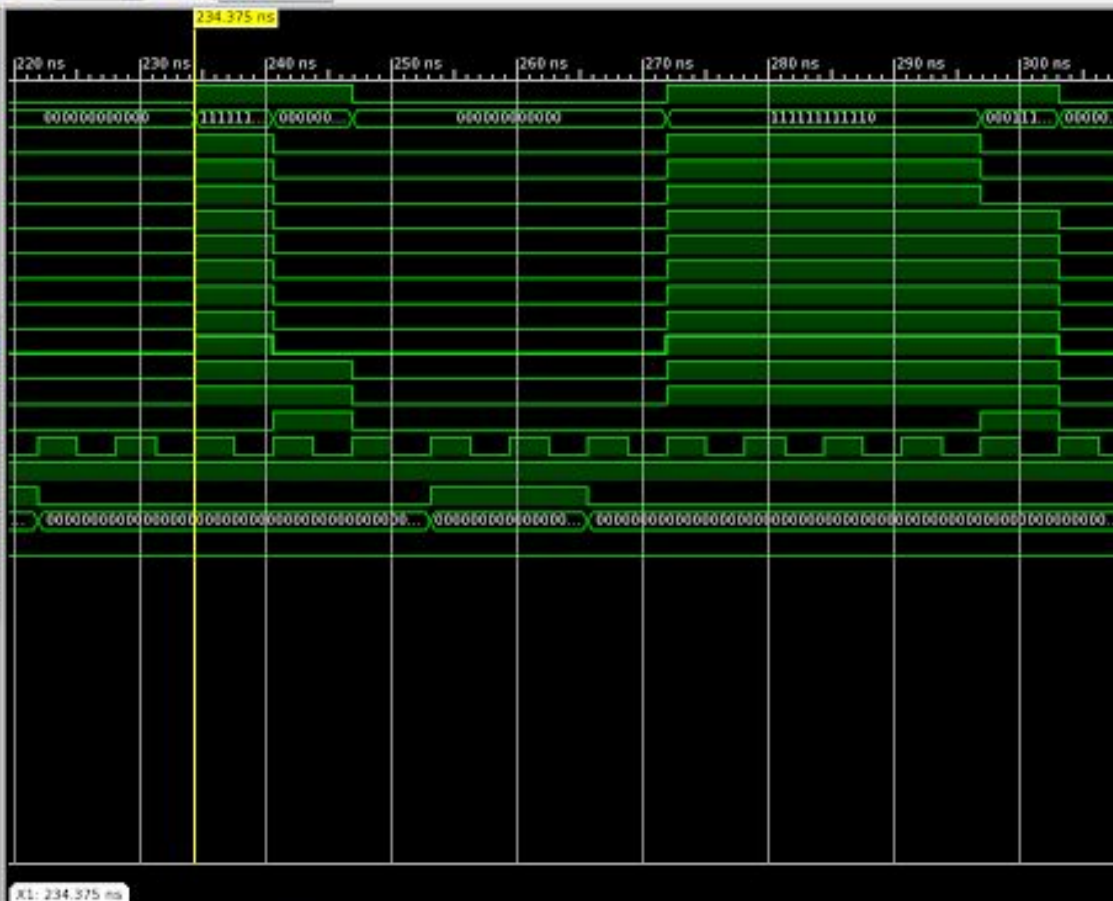

X1: 234.375 ns

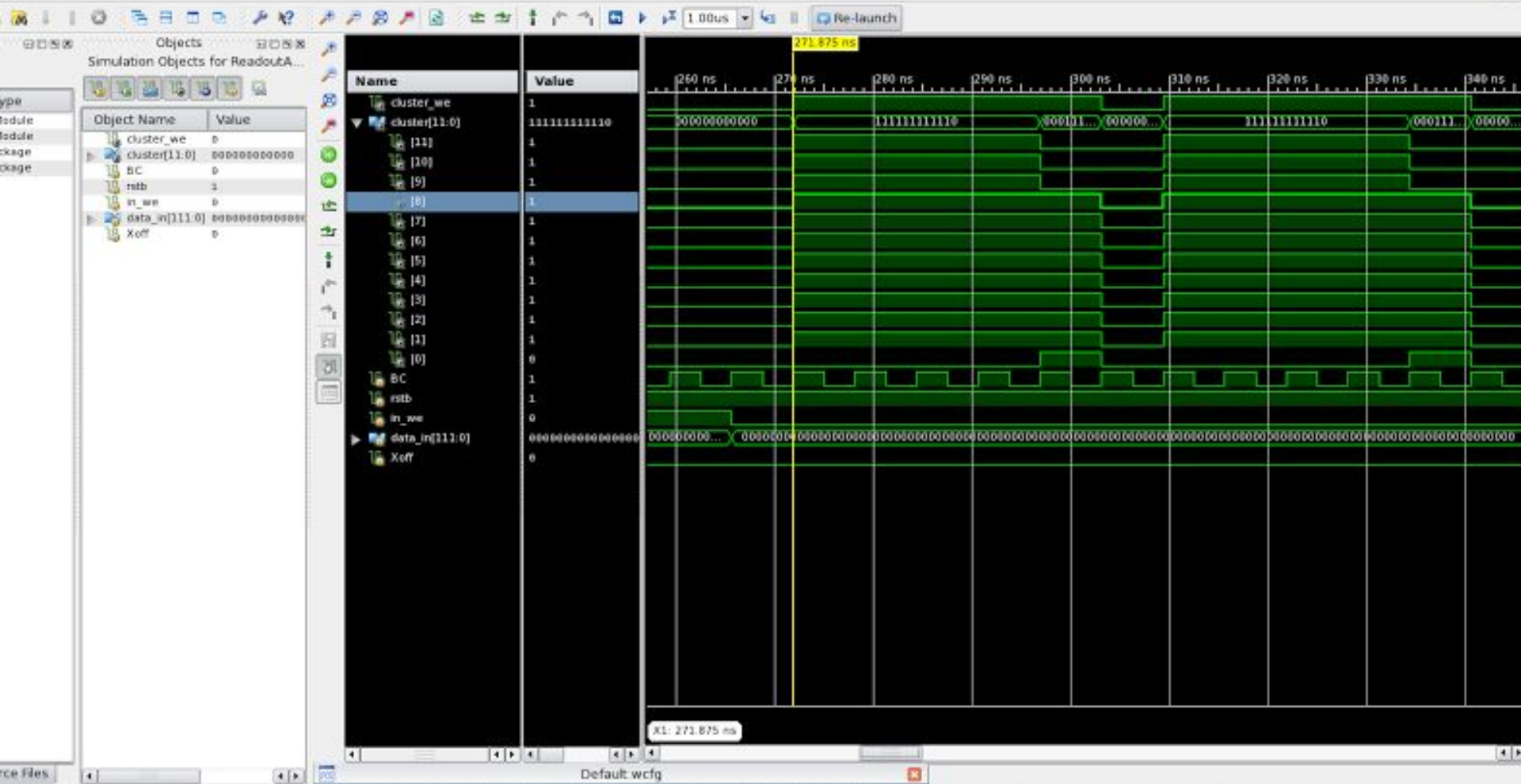

- Next steps: in correspondence with Aditya, need to implement a latch that temporarily holds data if Xoff is asserted
- If no data is associated with a BC, need to send a “no data” signal
- Perhaps this could be done by sending one single packet, as this is not associated with any valid data (the shortest actual data requires 2 packets)