



# Fast(er) Emergency Shutdown



Michael Ritzert


[michael.ritzert@ziti.uni-heidelberg.de](mailto:michael.ritzert@ziti.uni-heidelberg.de)

PXD Workshop

Hamburg

 23.09.2019

- Objective: Improve shutdown time on beam-loss conditions.
- Current situation:
  - All interlocks are received via the VLHI system, which provides only a slow signal (up to 8 ms response time of the output module).
  - On power-off, the charge in the module is only drained parasitically.
- Two (mostly) independent subprojects identified:
  - Add an additional interlock input directly from the DCU.  
⇒ Start the shutdown procedure earlier.
  - Actively short the power supply outputs.  
⇒ Speed up the shutdown.
- Both subprojects require modifications to the power supply hardware, but in different areas.  
⇒ Implement at the same time?
- With both projects implemented, we still will not completely power off before the beam dump is complete.



# Direct Interlock from the DCU

- Add an additional direct interlock line from DCU to PXD PS.
  - A suitable signal is already available on top of Belle.
  - It's a single NIM signal, so my proposal is to receive it once and then distribute internally (between Backplanes).
- Modify the interlock cabling to connect this as the second interlock of the PS unit.
- Add circuitry to disable the interlock to the Backplane.
  - The „normal“ interlock can be controlled via the VLHI.
  - The new diamond interlock also needs some sort of control.
  - Proposal: Modify the PS backplane to make the interlock switchable from the Crate Controller:

We are lucky: The CC design was for four PS units per backplane, we have only three.


⇒ There is one more **control bit** available. We should be able to use that.

⇒ We need only modify the (hopefully cheap) backplane, not the more complex CC.


# Active Power-Off
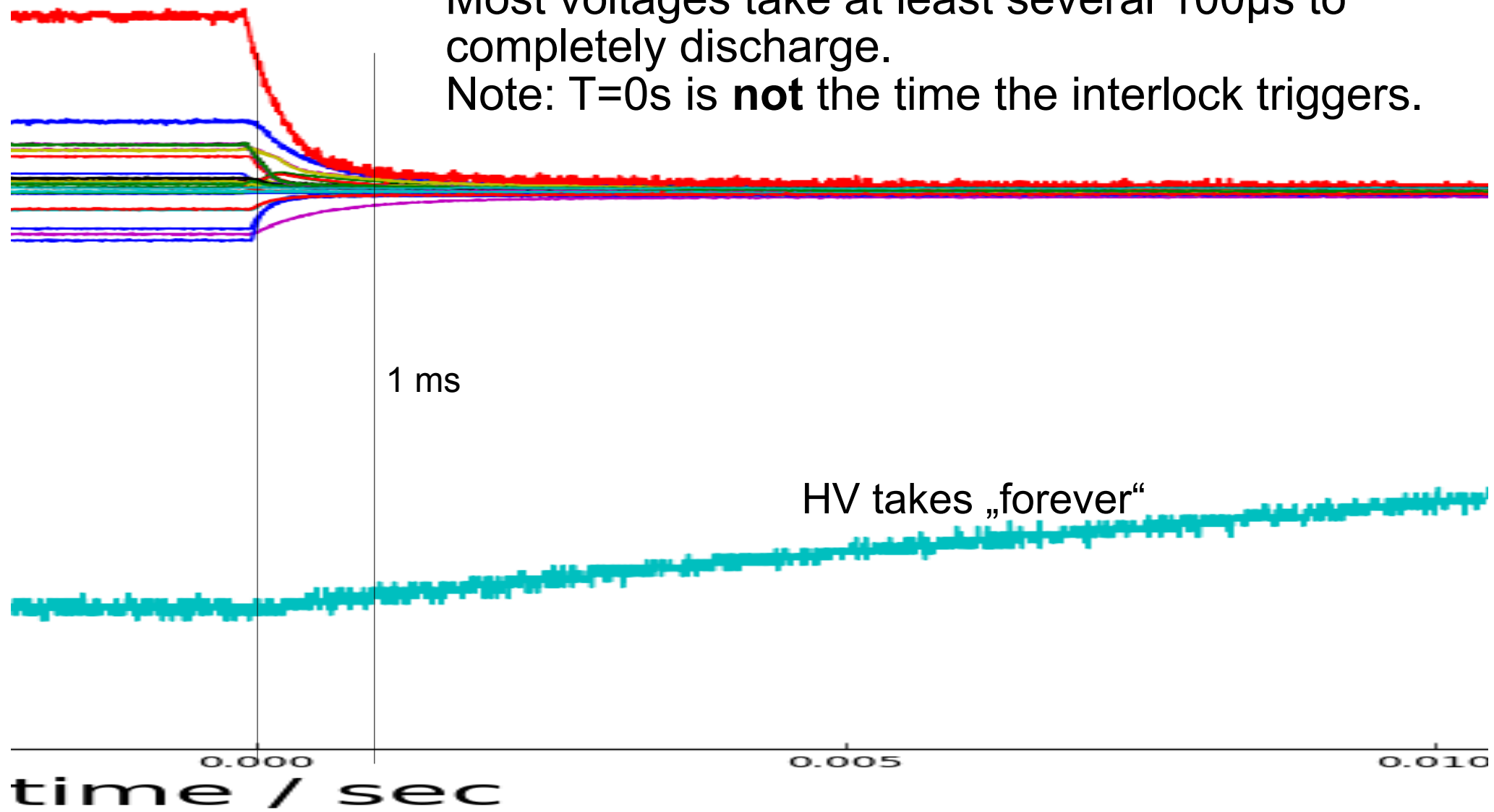
# Where We Are Coming From


- Philipp's and Markus' measurements of the shutdown timing:  
Most voltages take at least several 100 $\mu$ s to completely discharge.  
Note:  $T=0$ s is **not** the time the interlock triggers.



# Unipolar Output Stage

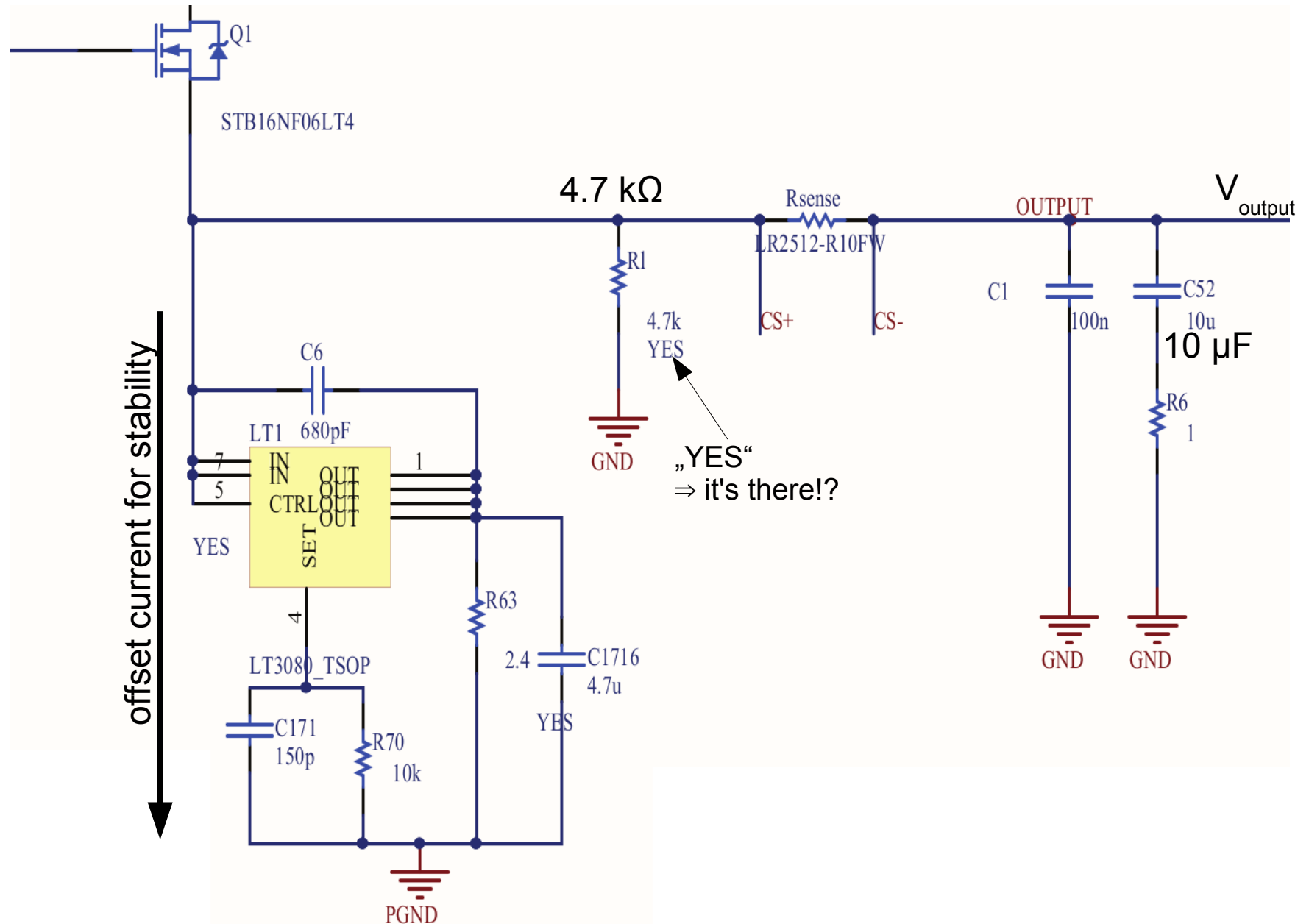

# The Basic Idea (First Test PCB)

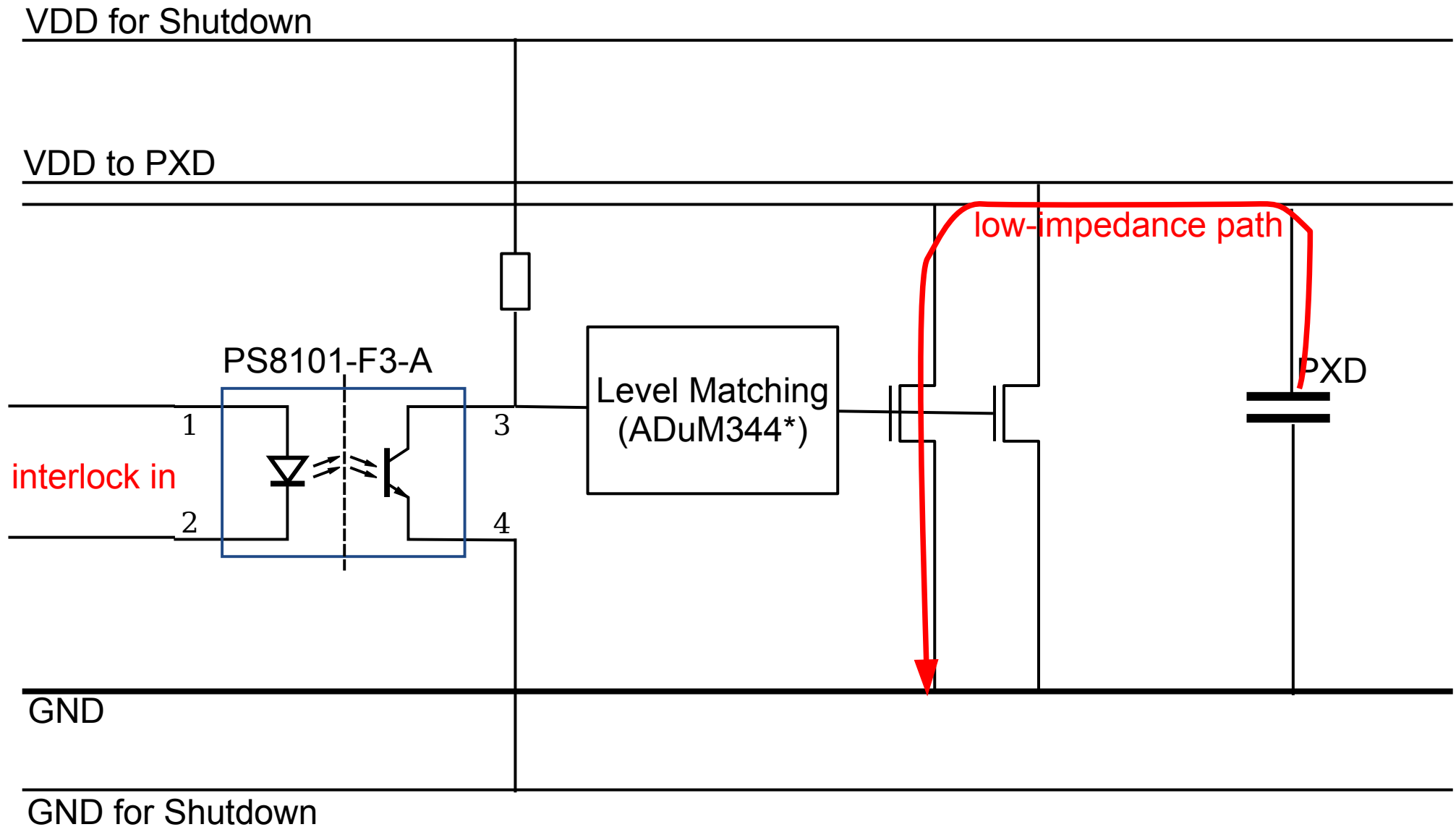

Same Input as PS


Power MOS  
to Shorten



- The PS is a modular design with
  - Back PCB
  - Front PCB
  - MCU card
  - Regulator cards (3 different kinds)
  - DC/DC card
  - OVP card
- All cards can be replaced independently.
- The interlock connectors are on the back PCB.
- Interlock handling is on the MCU card.
- Connections between all cards are on the Front PCB.
  - Also the output connectors.
  - ⇒ This is **the** central place.

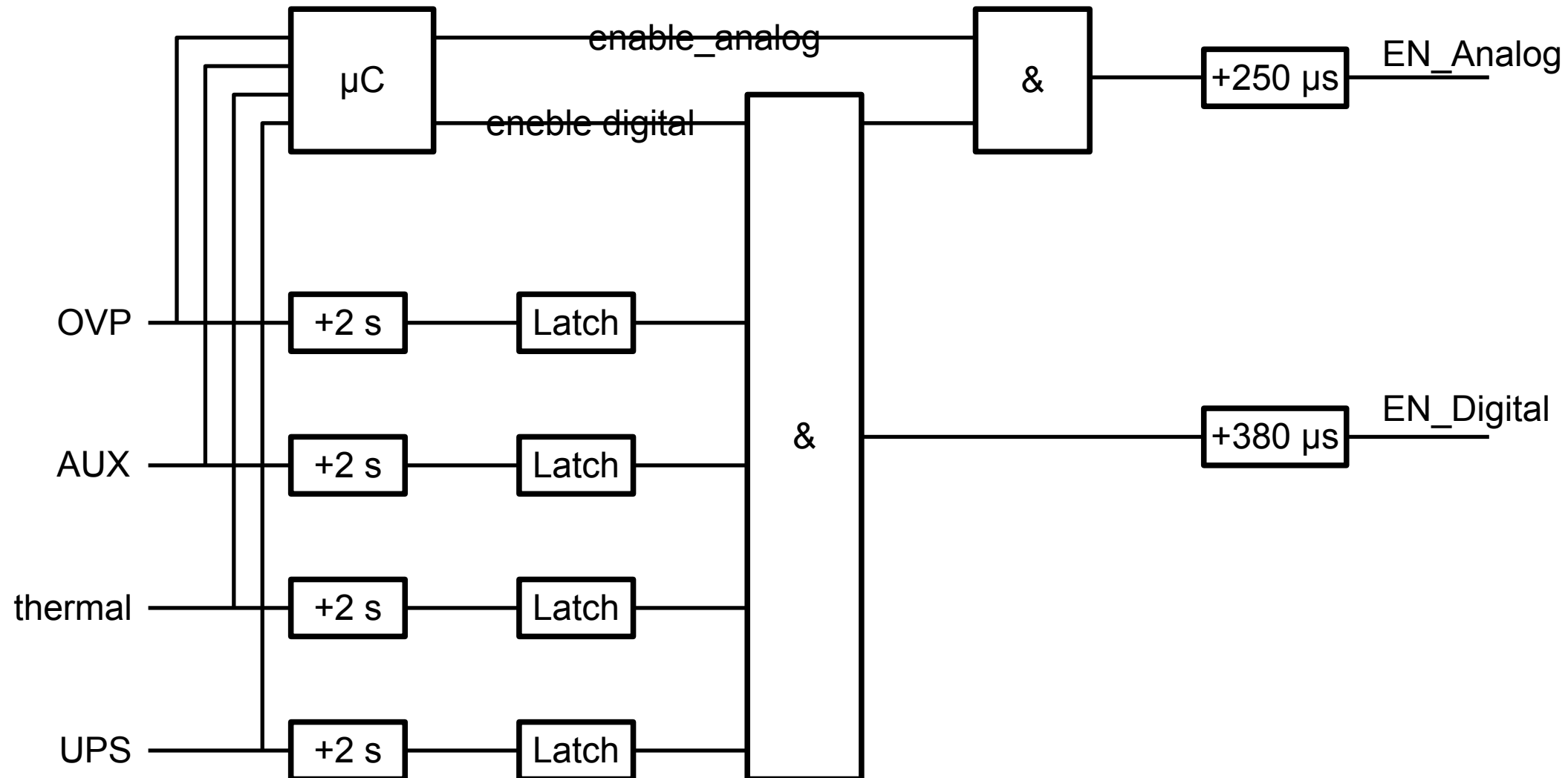
# Delays within the PS Unit

- Fixed delays to ensure „analog off first“.
- Purpose of the 2 second(!) delay at the input unclear.



 
# The Plan

- Remove all fixed delays inside the PS unit.
    - Just remove the parts and shorten input and output pads.
    - All on the MCU card.
  - On the Front PCB we have
    - All output signals.
    - GND/5V for all floating power domains.
    - The „enable“ signals, but not the interlock signals.
    - quite a bit of space
- ⇒ Place the fast shutdown circuitry here.


 
## Are There Other Options?


- The PS is a convenient place for the circuitry.
- But it's not the only one: There's also the Dockboxes
  - We can access all the voltages.
  - We can bring in a control signal.
  - The resistance to the modules is lower.
  - Problem: There's no fixed supply for each floating power domain.
- Shorting the outputs is an obvious improvement.
- Are there more ideas?



# Next Steps

 
## Next Steps for DCU Interlock

- Design the interlock receiver for the PS backplane.
- Verify the availability of the interlock signal on site (during B2GM).
  - Plan the cable routing for the last stretch to the PS rack.
- Understand the current interlock distribution cabling @ KEK.
- Verify availability of parts required for new batch of the PS Backplanes.


 
## Next Steps for Fast Shutdown

- Finish the layout of the test PCB.
- Modify one PS unit to remove all hardwired delays.
  - At this time check if it's suitable to access the interlock signal.  
Side remark: We always talk about „Fast **Emergency** Shutdown“.  
We do get that when we use the enable signals.  
With the interlock signal, its a „Fast **Interlock** Shutdown“.  
⇒ We need to decide what we actually want.
- Re-do the shutdown measurements with the modified PS and the test board.
  - Possible problems might come from initially very high currents when shorting a charged capacitor.
  - Measure discharge time.
  - Observe dhp-io.
  - ⇒ Hopefully confirmation that the idea is good.⇒ Go / No Go decision.
- Verify availability of parts required for new batch of the Front PCB.



Thank you!



## RC (C only on Kapton)

net	R	C	R×C
clear-off	6 $\Omega$	2.2 $\mu\text{F}$	13.2 $\mu\text{s}$
clear-on	4 $\Omega$	2.2 $\mu\text{F}$	8.8 $\mu\text{s}$
dcd-amplow	2 $\Omega$	22 $\mu\text{F}$	44 $\mu\text{s}$
dcd-avdd	1 $\Omega$	66 $\mu\text{F}$	66 $\mu\text{s}$
dcd-dvdd	2 $\Omega$	22 $\mu\text{F}$	44 $\mu\text{s}$
dcd-refin	11 $\Omega$	22 $\mu\text{F}$	242 $\mu\text{s}$
dhp-core	3 $\Omega$	22 $\mu\text{F}$	66 $\mu\text{s}$
dhp-io	5 $\Omega$	22 $\mu\text{F}$	110 $\mu\text{s}$
gate-off	5 $\Omega$	2.2 $\mu\text{F}$	11 $\mu\text{s}$
gate-on[123]	17 $\Omega$	2.2 $\mu\text{F}$	37.4 $\mu\text{s}$
source	20 $\Omega$	2.2 $\mu\text{F}$	44 $\mu\text{s}$
sw-dvdd	61 $\Omega$	2.2 $\mu\text{F}$	134.2 $\mu\text{s}$
sw-sub	4 $\Omega$	2.2 $\mu\text{F}$	8.8 $\mu\text{s}$

