



# BCM1F 'B.T.O.' Modules



## Outline

- Why 'Built to order' Modules?
- VETO Module
- Look Up Table
- Possible Extensions
- Summary



# BCM1F 'B.T.O.' Modules



## Why 'Built to order' Modules?

### a) lack of performance of commercial modules

Here: TDC buffer memory too small or readout too slow

*While block transfer is still in progress the buffer memory is already overwritten by new input data.*

### b) need for versatile, programmable functionality

Here: multiple logic operations on digitized sensor signals, supplemental i/o signals

*Request for a flexible, multi-channel coincidence logic to allow for a fast luminosity assessment.*



# BCM1F 'B.T.O.' Modules



## VETO Module (1)

TDC Block Transfer time (16k x 32bit): 3.7ms

2nd half of buffer is filled while 1st one being read out

-> overall input rate limit per channel to avoid overflow is:

$$\frac{50\% \text{ of buffer}}{\text{transfer time} * \text{nb. of channels} * \text{storage width}} = 0.54\text{MHz or } 1.85\mu\text{s}$$

Lumi estimation however gives 1.25MHz (800ns) Hit rate/channel

-> Inputs of TDC have to be blocked during readout!




# BCM1F 'B.T.O.' Modules



 
## VETO Module (2)

Designed and built on-purpose.  
Simple gating function:



 ... may as well be used as *OR* (common test)  
with inverted polarities








# BCM1F 'B.T.O.' Modules


 
## Look Up Table (1)

- Back-to-back trajectories allow estimation of luminosity
- Count coincidence rates between opposite sensors of BCM1
- Timing is in 1st approximation identical - same distance from I.P.  
(6ns time of flight)



A: -z TOP & +z BOTTOM  
B: +z TOP & -z BOTTOM  
C: +z NEAR & -z FAR  
D: -z NEAR & +z FAR




# BCM1F 'B.T.O.' Modules


 
## Look Up Table (2)

- General Purpose I/O Register v1495 (CAEN)
- 6U VME module with up to 6x32 channels in LVDS/ECL or TTL/NIM standard
- User configurable FPGA & several delay circuits on board
- 40MHz system clock





# BCM1F 'B.T.O.' Modules



## Look Up Table (3)

current functionality:

- Feed 8 digitized sensor inputs (diff. ECL) to the input
- Process 4 coincidences  
(and/or more functions such as synchronisation;  
selection is subject to user accessible registers)
- Provide 4 diff. ECL outputs to (external) scalers




# BCM1F 'B.T.O.' Modules



## Wiring of the modules

(courtesy of E. Castro Carballo)

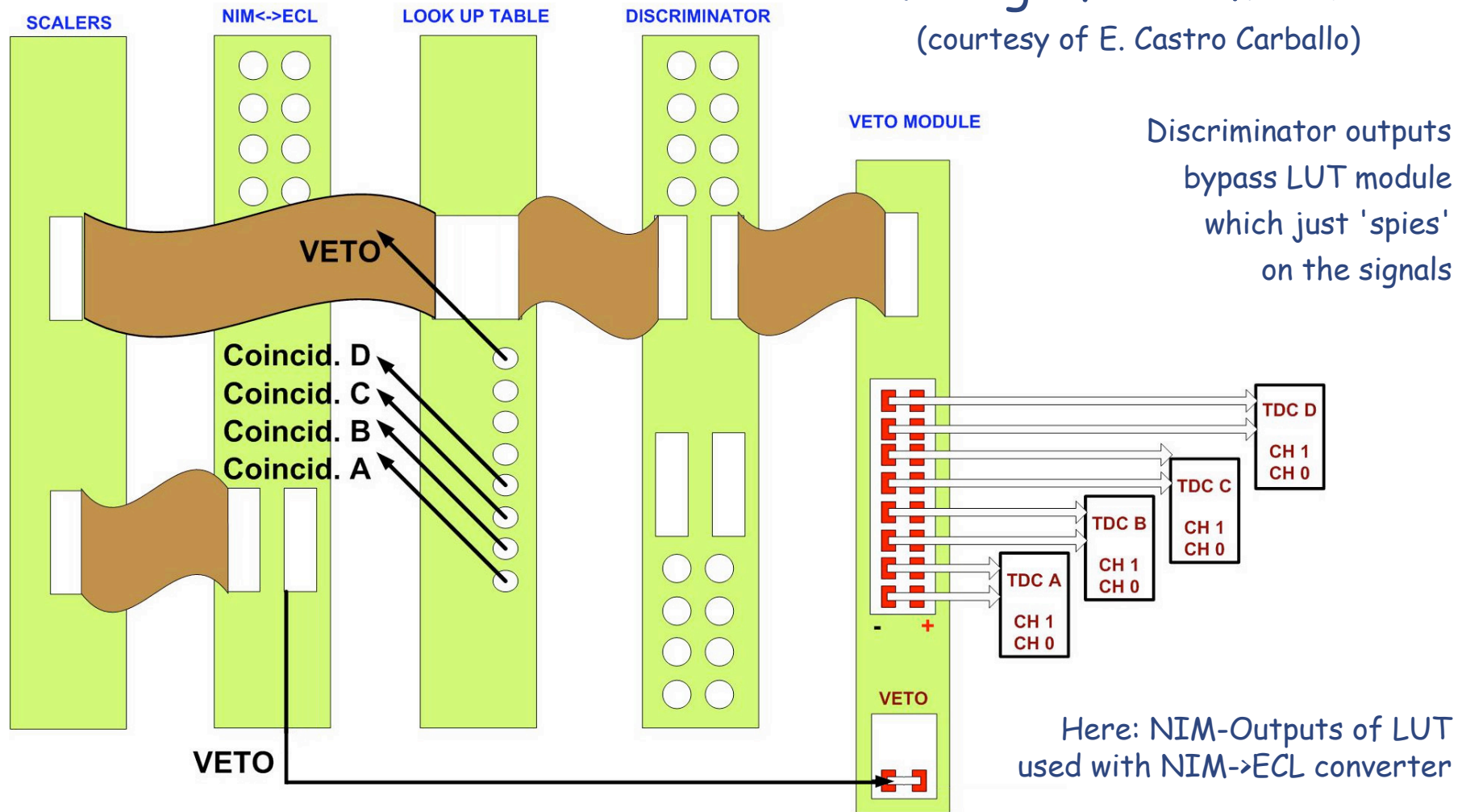



# BCM1F 'B.T.O.' Modules




## Look Up Table (4)


simple analog

OR


synchronized  
coincidence

 

 *Building a coincidence by  
simple logic AND function.*



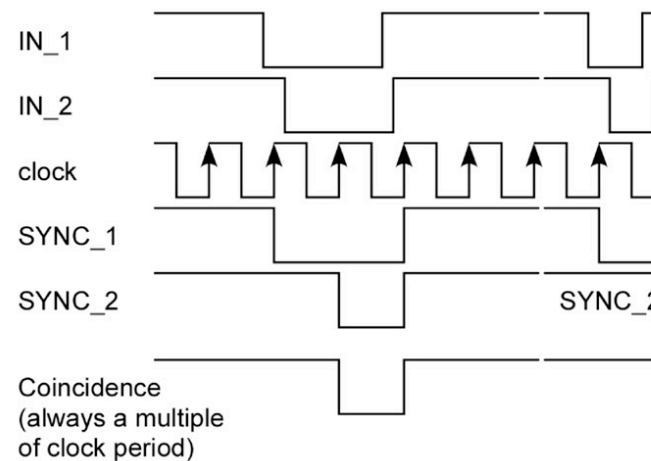*Problems when inputs are short  
and/or displaced in time!*



*Building a coincidence from  
synchronized input signals.*

*Problems when inputs are  
shorter than the clock period!*





# BCM1F 'B.T.O.' Modules



## Look Up Table (5)

- Programming of the module functionality in VHDL
- Compiling with manufacturer's software
- Flashing the module's non-volatile memory  
(Handler © M. Ohlerich/ R. Schmidt)
- Function is in effect after power-on

```
--#####  
-- Lookup table  
--#####  
  
SYNC: process(nLBRES, LCLK, DET_IN, BNCH_CLK)  
begin  
    if nLBRES = '0' then -- reset  
        SYNC_IN <= X"00";  
    elsif LCLK'event and LCLK='1' then -- run on LCLK clock  
        if UNIT_MODE = '1' then -- sync to internal clock  
            SYNC_IN <= DET_IN;  
        else -- don't sync  
            SYNC_IN <= DET_IN;  
        end if;  
    end if;  
end process;  
  
LUT: process(nLBRES, LCLK, SYNC_IN, COIN_OUT)  
begin  
    if nLBRES = '0' then -- reset  
        COIN_OUT(3 downto 0) <= X"0";  
    elsif LCLK'event and LCLK='1' then -- run on LCLK clock  
        -- mapping checked with updated wiki table (04feb10):  
        COIN_OUT(0) <= SYNC_IN(0) and SYNC_IN(5); -- -Top+Bot  
        COIN_OUT(1) <= SYNC_IN(1) and SYNC_IN(4); -- -Bot+Top  
        COIN_OUT(2) <= SYNC_IN(2) and SYNC_IN(3); -- -Out+Inn  
        COIN_OUT(3) <= SYNC_IN(6) and SYNC_IN(7); -- -Inn+Out  
    end if;  
    OR_OUT <= COIN_OUT(0) or COIN_OUT(1) or COIN_OUT(2) or COIN_OUT(3);  
end process;  
  
--#####
```



# BCM1F 'B.T.O.' Modules



## Look Up Table (6)

Additional features:

- Provide the gating signal for the VETO module by means of a dedicated register, which is written by the BCM1F operation program
- Latch the Beam Abort signal in a dedicated register, which is read by the BCM1F operation program

Possible extensions:

- Process more (or different) coincidences
- Implement the scalers for all coincidences
- Directly link the VETO to the DRDY signal of the TDC (exclude software interaction)
- Receive and multiplex other common LHC signals such as triggers



# BCM1F 'B.T.O.' Modules



## Summary

Two 'built to order' resp. 'programmed to order' modules have been successfully implemented into the readout system of the BCM1F:

- an on-purpose designed and manufactured ECL gating module and
- a versatile programmable commercial module.

Extensions of it's functionality are possible and planned.