

A Handheld Pulsar


with Realistic Detector Pulse Shape

Michael Wiebusch

GSI EEL - AESD


21.03.2022

- "Prelude" - The Battery Pulser

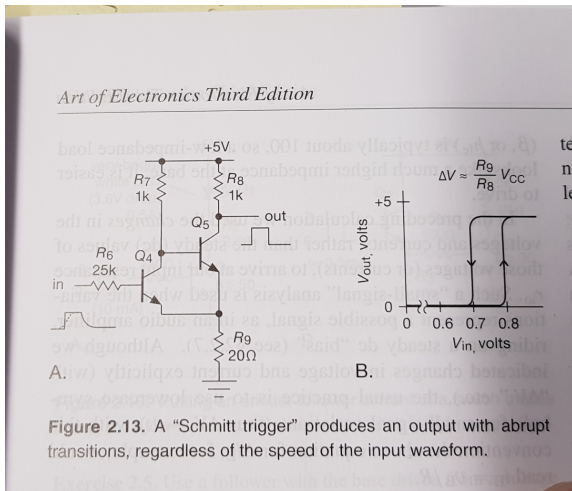


- From Paul Horowitz - The Art of Electronics
- Only two transistors to build a Schmitt trigger?
→ I did not know that!

A trip to SPICE land

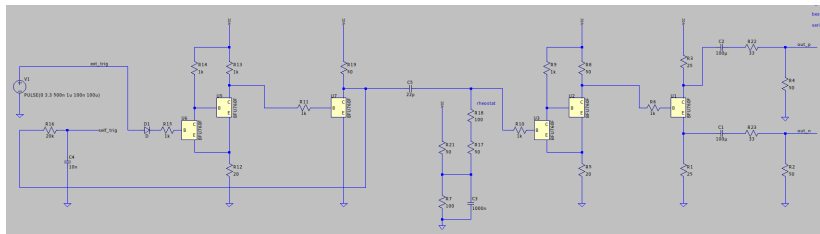


- ... It all started with fast transistors (BFU760, $f_T = 45\text{GHz}$) and SPICE
- We had a lot of these transistors in stock for building discrete preamplifiers.

Working principle

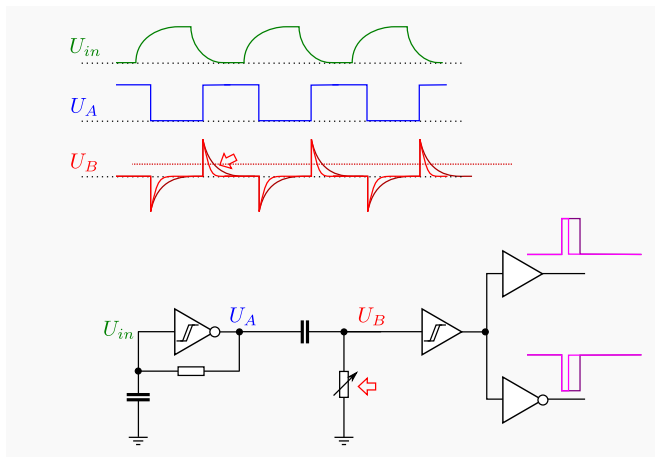


- (all with discrete transistors)

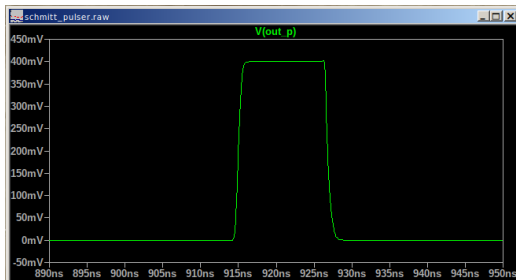


- It is short! (Pulse width down to several ns)
- It is fast! (sub-nanosecond edges!)
- It is clean! (no tails)
- Let's build this!

BatteryPulser1 PCB

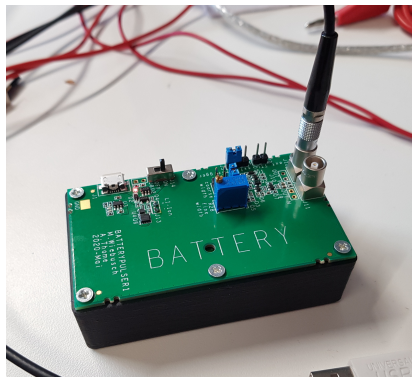


- Positive and negative polarity 50 Ω LEMO outputs, one can always be used as trigger out.
- Adjustable width (multiturn pot)
- On-board Li-Ion charger circuit
- 3d-printed case has space for recycled 18650 Li-Ion cell (from notebook battery)

BatteryPulser1 PCB performance


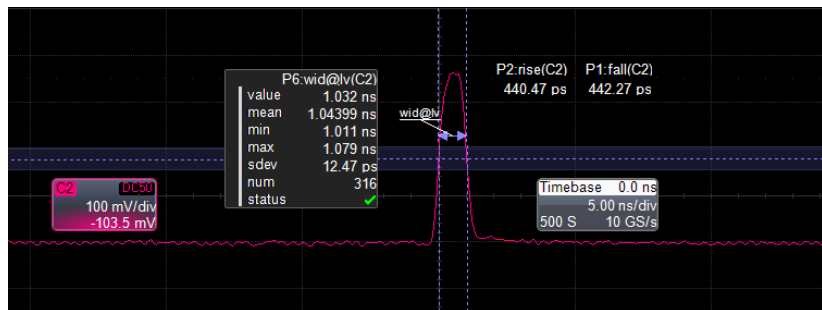


- pulse height = ± 400 mV
- FWHM = 1 μ s down to 1 ns
- edges ≈ 440 ps
- pulse width and timing is extremely stable

Games to play with BatteryPulser1

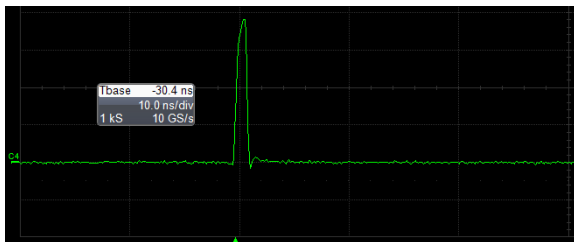

Games to play with BatteryPulser1

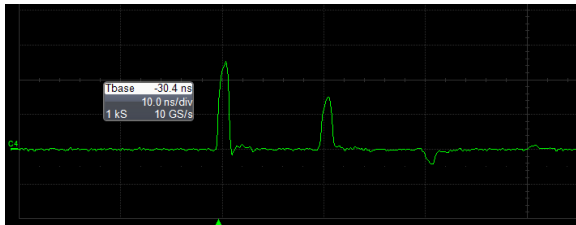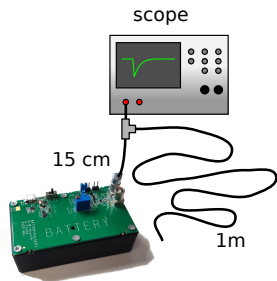

- "Main Course" - The Spectral Pulser

Question

- What else can we do with this technology?


Question

- What else can we do with this technology?
- Can we make pulses that look like detector signals?

Question

- What else can we do with this technology?
- Can we make pulses that look like detector signals?
- Can we have a charge/amplitude spectrum?


Working principle

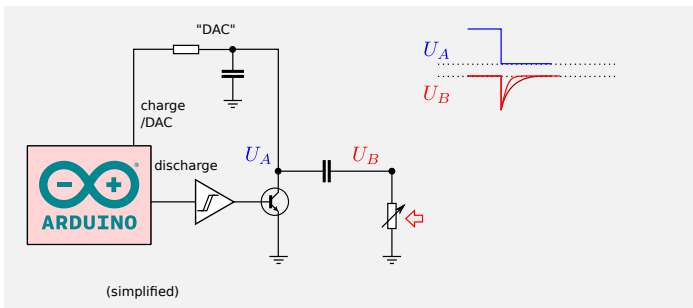

general principle

- Use GPIO pin to charge a capacitor to desired amplitude
- Trigger a fast transistor to discharge capacitor → create heaviside edge
- Feed edge into a CR filter to create an exponential pulse. Changing the "R" changes the tail.
- A subsequent RC filter can reduce the steepness of the leading edge



Working principle

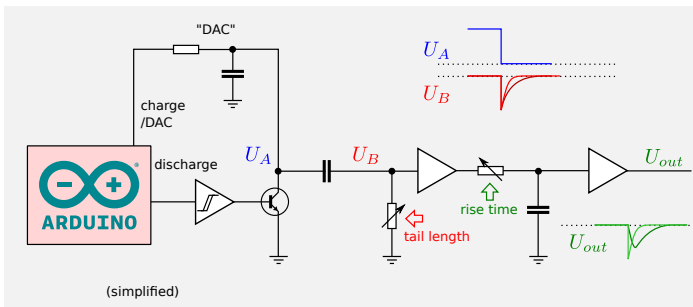

general principle



- Use GPIO pin to charge a capacitor to desired amplitude
- Trigger a fast transistor to discharge capacitor → create heaviside edge
- Feed edge into a CR filter to create an exponential pulse. Changing the "R" changes the tail.
- A subsequent RC filter can reduce the steepness of the leading edge

One shot PWM DAC

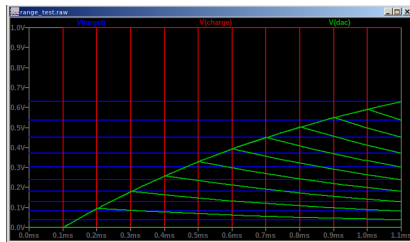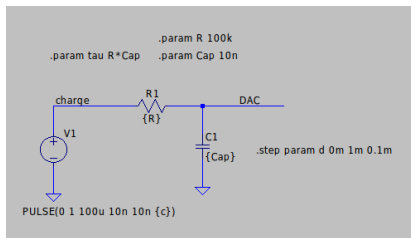

- Combination of RC charge and discharge
- Advantage over "charge-only" DAC:
 - Better precision for small amplitudes
 - No need for Tri-State or sample-and-hold
 - constant sampling time: $T_{charge} + T_{discharge} = T_{sample} = const$
- Above example: $\tau = RC = T_{sample} = 1\text{ ms}$
- The discharge helps improving the amplitude precision!

One shot PWM DAC

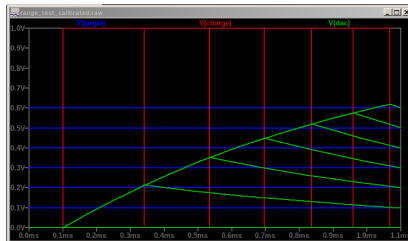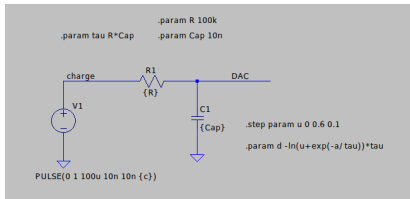

- There exists an analytic function to calculate charge/discharge time from desired target amplitude
- $\frac{d}{\tau} = -\ln\left(\frac{U_{DAC}}{3.3V} + e^{-(c+d)/\tau}\right)$
- $d = T_{discharge}$, $c = T_{charge}$, $\tau = RC$

Immitating detector seeing multiple "lines"


```
pro_micro_spectral_pulser | Arduino 1.8.10
File Edit Sketch Tools Help
pro_micro_spectral_pulser

void loop() {
  // put your main code here, to run repeatedly:

  int lines = 4;
  int i = rand0e(0,lines);


  switch(i){
    case 0:
      pulse_mv(100);
      break;
    case 1:
      pulse_mv(200);
      break;
    case 2:
      pulse_mv(50);
      break;
    case 3:
      pulse_mv(400);
      break;
  }
}

Done uploading.
```

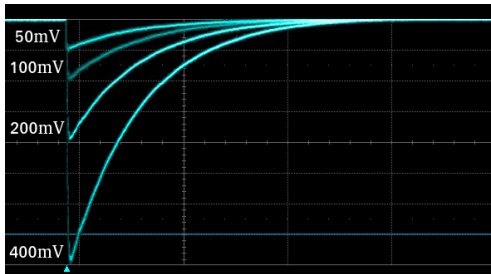


- The math can be done on a microcontroller and hidden behind high level functions

The Device - SpectralPulser1

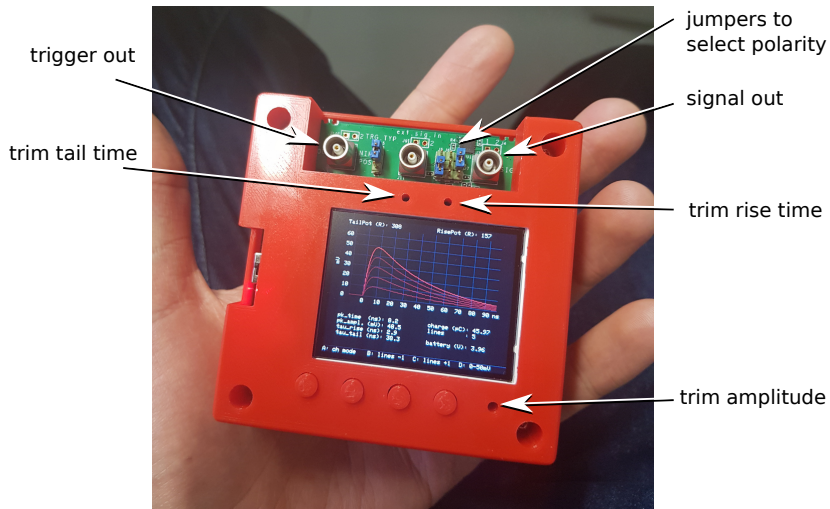


Preview vs scope

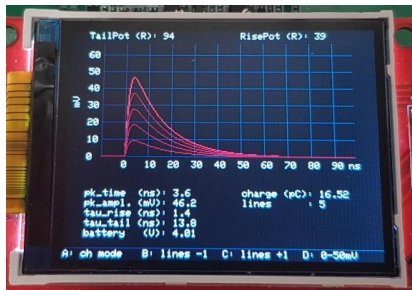



preview

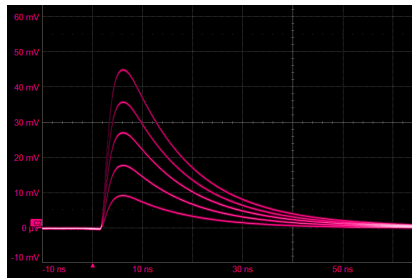- Model circuit behaviour with analytical function
- Plot function and print pulse characteristics on display
i.e. peaking time, peak amplitude, τ_{rise} , τ_{tail} , charge
- peaking time: 2 ns to 30 ns
- decay constant τ_{tail} : 3 ns to 110 ns
- Preview is not perfect, but within $\approx 5\%$ error margin
- 2.2" TFT with ILI9341 controller




scope (into 50 Ω)

Amplitude histogram

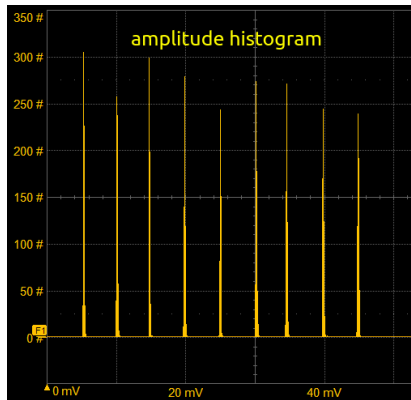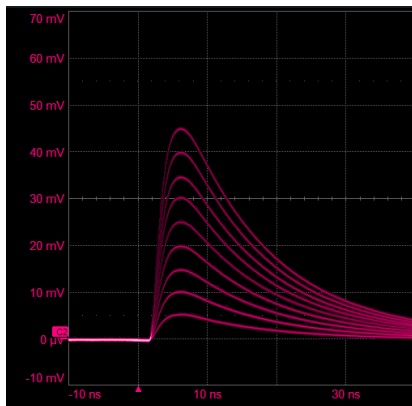


- Amplitude spectrum recorded on oscilloscope
- due to self-similarity of pulse \rightarrow amplitude spectrum \propto charge spectrum

SKY12347-362LF

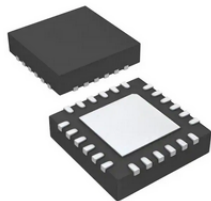


- The RC-DAC is only "half the truth"
- To extend the dynamic range a programmable RF attenuator IC is used:
SKY12347
- 0 dB to 31 dB in 0.5 dB steps
- DC-3 GHz (according to datasheet)
- 1 dB insertion loss
- 50 Ω in, 50 Ω out
- Attenuator sets "coarse" amplitude, RC-DAC sets remaining "fine" amplitude
- SpectralPulser1 has three amplitude ranges:
0 mV to 500 mV,
0 mV to 50 mV,
0 mV to 5 mV
- 0.1 pC to 1300 pC (also depends on τ_{tail})

Bonus Feature - Attenuator mode

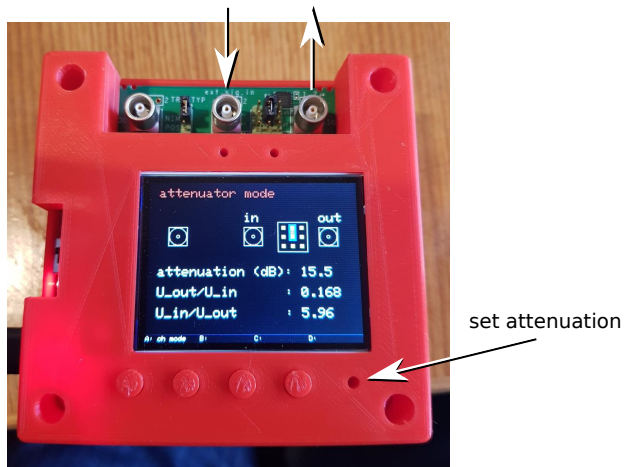

- What you see is what you get

What about the potentiometers?

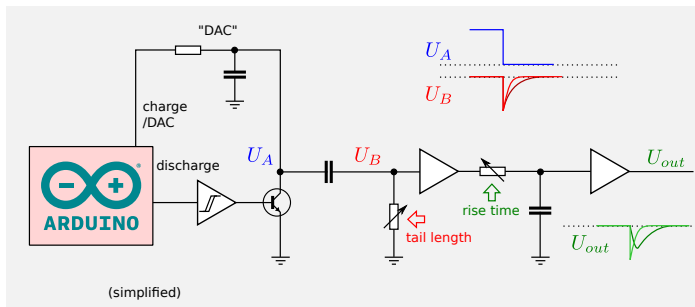


How do we read out the multturn potentiometers?


- The trimmers determine the shape of the pulses.
- Cannot use digital potentiometers, not HF compatible.
- The pulses are very fast, only AC properties matter → AC coupling.
- With GPIOs and additional transistors trimmers can be made part of DC voltage dividers, measure voltage drop on trimmer with Arduino ADC pin.
- After each few hundred pulses, read out potentiometers and update plot.

Example - Testing a Preamp


preamp output

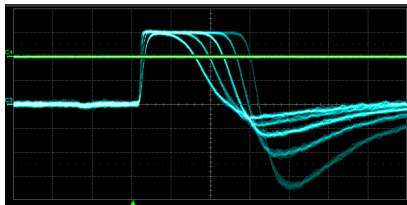

preamp output ToT spectrum

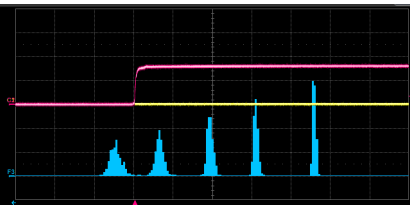

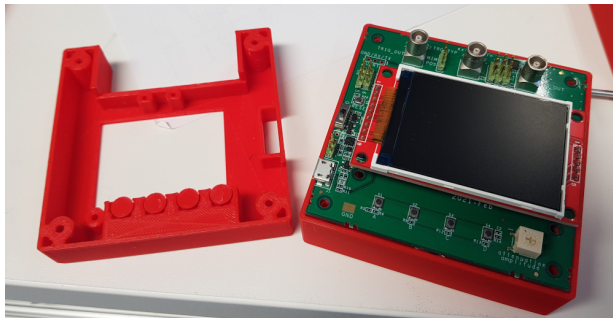- With scope persistence you can directly see how the amplifier responds to different charges/amplitudes
- Directly see walk!



- 3d printed - designed (coded) in OpenSCAD
- there is room in "the basement" for 1-2 Li-Ion cells

Thank you for your attention