


aCSPMA12 PCB design

(assembly/)a Cherenkov Silicon PhotoMultiplier Array
Printed Circuit Board design review

Daniel Klein

DESY, FH-FTX-SLB-LUXE meeting
14th December 2023

Cherenkov detector

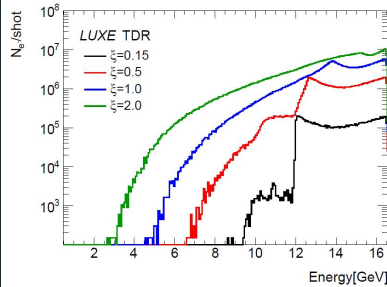

Cherenkov detector


photodetectors

15.5 GeV
13.5 GeV
9 GeV
5 GeV

scintillator screen
+ camera system

e^- trajectories

dipole magnet

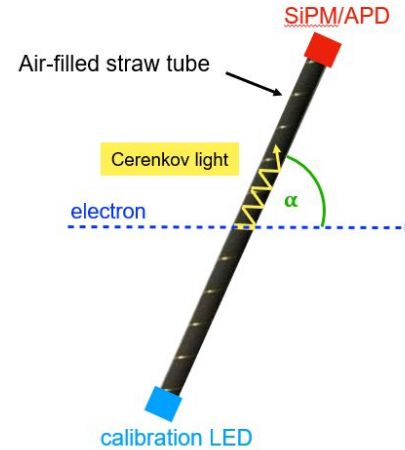

High e^- rate from Compton scattering- Sig/Bkg ~ 100

Goal: Measure non-linear Compton spectrum- Compton edges shift as function of the Laser intensity.

Dipole spectrometer + combined detector: Scintillator screens and segmented gaseous Cherenkov detector.

Straw tube light guides: Cherenkov light in air reflected towards photodetector.

Topics encountered

Why do we do this? Cherenkov detectors

Geometry choices

The importance of scientific communication





Noise filtering - in series or parallel? Measurements / Experimenting with filters

Impedance matching & Readout line biasing

electrical Schematic

V.00 - multiple options?

Power budget?
5U 7mA for ?

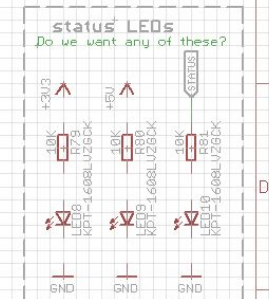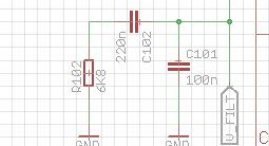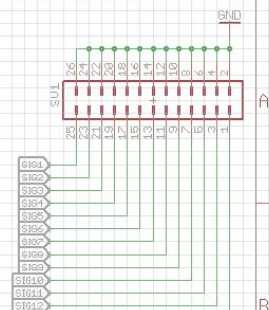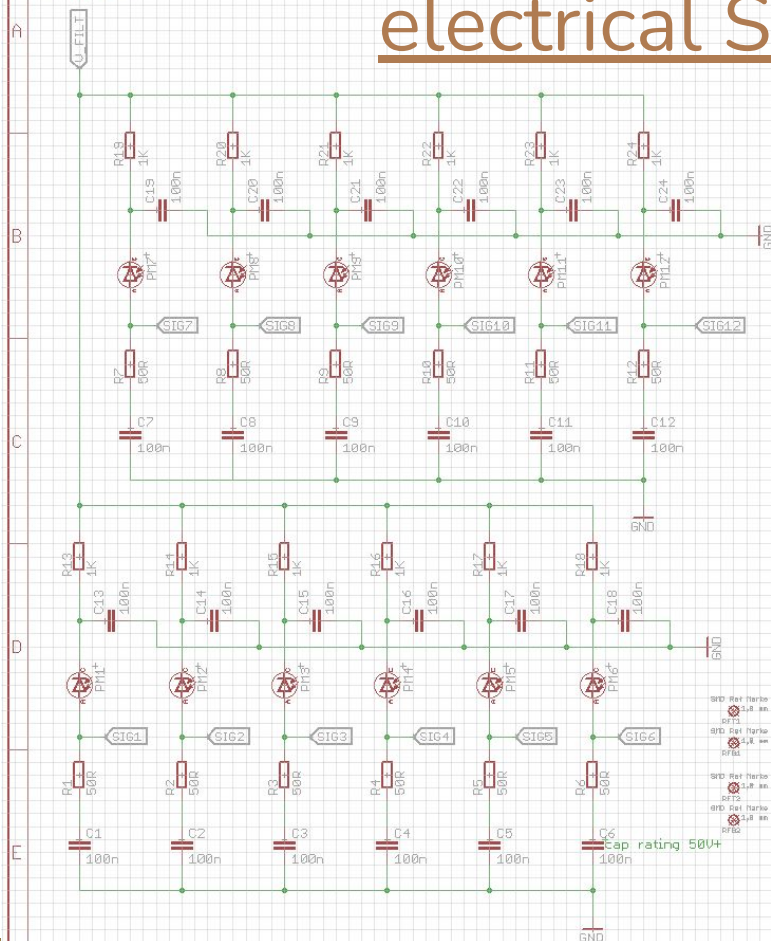

connect screw mounts to GND?



DESYP-LP-Nr.:

Benennung: aCSPMA12

Kurzbeschreibung:

Gezeich. für Gruppe FS-LA

Geänd. Anforderer

Freigabe WA-Nr:

Dates: not saved!

Size:

DESYP
Hamburg

(C) DESYP FS-LA


DESYP behält sich alle Rechte vor.
Schwerpunkt: 100 Jahre
all rights reserved, reserved to
production notice 100 Jahre.
Further enquiries please contact
DESYP group IT-IT
Tel: +49 40 2000-3020

Sheet: 1/1

aCSPMA12.v1 2023-12-13
kleindan 8 DESX FH-FTX-SLB-LUXE

LED10 LED9 LED8

Board layout (polygons hidden)

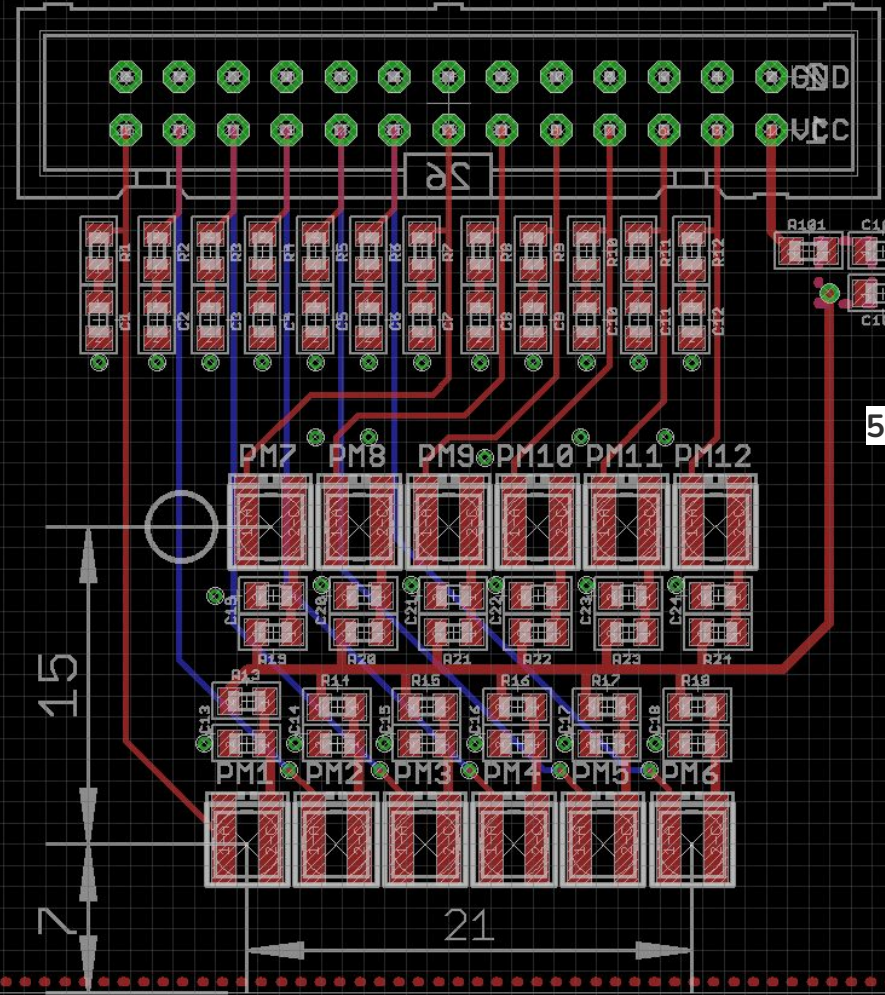



50*80mm = 1/4 "Eurocard"


notted

top



Power in- connector and filter

Filtering the input voltage ~40V

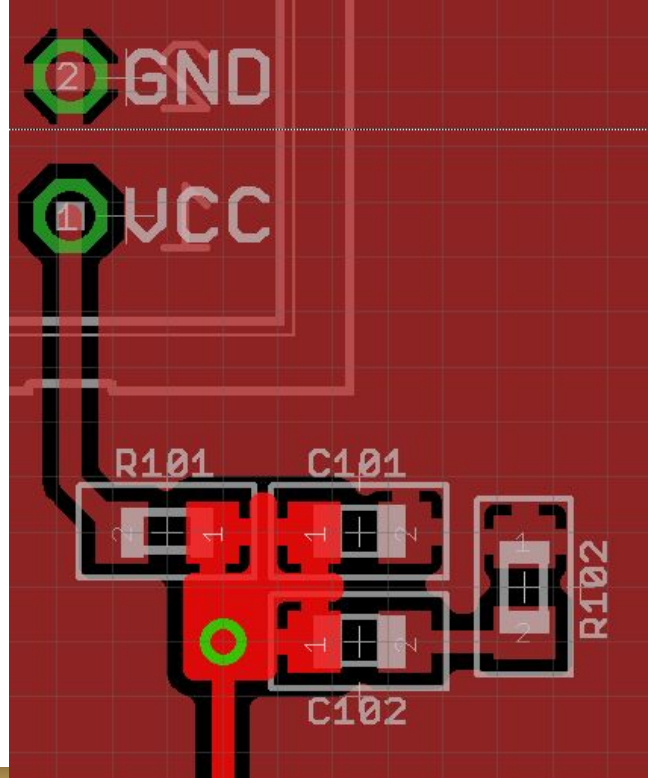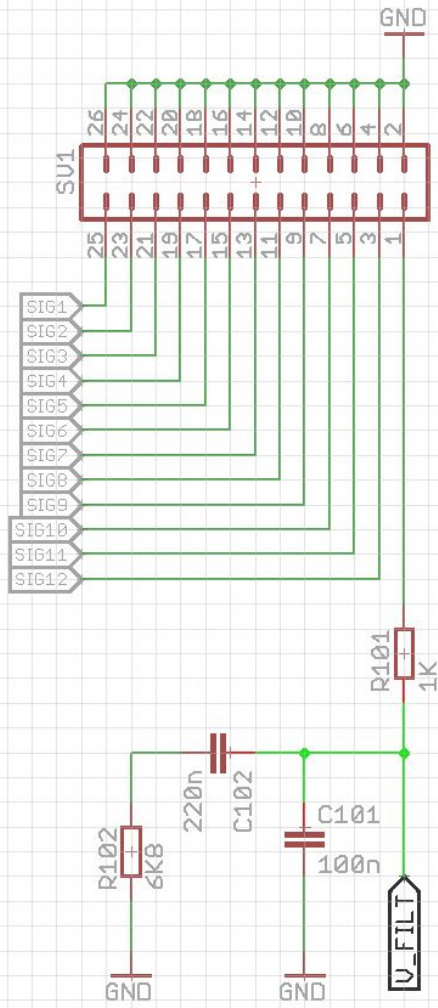

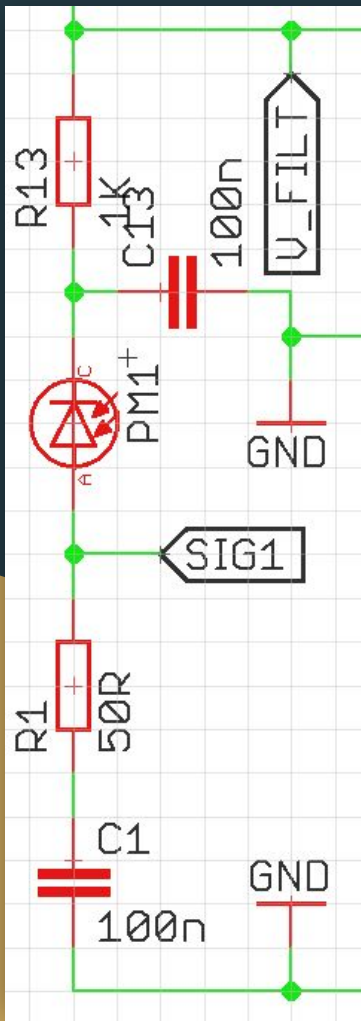

SiPM unit

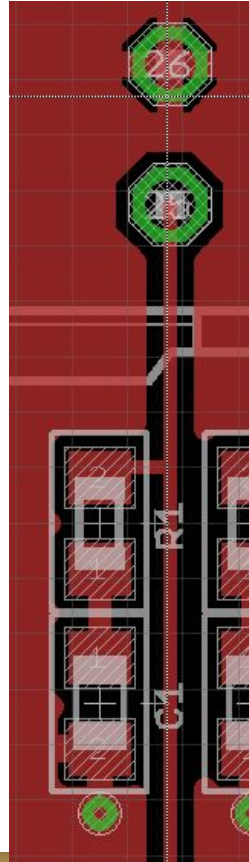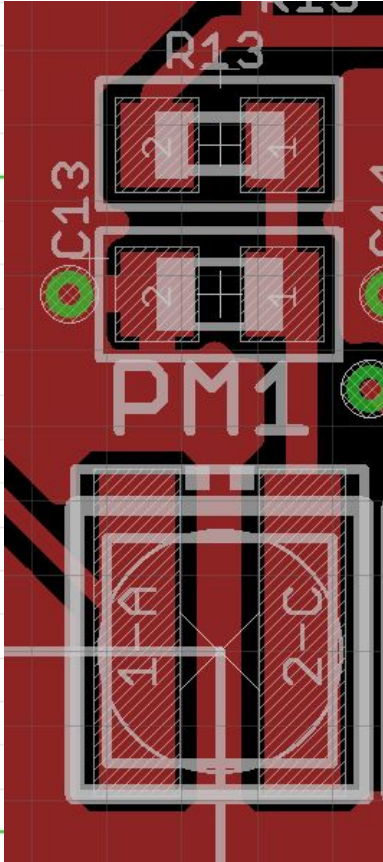


- Schematic, signals
- PM unit, input V
- Output, impedance matching and DC bias blocking



The impedance matching issue

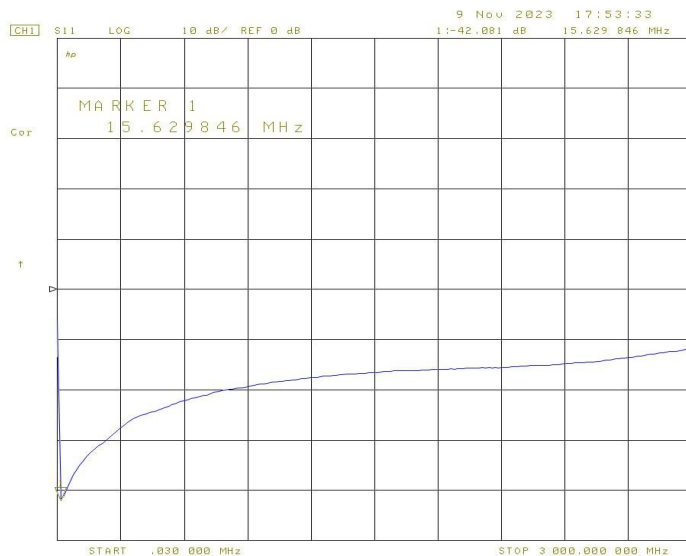We deliberated for a while how to correctly dress the output lines leading from the SiPMs to the ADC readout pins.



Outlook - near future / planned research

Polishing and ordering v1 PCBs (from multi-cb)

mid-January: Experimental measurements - lock down component values - order components if necessary.

late-Jan / early-February: Printing and in-house assembly :-)

Tackle another part of detector?

Write first thesis chapter?

END

aCSPMA12.v1 + 2023-12-13
kleindan e -FH-FTX-SLB-LUXE

LED10 LED9 LED8

Board layout

50*80mm = 1/4 "Eurocard"


40

70

21

15

7

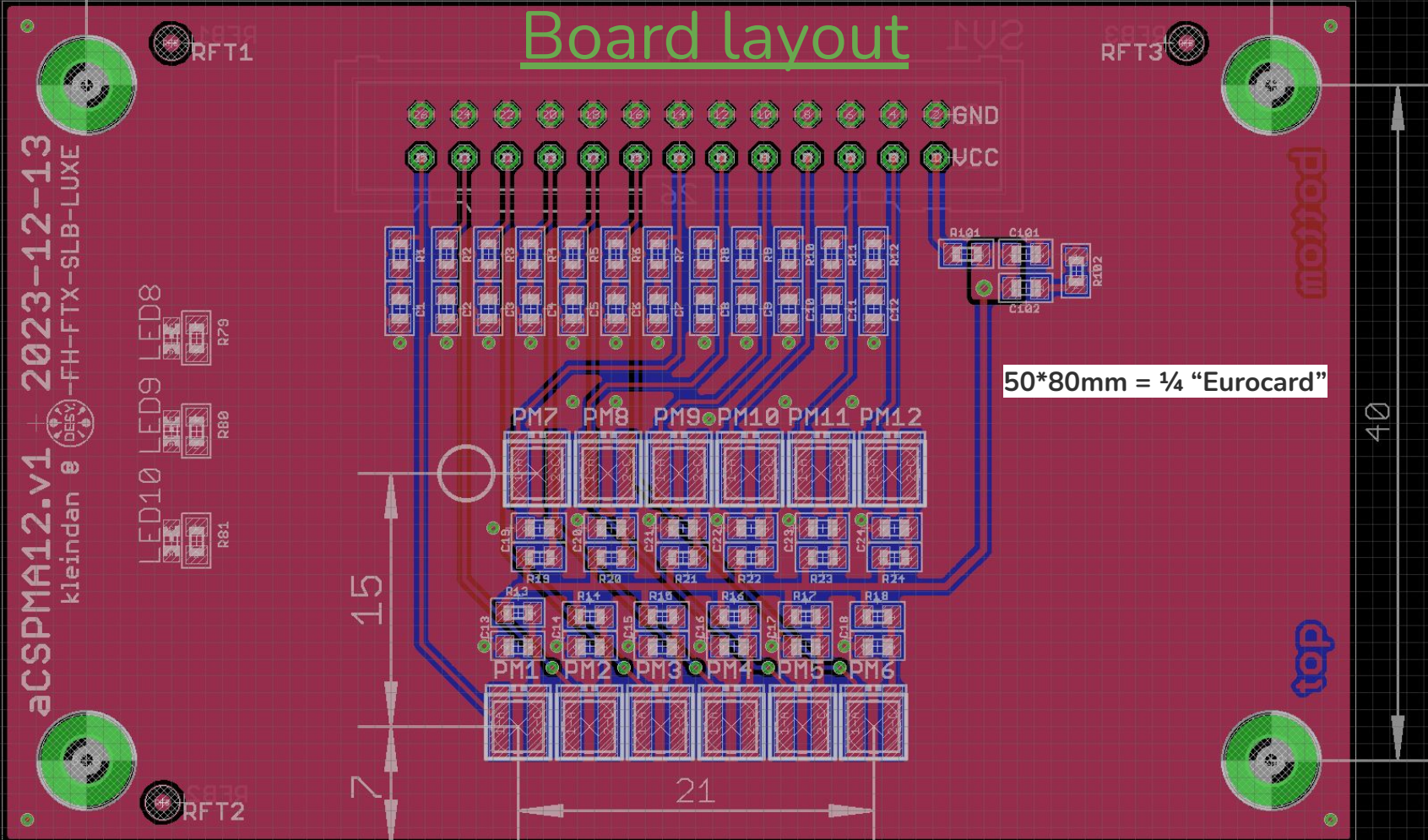

Prelim takeaway

~~A little text on each slide — this is the takeaway~~

~~What is the cherenkov detector~~

~~Graph and illus from p4 in CDT presentation~~


~~Illus from p6~~

~~Zoomed cutouts of relevant circuit/board sections while highlighting certain topics~~


~~Outlook slide — future planned research — measurements/experiments in Jan — Printing and assembly in Feb, hopefully~~

Send slides to Antonios to discuss order of story telling

Send slides to Gudrid in advance

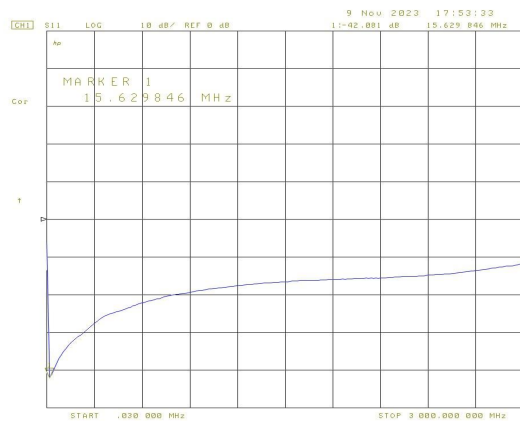

S11

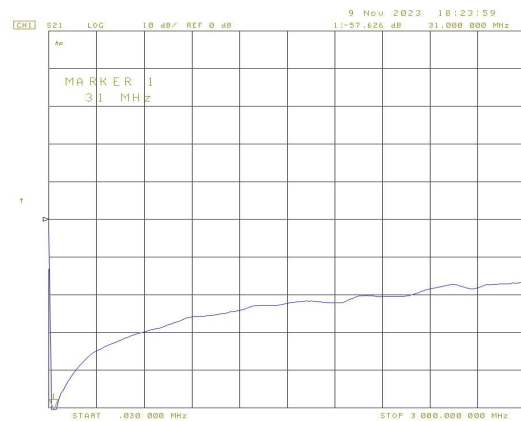

S21

