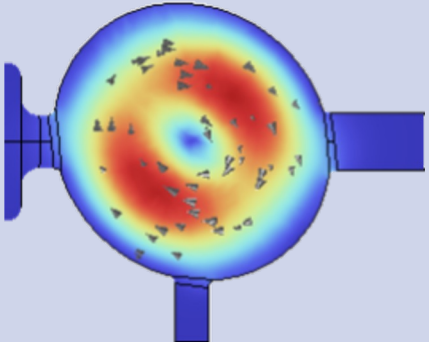
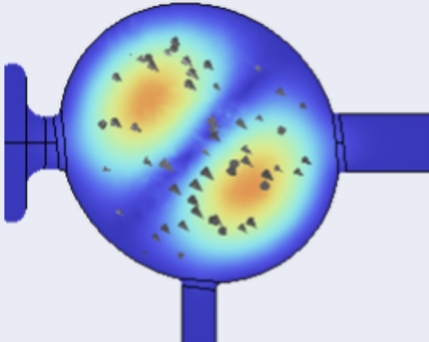
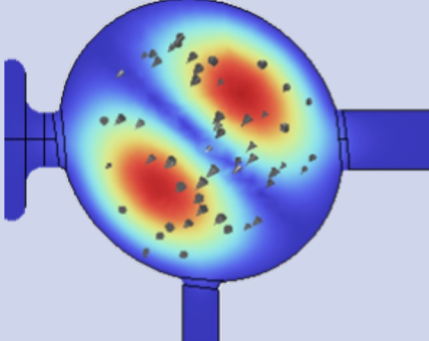




Electromagnetic Modes of the MAGO Cavity

Status Update

Tom Krokotsch, Lars Fischer


Warm Measurement of EM Modes in MAGO cavity

Simulated Eigenfrequency	Electric Field Distributions
(previous mode ~1.80 GHz) 2.07306 GHz (Pi-mode) 2.07311 GHz (0-mode)	
2.07710 GHz 2.07717 GHz (probably bad coupling to antenna)	
TE ₀₁₁ 2.10381 GHz 2.10390 GHz (next mode: ~2.26 GHz)	

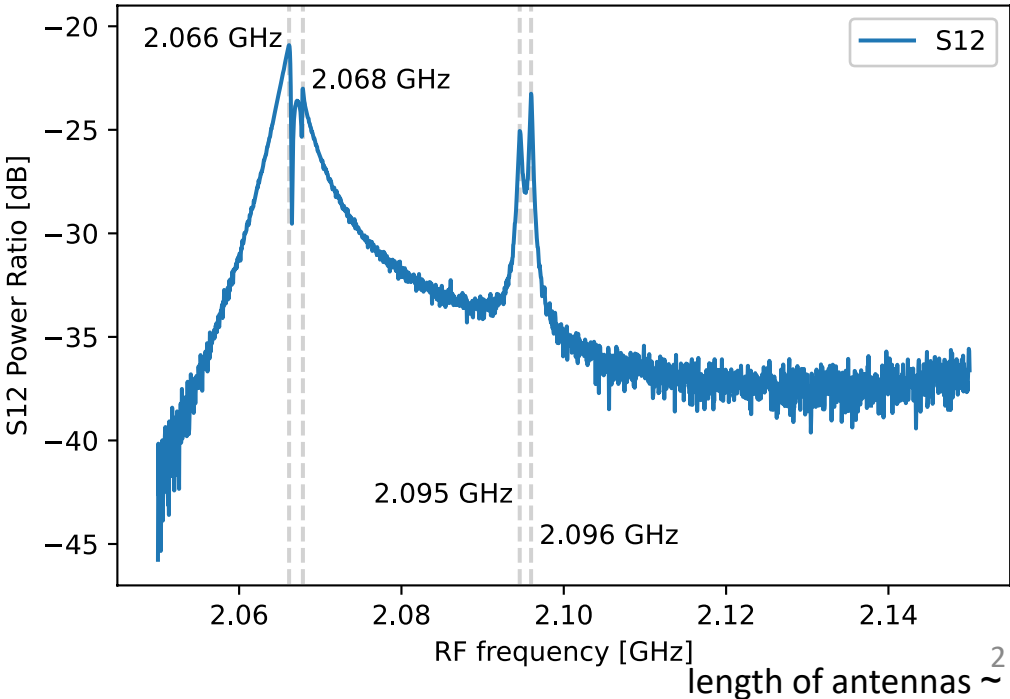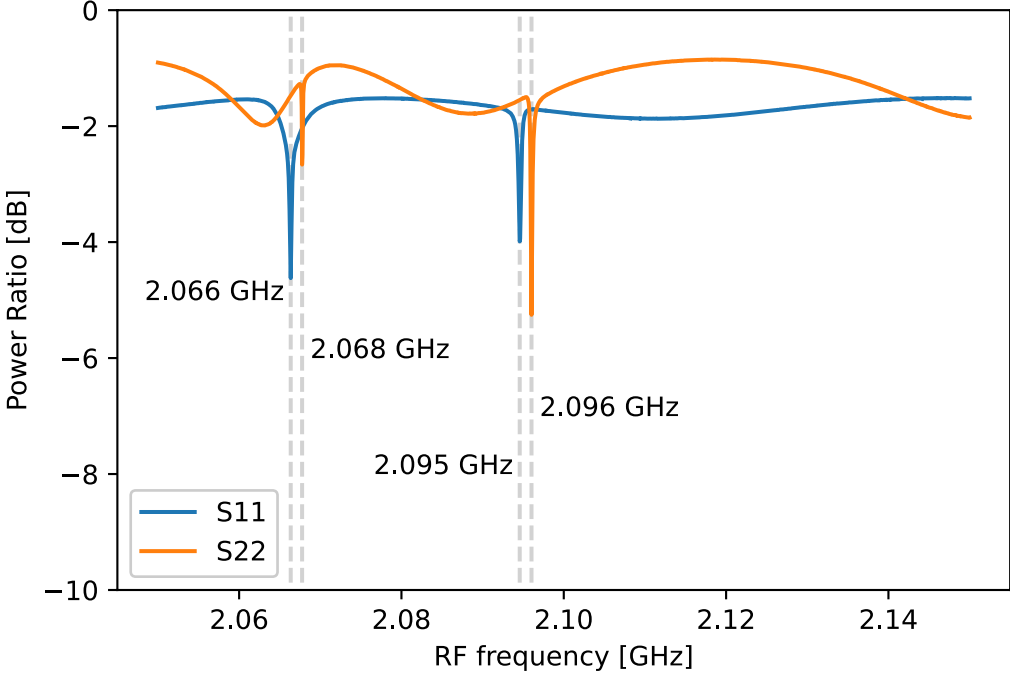


length of antennas ² ~ 11 cm

Shorting the Cavity: Pictures

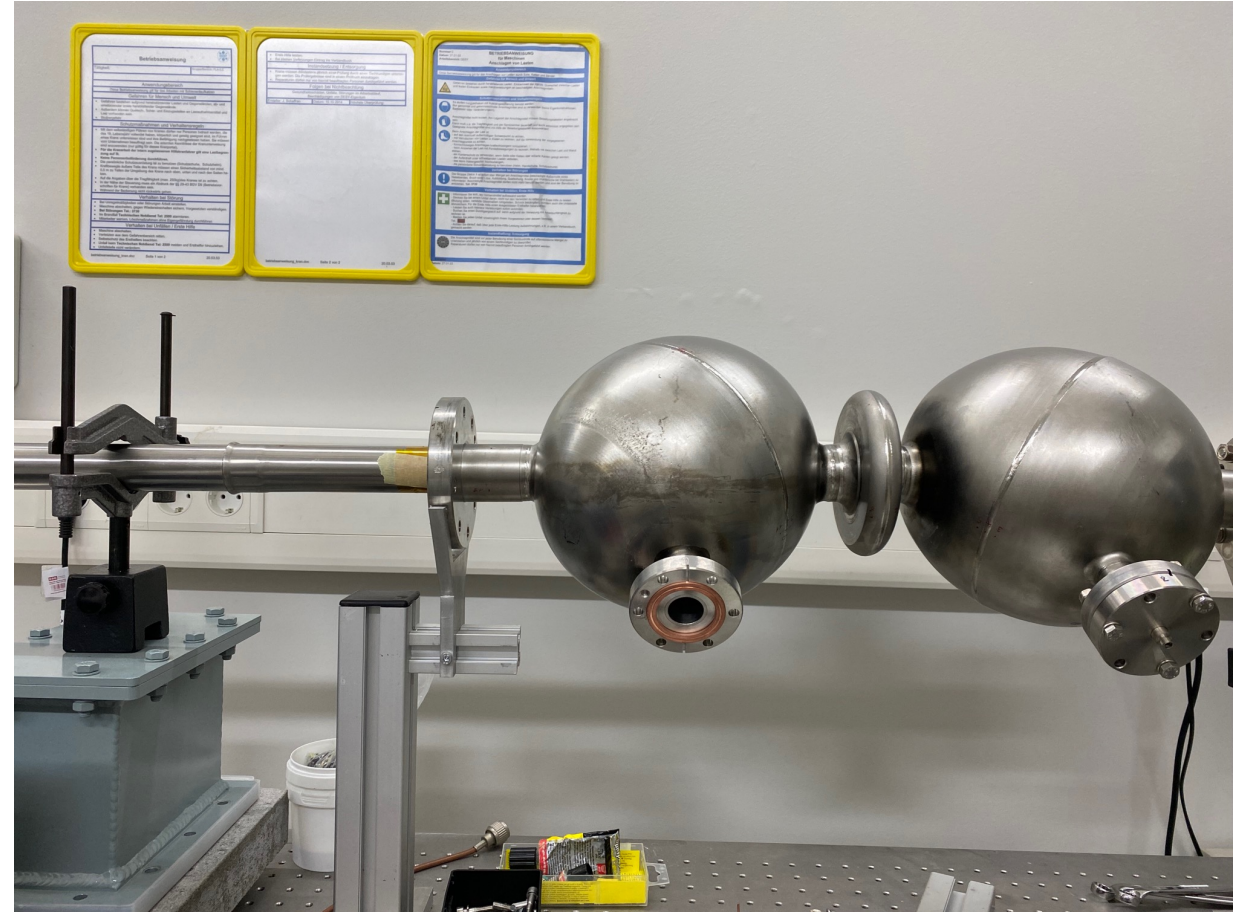


Shorting the Cavity: Results

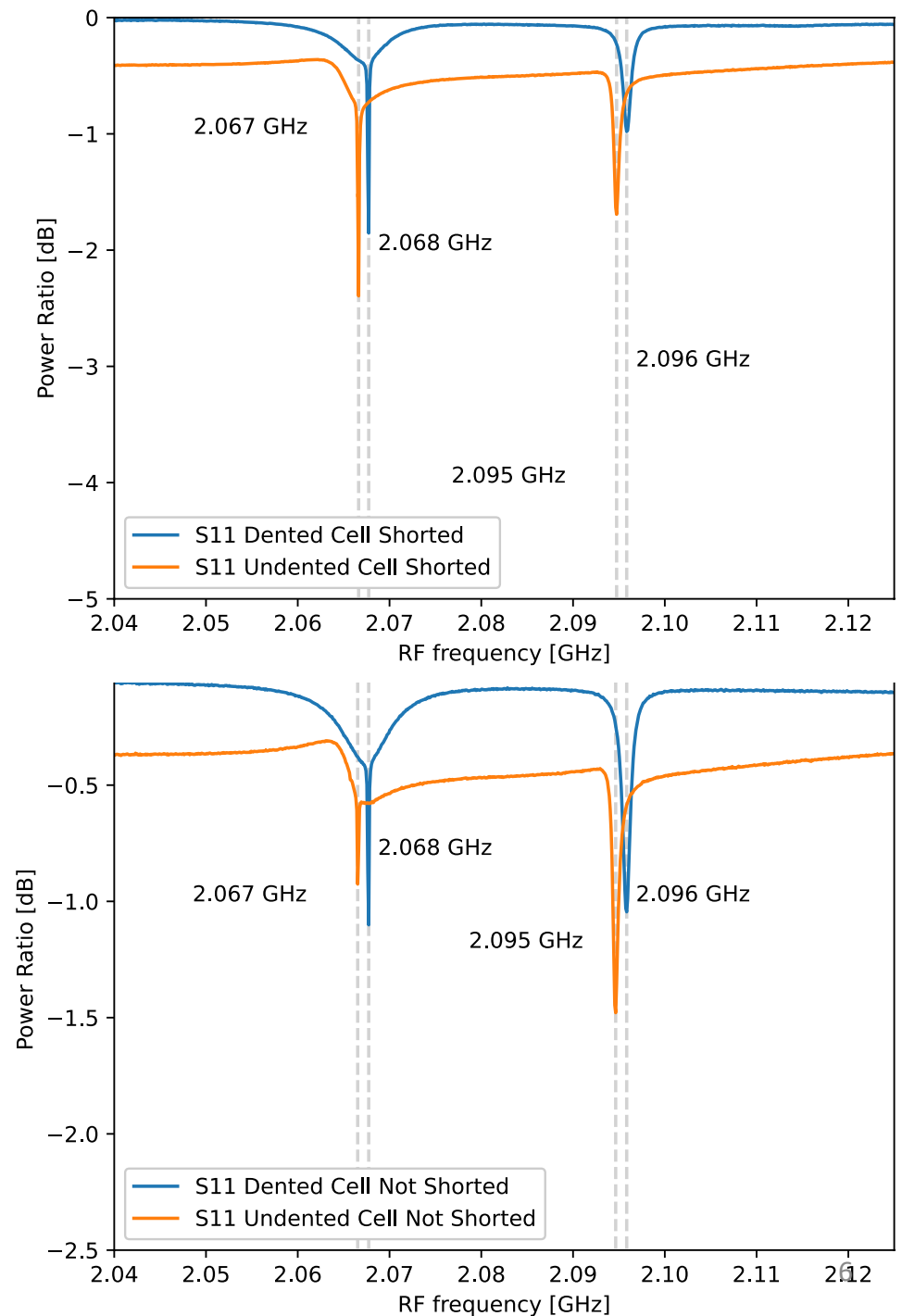- The Eigenfrequencies of the single cells are identical to the non-shorted case
- They also (almost) match with the previous results (slide 1)



Explanation through Equivalent Circuits


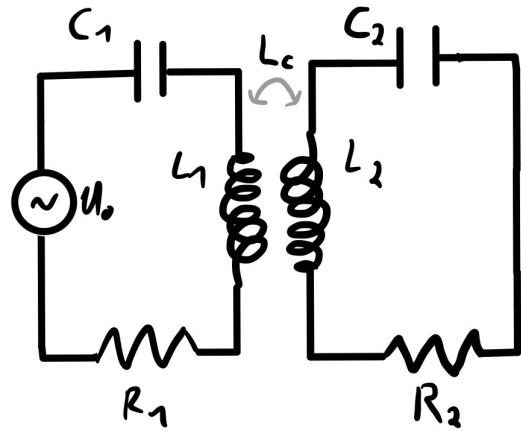


- Model the two MAGO cells as inductively coupled RLC circuits
- External oscillator $U(t)$ in circuit 1
- Mechanical analogue: double pendulum (small angles)

• E.O.Ms:

$$L_1 \ddot{I}_1 + R_1 \dot{I}_1 + \frac{1}{C_1} I_1 = -L_c \ddot{I}_2 + \dot{u}$$
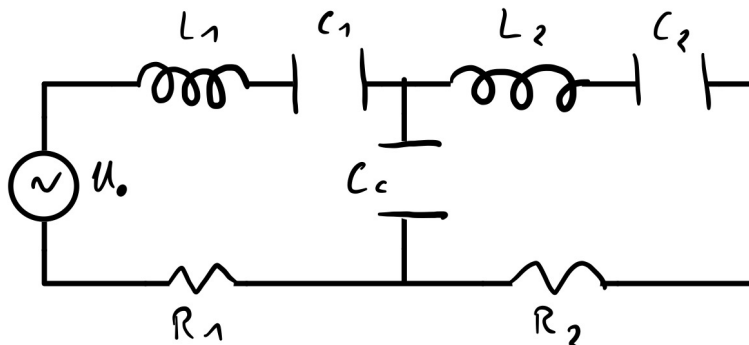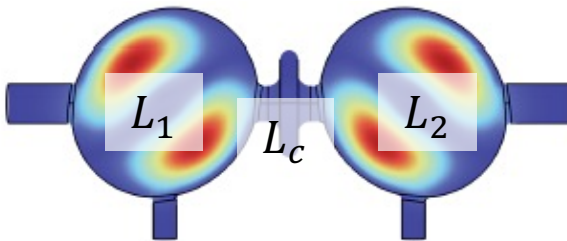
$$L_2 \ddot{I}_2 + R_2 \dot{I}_2 + \frac{1}{C_2} I_2 = -L_c \ddot{I}_1$$



- Capacitively coupled circuits yield same qualitative results
- Mechanical analogue: coupled pendula (small angles)

• E.O.Ms: replace $L_c \frac{d^2}{dt^2} \rightarrow 1/C_c$



Solution of the coupled E.O.Ms

- Define parameters



- $k = L_c / \sqrt{L_1 L_2}$ (coupling strength)

- $\Delta\Omega = \Omega_2 - \Omega_1$, $\Omega_i = \frac{1}{\sqrt{L_i C_i}}$
 (single cell Eigenfrequencies)

- $\omega_\pi - \omega_0 \approx k \frac{\Omega_1 + \Omega_2}{2} \approx k \frac{\omega_\pi + \omega_0}{2}$

valid for $1 \gg k \gg \frac{\omega_2 - \omega_1}{(\omega_1 + \omega_2)/2}$ and $R_1 = R_2 \approx 0$

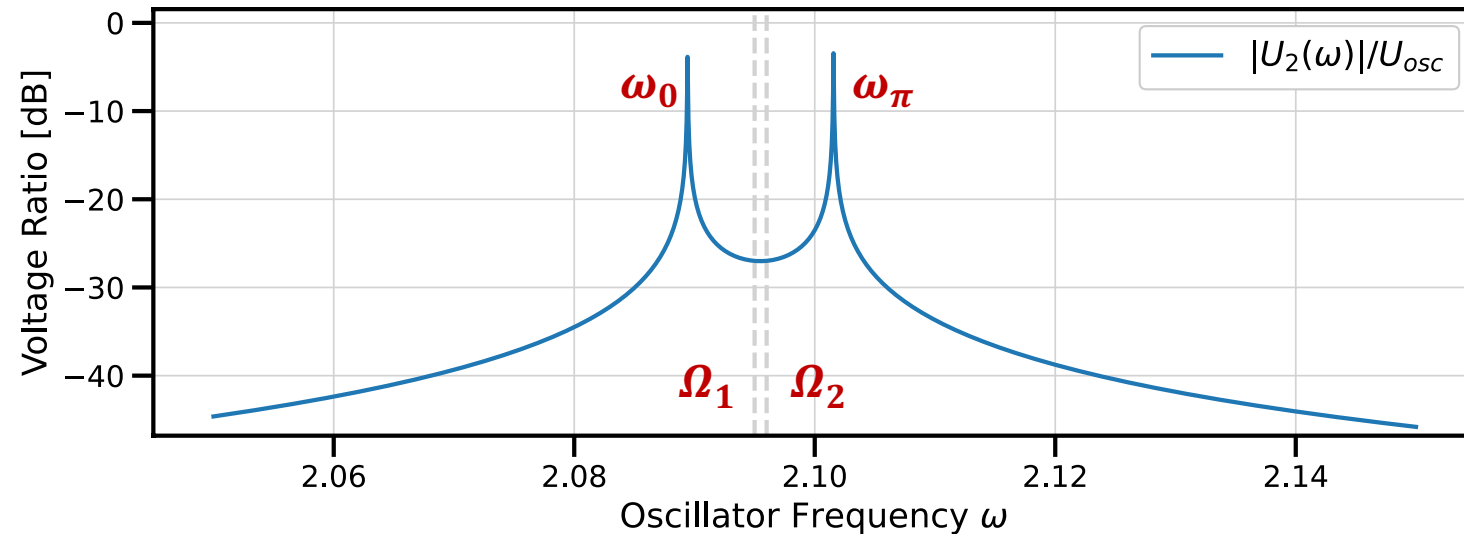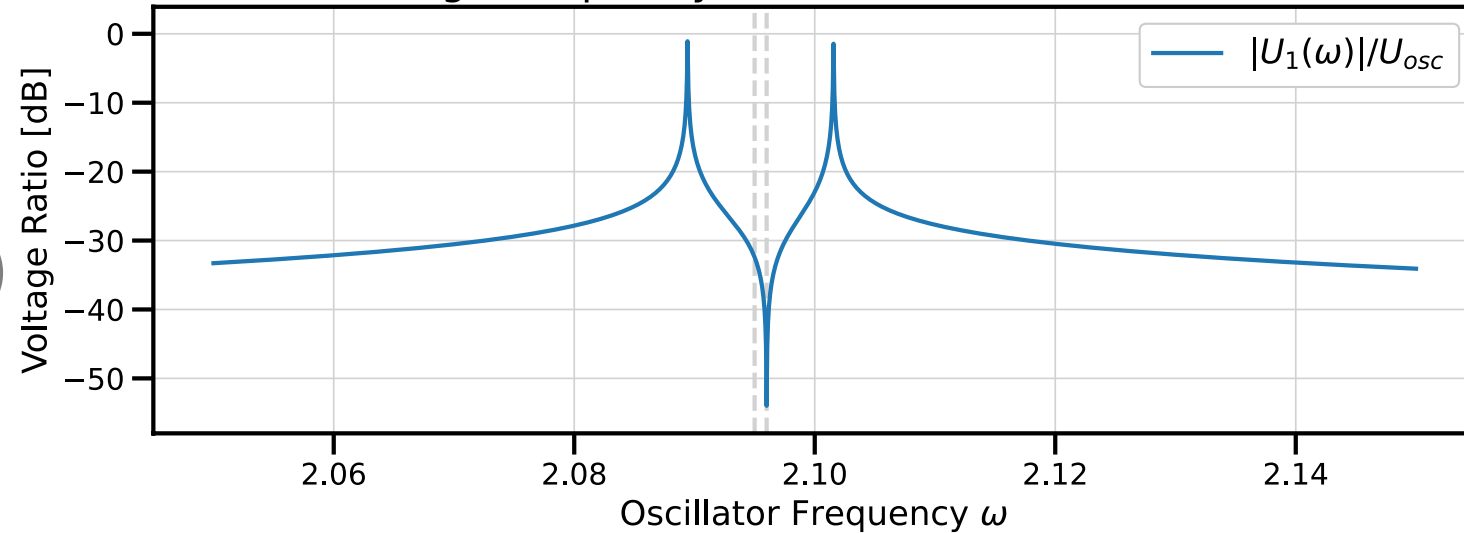Voltage Frequency Distribution in Both Circuits




$$k = 10^{-2}, \quad \Delta\Omega = 1 \text{ MHz}$$

Solution in The Time Domain



→ Fourier transform spectrum assuming $U_0 = U_{osc} \sin(\omega_{peak} t)$

Symmetric (0) Mode ω_0

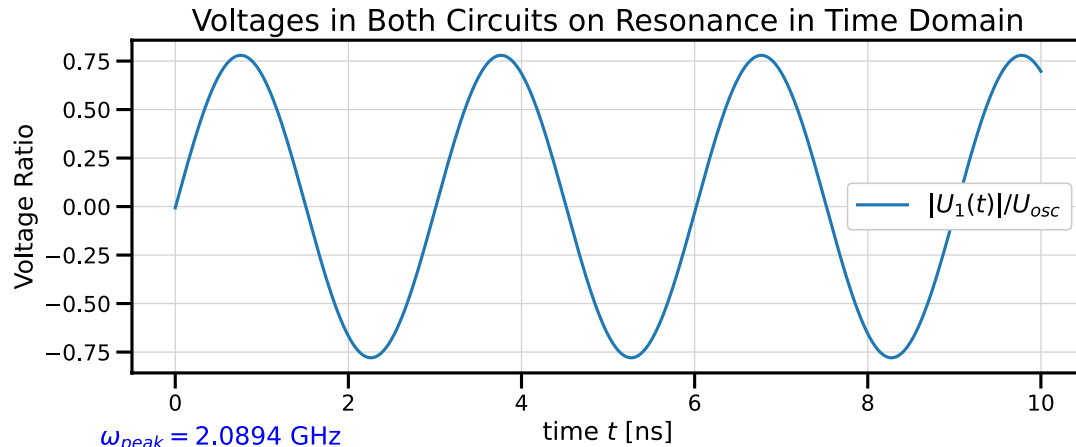


Circuit 1

Antisymmetric (π) Mode ω_π

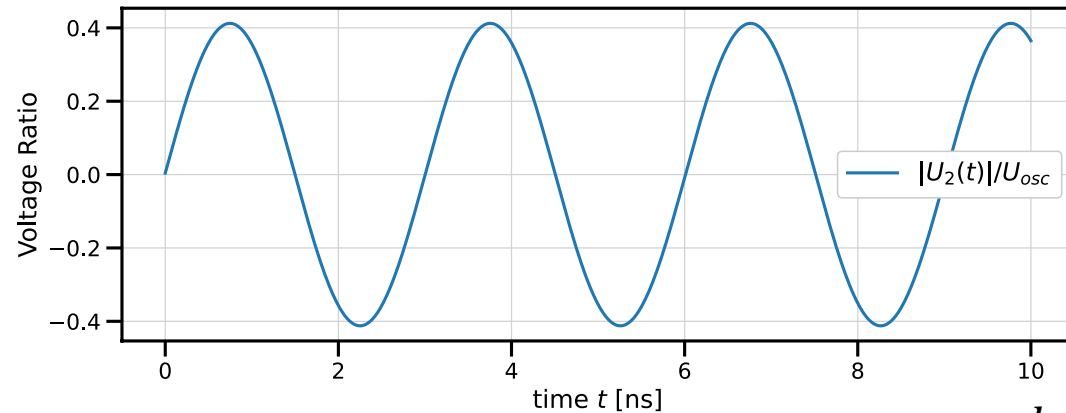
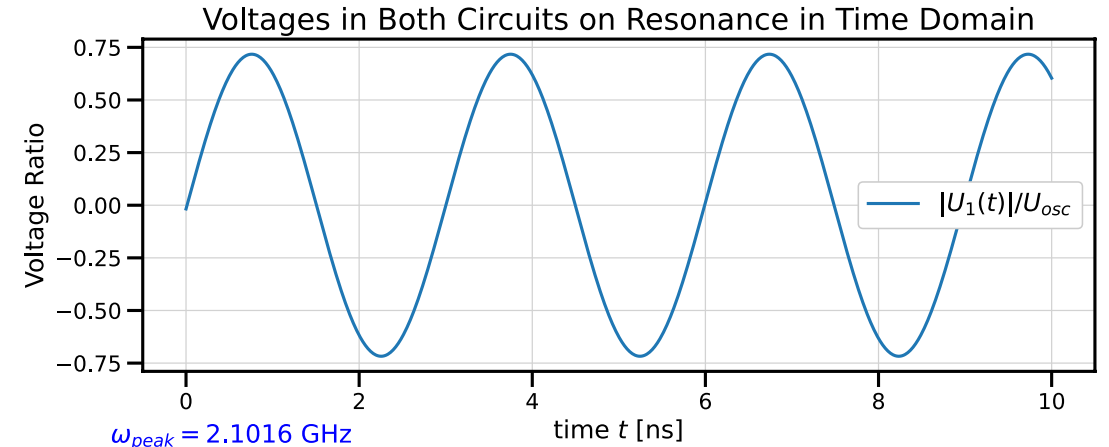


Circuit 2

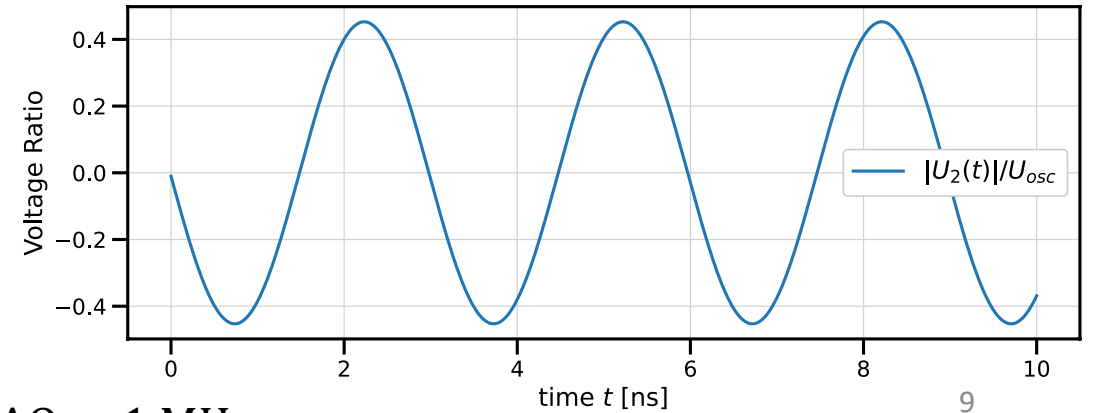

$k = 10^{-2}, \quad \Delta\Omega = 1 \text{ MHz}$

Comparison to Measurement

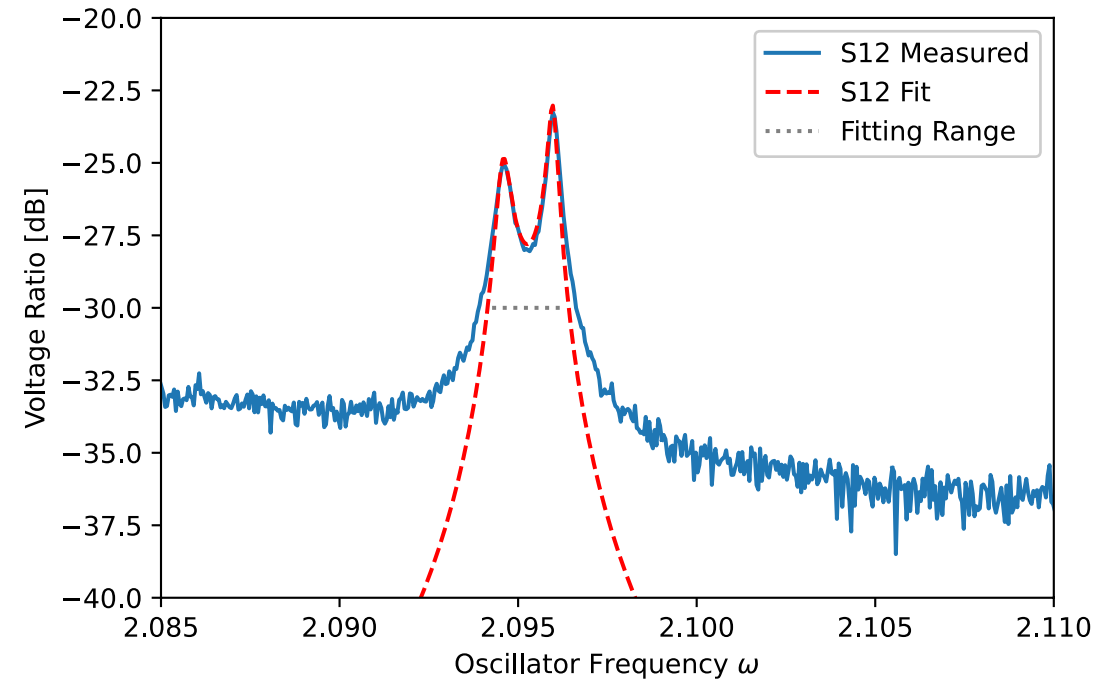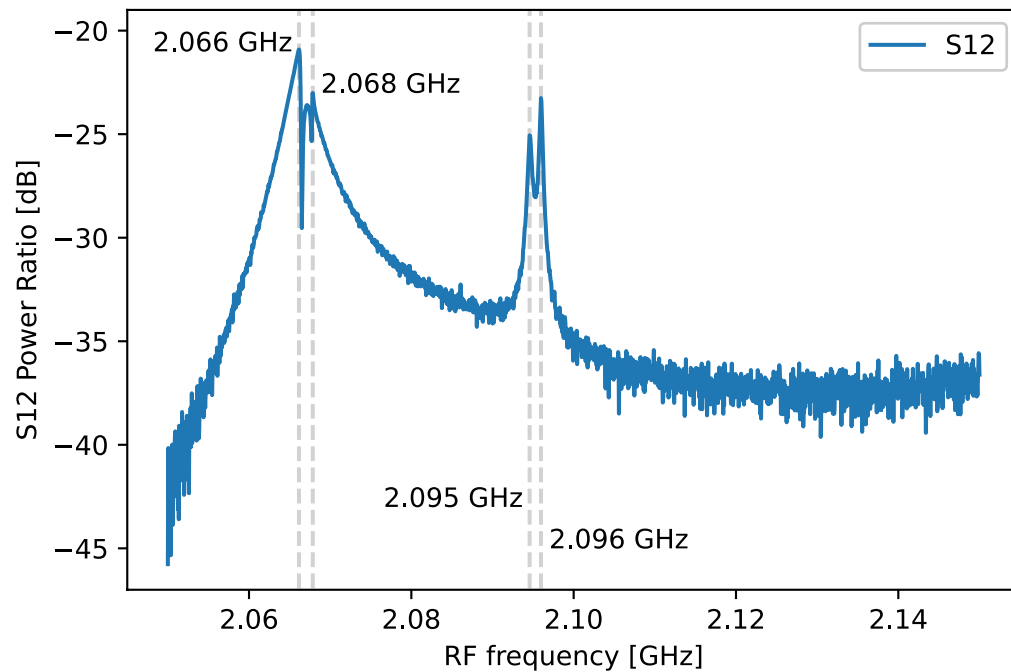


tentative results: (S12 and $|U_2/U_0|$ are not exactly the same)

$$k = 0.5 \cdot 10^{-5}, \quad \Delta\Omega = 1.4 \text{ MHz}, \quad Q_1 = 0.5 \cdot 10^4, \quad Q_2 = 0.8 \cdot 10^4$$

Varying coupling parameter k

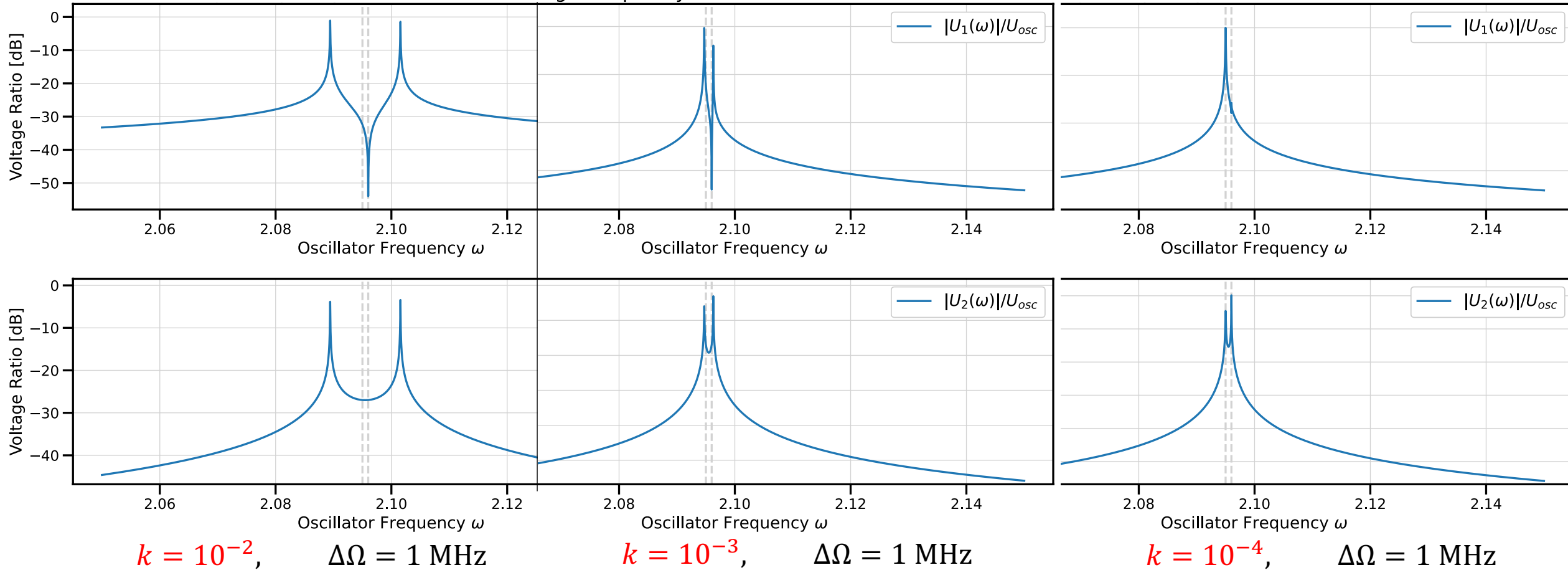Voltage Frequency Distribution in Both Circuits







$Q_1 = 5 \cdot 10^{-4}, \quad Q_2 = 3Q_1$ (leads to different peak sizes)

Effect of bad coupling $k = 10^{-4}$


- No 0 and π modes anymore
- Large Amplitude Difference

Arbitrary Phase Shift

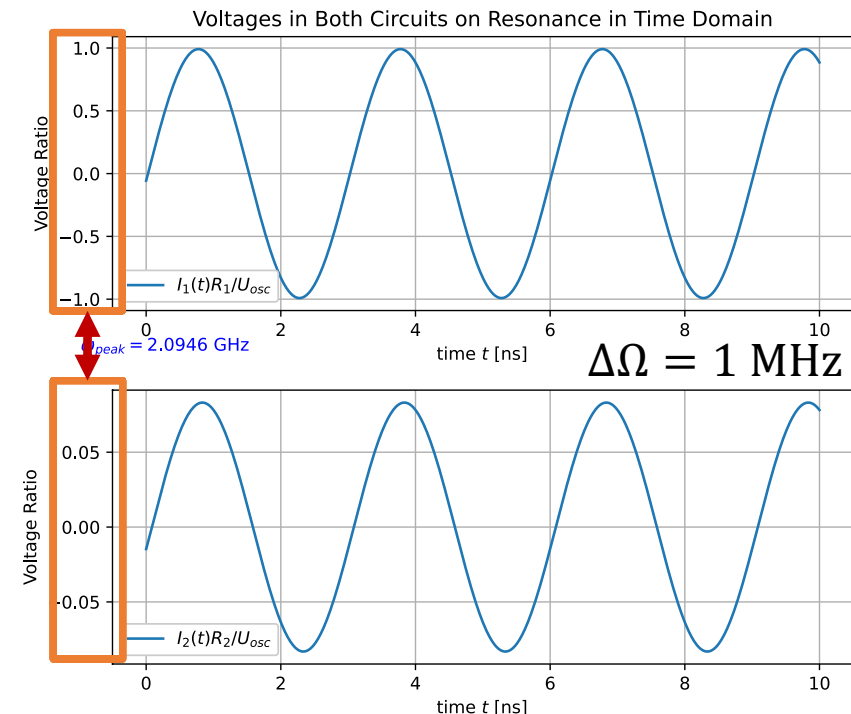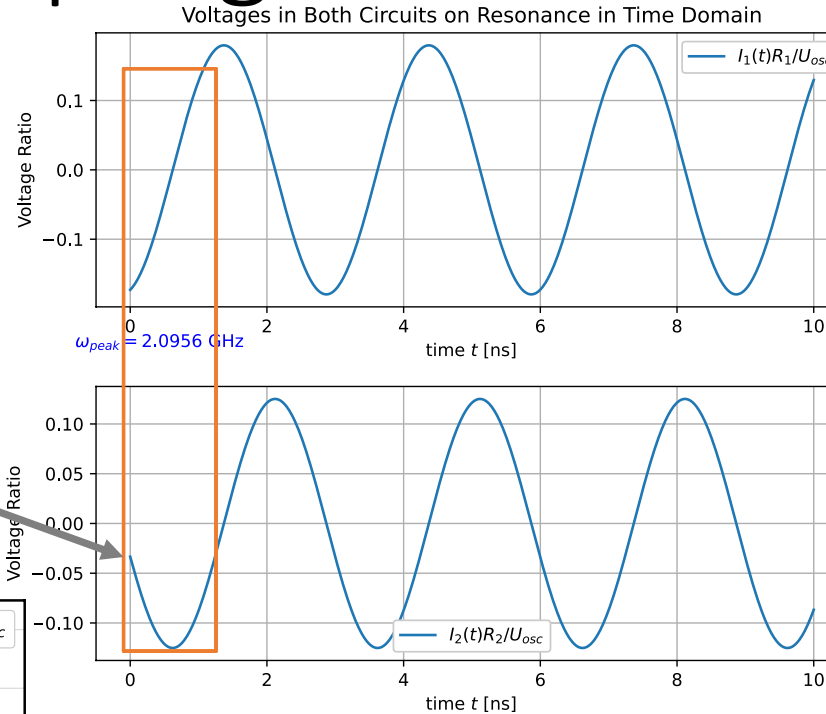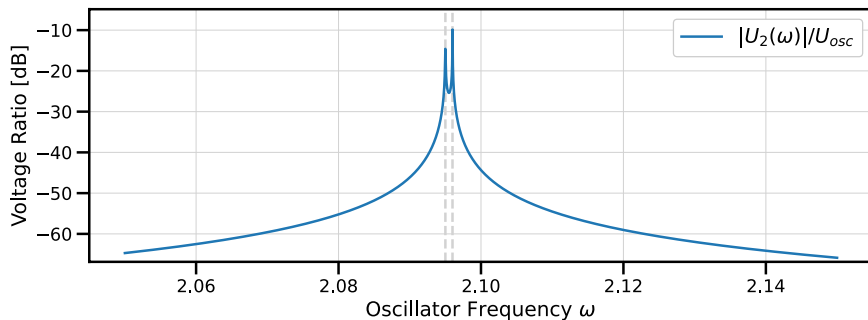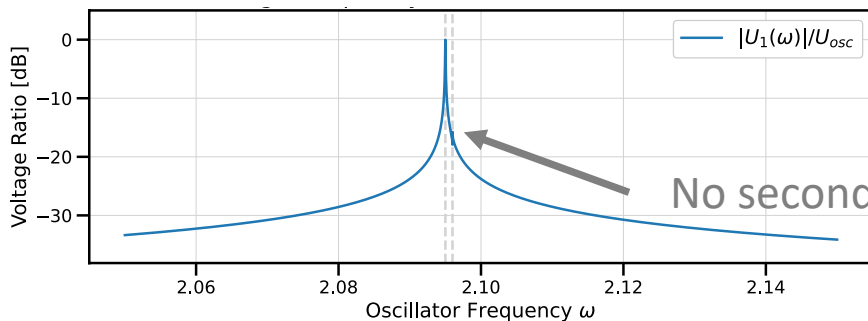


⇒ Problem in Mech-EM-coupling: $C_{01} \propto \int (dS_{cavity} \cdot \xi_{mech}) \cdot (E_0 \cdot E_1)$

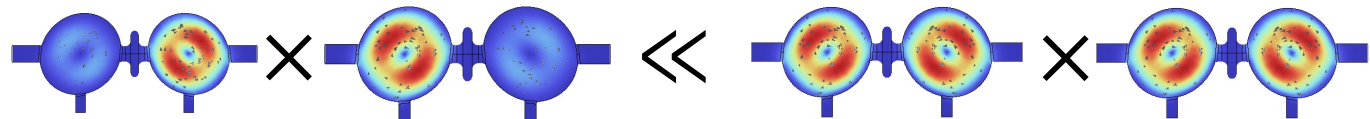- Phase shift of mechanical mode needs to match phase shift of EM-mode
- Low amplitude ratio enters C_{01}





Design Requirements

$$Q_1 = Q_2 = 10^9$$

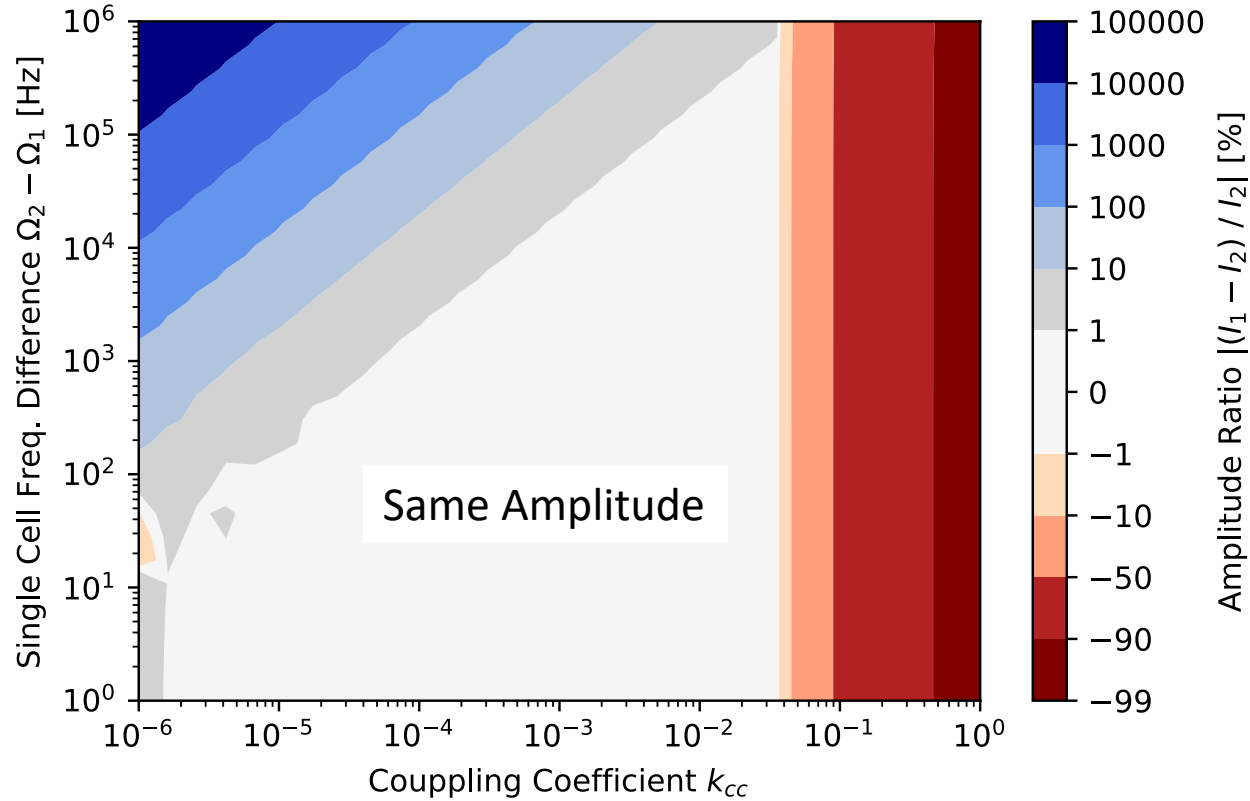

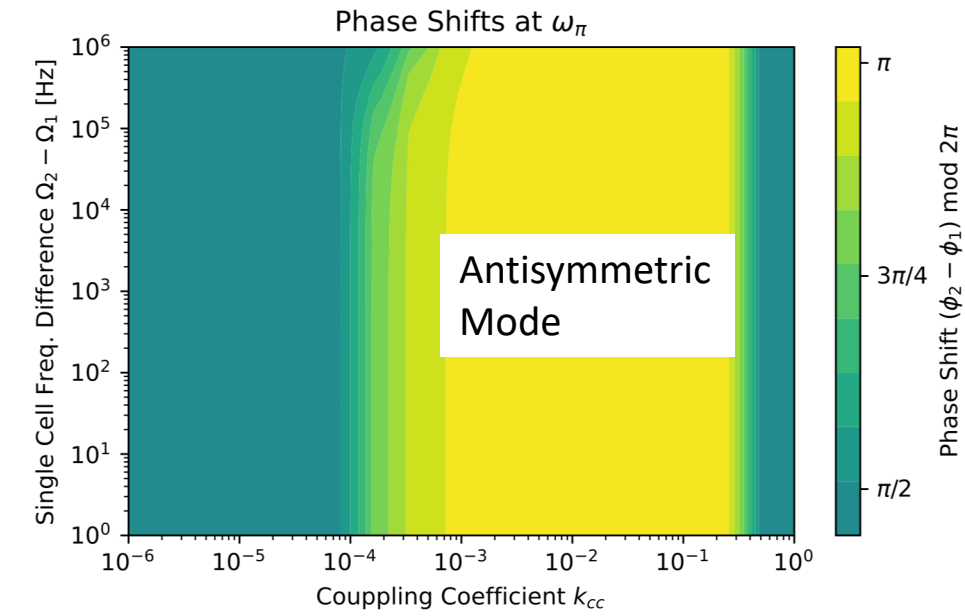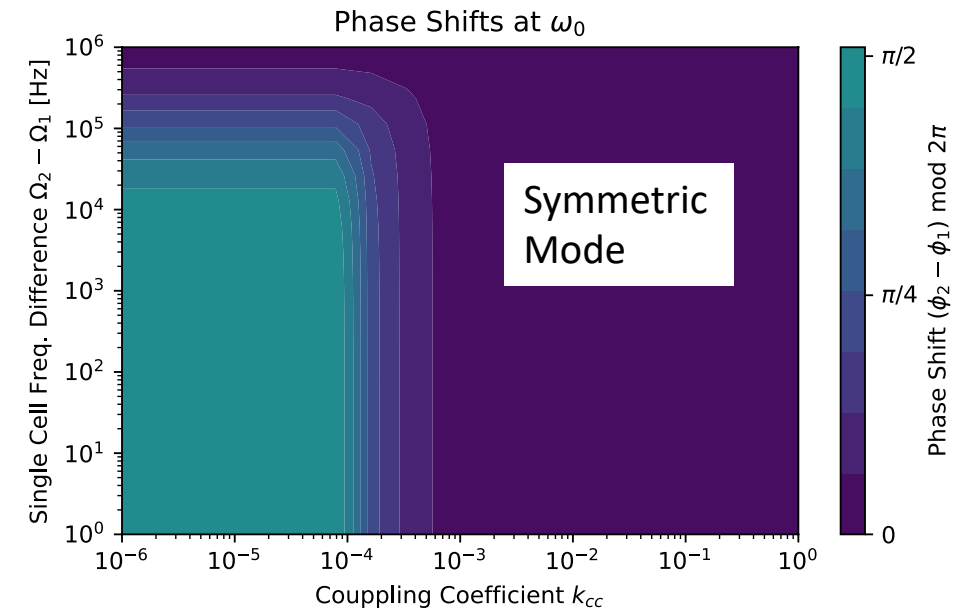- (k, Ω_1, Ω_2) determine GW Frequency ω_g sensitivity through $k(\Omega_2 - \Omega_1) = \omega_\pi - \omega_0 \approx \omega_g$
- k and $\Omega_2 - \Omega_1$ should be chosen to create same Amplitude in both cells
- Q_1, Q_2 need to be $\gg 10^9$ to avoid arbitrary phase shifts



$$Q_1 = Q_2 = 10^4$$

For $Q_1, Q_2 \mapsto 10^{10}$: $\Delta\phi \mapsto 0 / \pi$

Conclusion

- The coupling of the two MAGO cavity cells is likely too bad to form the predicted mode patterns
- We expect the field strength in both cells to differ significantly (confirmed by COMSOL simulation)
 - Reduction of Mech-EM Coupling coefficient
- The predicted symmetric (0) and antisymmetric (π) modes should still appear in the superconducting state

REMAINING QUESTION: Will the MAGO cavity need to be reshaped?