

MAGO2.0 Meeting 15.05.24

Update Accelerometers, S Matrix Formalism

Tom Krokotsch



Vibration Measurement With New Accelerometers

- Accelerometer mounted on cavity
- Cavity struck with hammer
- Nominal sensitivity: 1 - 10 mV / ms⁻²

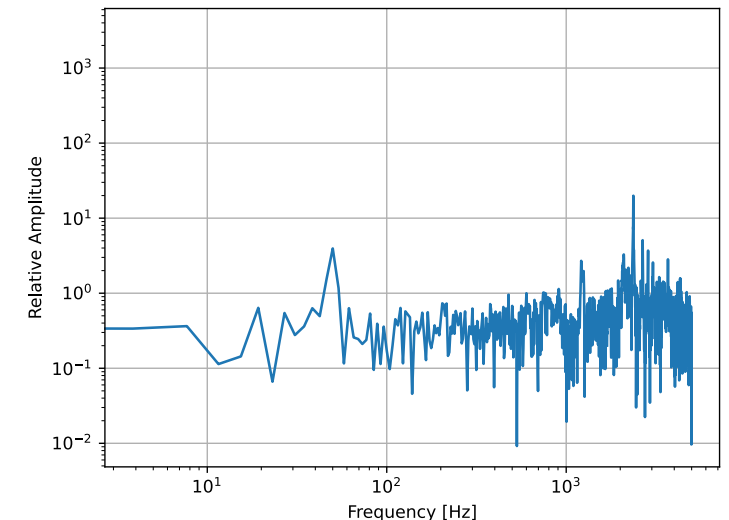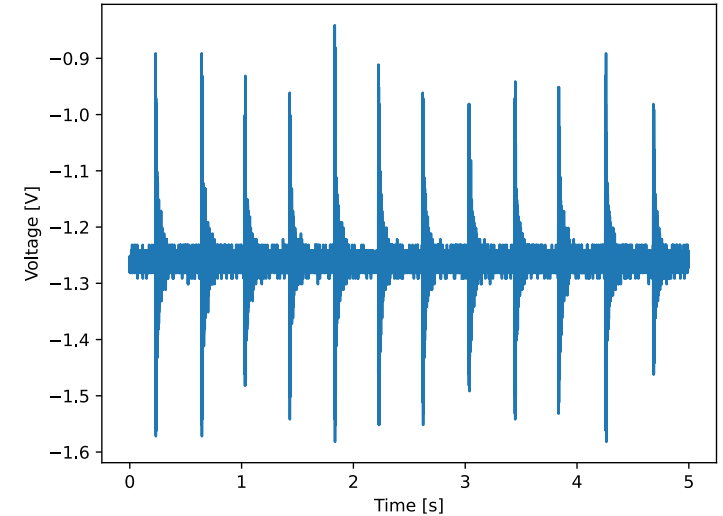Problem:



Noise floor too high. We want to resolve vibrational noise background, not just hammer blows

→ Better power source, amplifier or DAQ may help



Improved Sensitivity

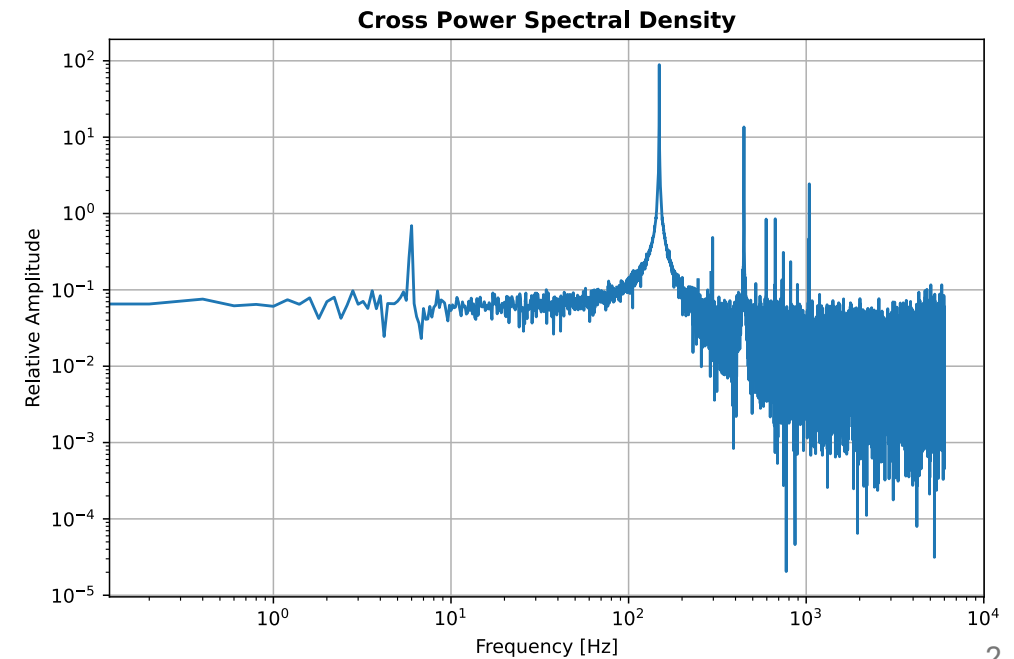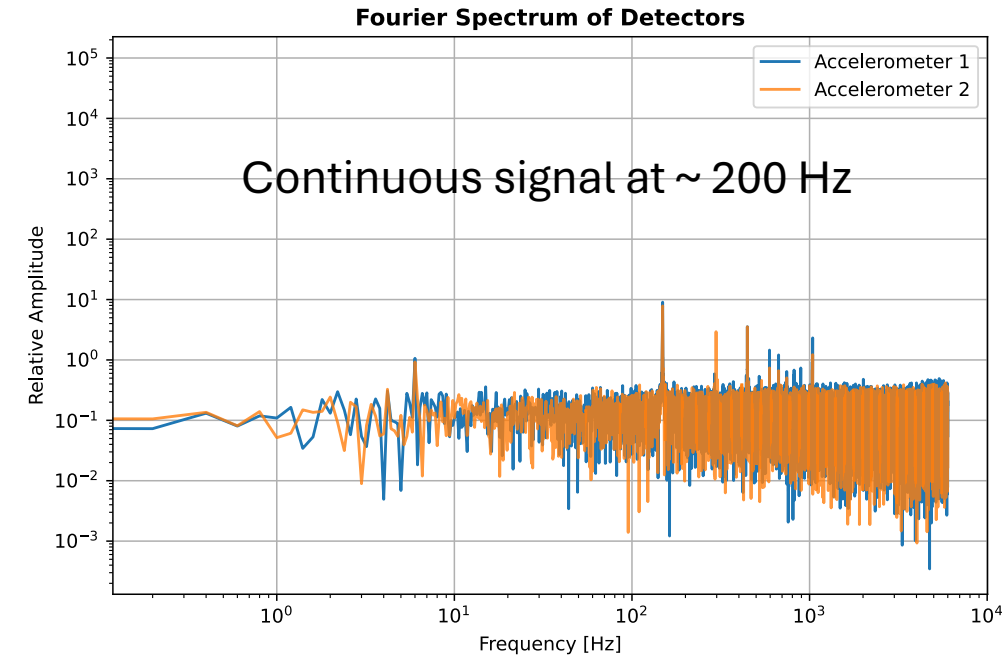- Use internal amplifier in DAQ for better resolution
- Cross correlate two detectors to suppress electronic noise



MAGO Equivalent Circuit

On resonance:

$$\frac{Z_{in}}{Z_c} = \frac{Q_{int}}{Q_e} = \frac{P_e}{P_{int}} \equiv \beta_{in}$$

$$\frac{Z_{out}}{Z_c} = \frac{Q_{int}}{Q_{out}} = \frac{P_t}{P_{int}} \equiv \beta_{out}$$


In steady state: $P_{in} = P_e + P_{int} + P_t$

$$\frac{P_b}{P_f} = \left(\frac{1 + \beta_{out} - \beta_{in}}{1 + \beta_{in} + \beta_{out}} \right)^2, \quad \frac{P_t}{P_f} = \frac{4 \beta_{in} \beta_{out}}{(1 + \beta_{in} + \beta_{out})^2}, \quad \frac{P_{int}}{P_f} = \frac{4 \beta_{in}}{(1 + \beta_{in} + \beta_{out})^2}, \quad \text{Stored energy } U_0 = \frac{4 \beta_{in}}{(1 + \beta_{in} + \beta_{out})^2} \frac{Q_{int}}{\omega_0} P_f$$

No backwards power, maximal stored energy, maximal transmission for $\beta_{in} = \beta_{out} + 1$ (if β_{out} is fixed)


‘critical coupling’ $\frac{P_b}{P_f} = 0, \quad \frac{P_t}{P_f} = \frac{\beta_{out}}{1 + \beta_{out}}, \quad \frac{P_{int}}{P_f} = \frac{1}{1 + \beta_{out}}, \quad \text{Stored energy } U_0 = \frac{1}{1 + \beta_{out}} \frac{Q_{int}}{\omega_0} P_f, \quad Q_L = \frac{1}{1 + \beta_{out}} \frac{Q_{int}}{2}$

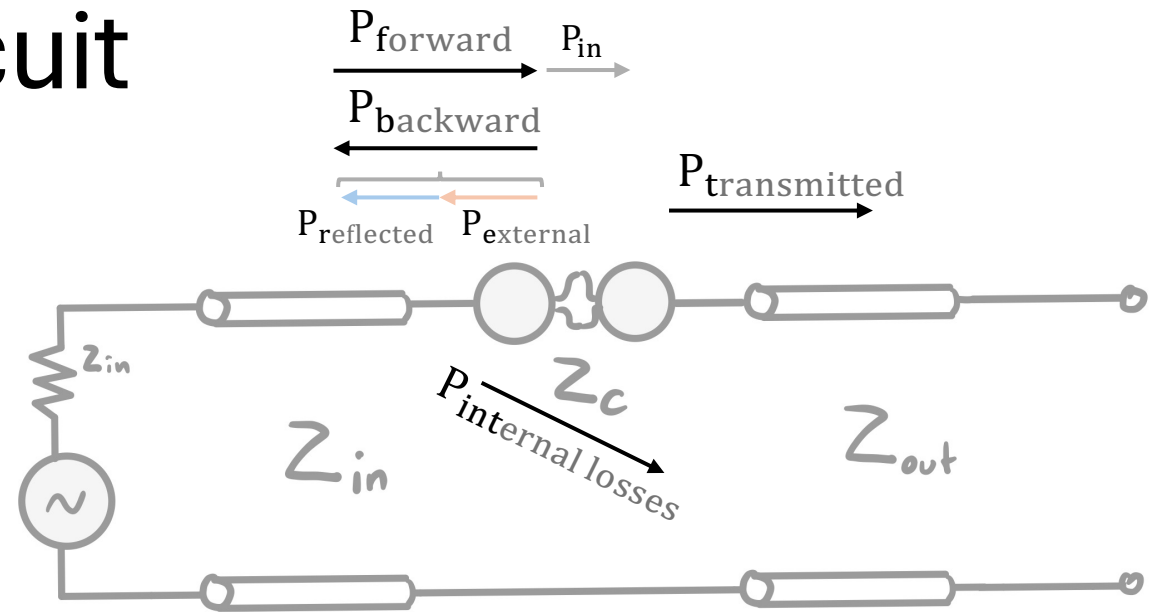$\beta_{in} = 1$ is not really critical coupling anymore!



Taking cavity coupling into account

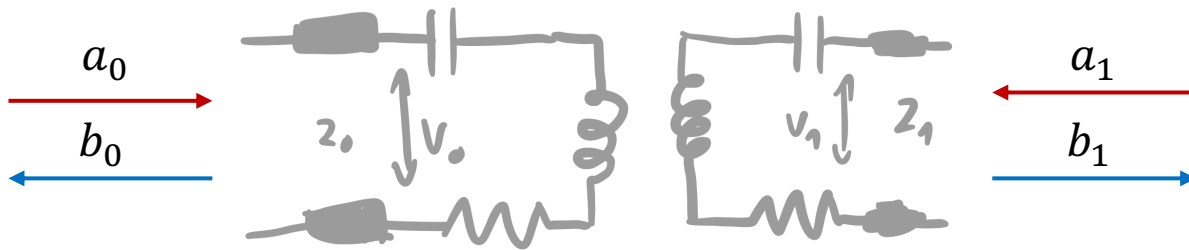Consider forward- (a) and backward- (b) travelling power waves



Impedance of single cavity cell: Z_c
Coupling impedance $Z_{cpl} = i\omega L_{cpl}$


The power relationships can be obtained from the S matrix

$$\begin{pmatrix} b_0 \\ b_1 \end{pmatrix} = S \begin{pmatrix} a_0 \\ a_1 \end{pmatrix}$$

In this case: $S = \frac{1}{(Z_c + Z_1)(Z_c + Z_0) - Z_{cpl}^2} \begin{pmatrix} (Z_c + Z_1)(Z_c - Z_0) - Z_{cpl}^2 & 2\sqrt{Z_0 Z_1} Z_{cpl} \\ 2\sqrt{Z_0 Z_1} Z_{cpl} & (Z_c - Z_1)(Z_c + Z_0) - Z_{cpl}^2 \end{pmatrix}$

If $Z_0 = Z_1$ is chosen, the most transferred power is the value which maximizes S_{21} : $Z_{0,1} = \sqrt{Z_c^2 - Z_{cpl}^2} \approx R_c$ on resonance
 $\Leftrightarrow \beta_{0,1} = 1$ as expected

Four port system

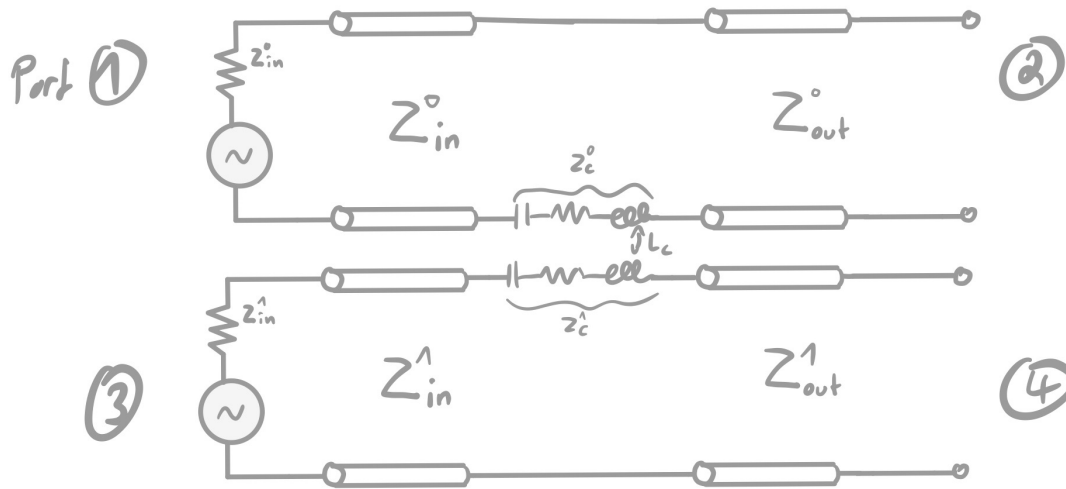


$$S = \frac{1}{Z_{tot}^1 - Z_{cpL}^2} \begin{pmatrix} (Z_{in} + Z_c - Z_{cpL}) Z_{tot}^1 - Z_{cpL}^2 & -2\sqrt{Z_{in} Z_{out}} Z_{tot}^1 & -2 Z_{in} Z_{cpL} & 2\sqrt{Z_{in} Z_{out}} Z_{cpL} \\ -2\sqrt{Z_{in} Z_{out}} Z_{tot}^1 & (-Z_{in} + Z_c + Z_{cpL}) Z_{tot}^1 - Z_{cpL}^2 & 2\sqrt{Z_{in} Z_{out}} Z_{cpL} & -2 Z_{out} Z_{cpL} \\ -2 Z_{in} Z_{cpL} & 2\sqrt{Z_{in} Z_{out}} Z_{cpL} & Z_{tot}^1 (Z_c - Z_{in} + Z_{out}) - Z_{cpL}^2 & -2\sqrt{Z_{in} Z_{out}} Z_{tot}^1 \\ 2\sqrt{Z_{in} Z_{out}} Z_{cpL} & -2 Z_{out} Z_{cpL} & -2\sqrt{Z_{in} Z_{out}} Z_{tot}^1 & Z_{tot}^1 (Z_c + Z_{in} - Z_{out}) - Z_{cpL}^2 \end{pmatrix}$$

for $Z_c^0 = Z_c^1$, $Z_{in}^0 = Z_{in}^1$, $Z_{out}^0 = Z_{out}^1$ and $Z_{tot}^1 = Z_c + Z_{in} + Z_{out}$

Also want to take magic Tees, and reflections at unused ends into account. To find total S matrix, need to consider transfer matrices T.
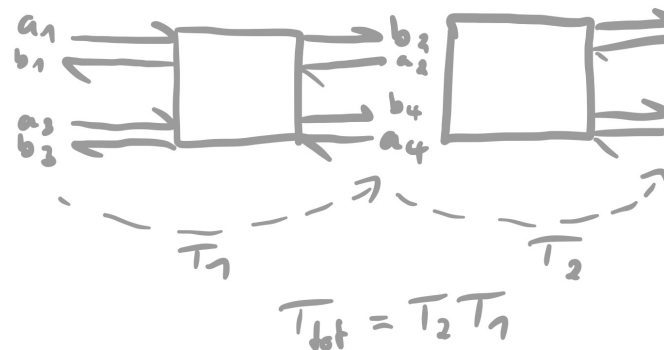
$$\begin{pmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{pmatrix} = S \begin{pmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \end{pmatrix} \text{ vs } \begin{pmatrix} b_2 \\ a_2 \\ b_4 \\ a_4 \end{pmatrix} = T \begin{pmatrix} a_1 \\ b_1 \\ a_3 \\ b_3 \end{pmatrix}$$



Finding the S matrix of cascaded system:

- First, find T matrix of all components
- multiply them
- Convert the total T matrix into a S matrix

Cascaded Network

Basic approach



S Matrix


$$\begin{pmatrix} 1 - \frac{2 Z_{in}}{Z_c - Z_{cpl} + Z_{in} + Z_{out}} & -\frac{2 \sqrt{Z_{in} Z_{out}}}{Z_c + Z_{cpl} + Z_{in} + Z_{out}} & 0 & 0 \\ -\frac{2 \sqrt{Z_{in} Z_{out}}}{Z_c + Z_{cpl} + Z_{in} + Z_{out}} & 1 - \frac{2 Z_{out}}{Z_c - Z_{cpl} + Z_{in} + Z_{out}} & 0 & 0 \\ 0 & 0 & 1 - \frac{2 Z_{in}}{Z_c + Z_{cpl} + Z_{in} + Z_{out}} & -\frac{2 \sqrt{Z_{in} Z_{out}}}{Z_c - Z_{cpl} + Z_{in} + Z_{out}} \\ 0 & 0 & -\frac{2 \sqrt{Z_{in} Z_{out}}}{Z_c - Z_{cpl} + Z_{in} + Z_{out}} & 1 - \frac{2 Z_{out}}{Z_c + Z_{cpl} + Z_{in} + Z_{out}} \end{pmatrix}$$

'Sensitivity enhancement (MAGO)'




$$\begin{pmatrix} 1 - \frac{8 Z_{cpl} Z_{in} (Z_c + Z_{in} + Z_{out})}{(Z_c - Z_{cpl} + Z_{in} + Z_{out}) (Z_c + Z_{cpl} + Z_{in} + Z_{out})^2} & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 + \frac{8 Z_{cpl} Z_{out} (Z_c + Z_{in} + Z_{out})}{(Z_c - Z_{cpl} + Z_{in} + Z_{out})^2 (Z_c + Z_{cpl} + Z_{in} + Z_{out})} \end{pmatrix}$$

Consider GW Signal

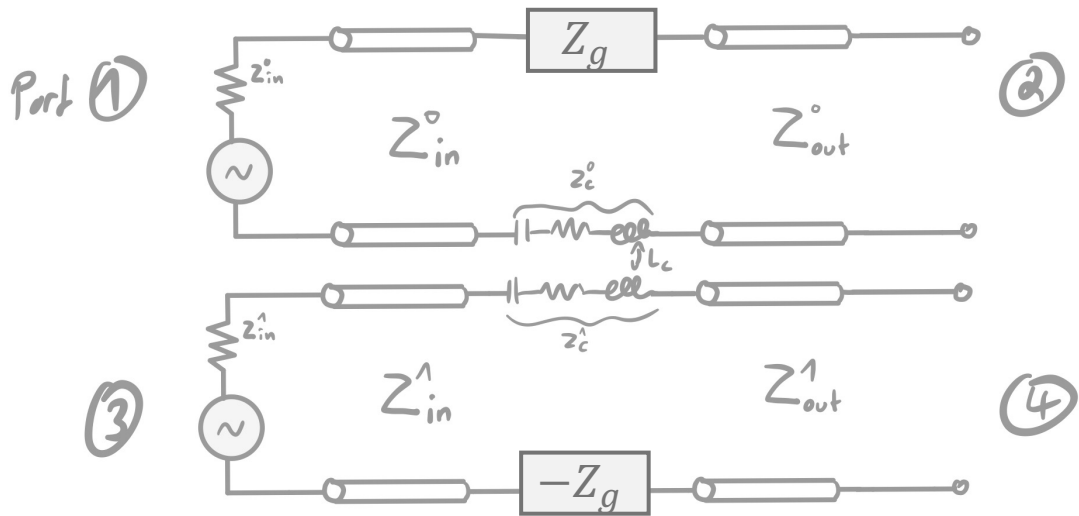

Basic approach $\frac{P_{sig}}{P_f} = 4 Z_g^2 \frac{Z_{in} Z_{out}}{Z_{cpl}^2 - Z_{tot}^2}$

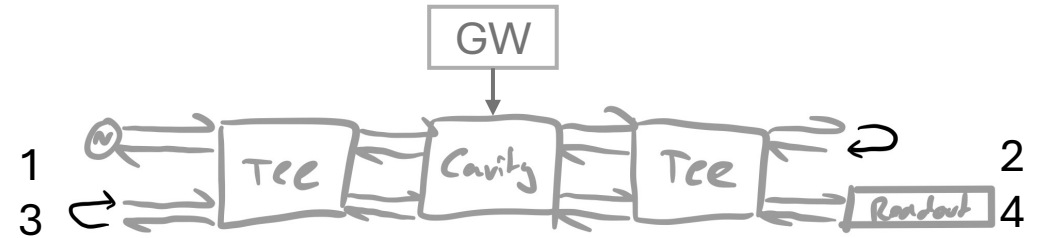‘Sensitivity enhancement (MAGO)’ $\frac{P_{sig}}{P_f} = 64 Z_g^2 \frac{Z_{in} Z_{out} Z_{cpl}^4}{(Z_{cpl}^2 - Z_{tot}^2)^4}$



Add small anti-symmetric excitation through positive and negative impedance in both circuits

$$(Z_{in} + Z_{out} + Z_c)I_1 = -Z_g I_1 - Z_{cpl} I_2 + U_0$$

$$(Z_{in} + Z_{out} + Z_c)I_2 = +Z_g I_2 - Z_{cpl} I_1 + U_0$$

→ Signal strength is proportional to pump energy

→ But at the same frequency as pump mode ($\omega_{GW} = 0$)