



Outline

- Aim
- Existing solution (wired NIM modules)
- Scheme
- Requirements
- Using a V1495 module
- Detailed Proposal
- Current Status



Aim

Gated Counting for separation of

- Beamgas events
- Afterglow events

see talks earlier this day!




BCM1F Beamgas & Albedo Logic - Wired Solution




Existing solution: A crate full of wired NIM modules

Existing solution: A crate full of wired NIM modules

 - lots of shaky switches
- bunches of cables
- ...



Logics Scheme

 

... and more requests to come (?)



BCM1F Beamgas & Albedo Logic - Requirements



Requirements:

2 **BPTX** inputs

8 **BCM1F** inputs

4 outputs - **Albedo** Scalers

8...32 outputs - **Beamgas** Scalers

8 **Gates** (8ns ... 50ns, 960ns)

21 **Delays** (11ns ... 202ns)

Solution with V1495:

Why?


- NIM and ECL I/O provided
- VME interface
- ease of programming

How?

- custom designed mezzanine
- 8 chips per board
- choice between gate or delay
- fully programmable

 Problems:

- bidirectional interface to FPGA
- 25MHz f_{max} (chip specs)




3 basic blocks:

Beam Gas


BPTX1

Albedo

plus one wide gate
utilizing a counter

 

Distribution among 2 modules:

 



2 types of mezzanines

2 types of delay chips (255ns, 65ns)

ECL outputs to scalers, LVDS links between modules

Prototyping mezzanine

  - test bidirectional ports to FPGA
- test serial protocol for setting delay/gate width
- test frequency limit
- test calibration





BCM1F Beamgas & Albedo Logic - Status



Serial Protocol

- registers for 8 chips and state machine implemented in FPGA
- readback to be tested

Bidirectional I/O and 3.3V interface


- under development

Timing Tests

- due

8-chip version

- design started

 



BCM1F Beamgas & Albedo Logic



Thank you for the attention!

Special thanks for challenging ideas and thorough discussions go to
David Stickland.