



AGH UNIVERSITY OF SCIENCE AND TECHNOLOGY

#### Readout electronics for LumiCal detector Present status and new developments

**Krzysztof Świentek** AGH-UST on behalf of FCAL Collaboration

Faculty of Physics and Applied Computer Science AGH University of Science and Technology

ECFA Detector Panel Meeting 10 June 2013, DESY in Hamburg, Germany



#### **Agenda**

- Present readout system for LumiCal and BeamCal detectors
  - Front-end electronics
  - 10b multichannel ADC
  - Detector module
- New ASIC developments for BeamCal
- New ASIC developments for LumiCal
- Conclusions




#### Present readout system for LumiCal and BeamCal detectors

- Front-end electronics
- 10b multichannel ADC
- Detector module
- New ASIC developments for BeamCal
- New ASIC developments for LumiCal
- Conclusions


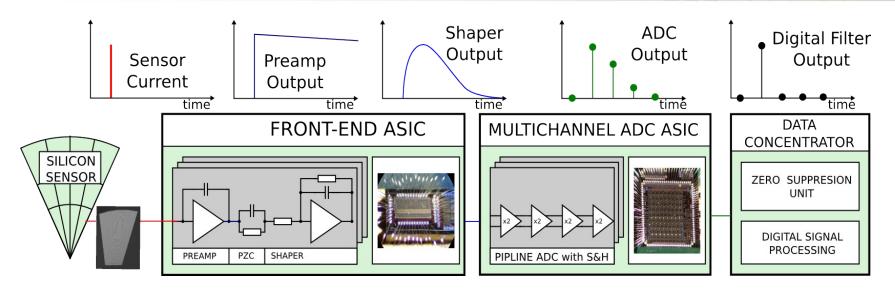
#### LumiCal (BeamCal) detector readout chain





## **Components of LumiCal detector readout** (used also for BeamCal):

- 8 channel front-end ASIC with preamp & CR-RC shaper Tpeak~60ns,
   ~9mW (AMS 0.35um)
- 8 channel pipeline ADC ASIC, Tsmp<=25MS/s,  $\sim$ 1.2mW/MHz (AMS 0.35um)
- FPGA based data concentrator and further readout



#### Front-end Electronics in AMS 0.35um

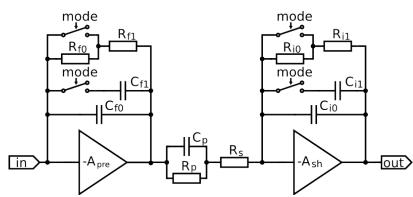

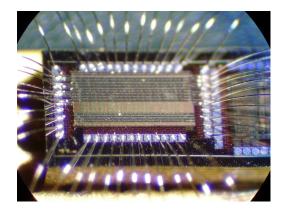


#### **Existing prototypes:**

- 8 channels in AMS 0.35um
- Cdet ≈ 0 ÷ 100pF (in new specs: Cdet<50pF)
- 1st order shaper (Tpeak ≈ 60 ns)
- Variable gain:
  - calibration mode MIP sensitivity (~4fC)
  - physics mode input charge up to 10 pC
- Prototypes fabricated and tested

-0.05

power consumption 8.9 mW/channel

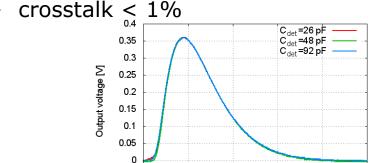

100

200

time [ns]


400


500

M. Idzik, Sz. Kulis, D. Przyborowski, "Development of front-end electronics for the luminosity detector at ILC", NIM A 608 p.169-174, 2009





#### Front-end ASIC measurement results

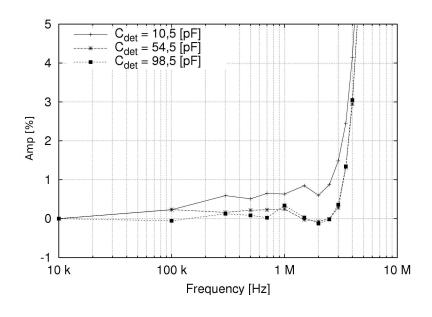

 

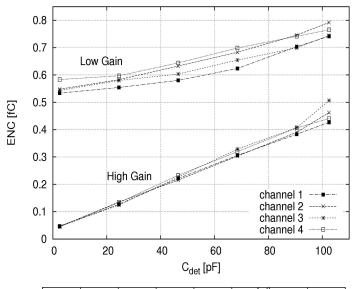- In physics mode the ENC is about
   0.6 fC and in calibration ~0.2 fC
- Linear range up to ~25 fC (calibration) and ~10 pC (physics)




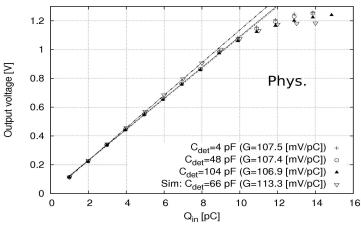



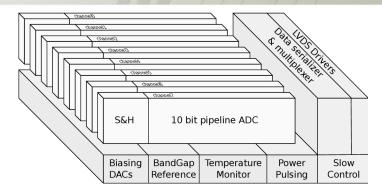
## Multichannel digitizer in AMS 0.35um architecture

- 8 channels of 10-bit pipeline fully differential ADC
- Technology AMS 0.35um
- Layout with 200um ADC pitch
- Multimode digital multiplexer/serializer:
  - Full serialization mode: one data link per all channels
  - Partial serialization mode: one data link per channel
  - Test mode: single channel output
- High speed LVDS interface (~1GHz)
- Power pulsing
- Low power DACs for internal settings
- BandGap reference source
- Temperature sensor




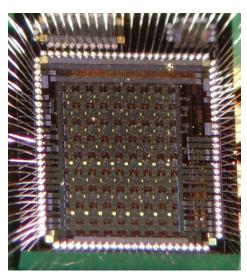

2.6mm x 3.2mm



#### **Pipeline ADC architecture**

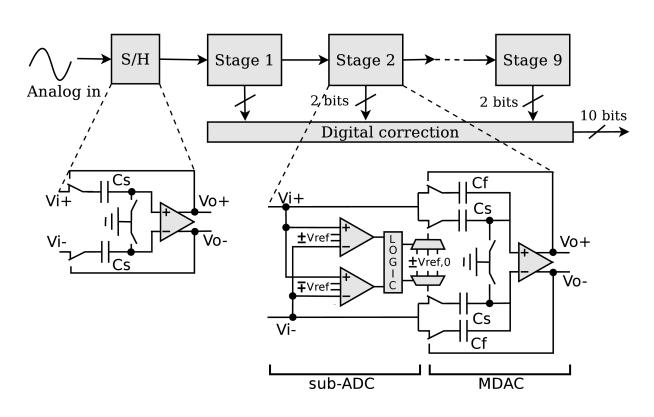


- 9 almost identical stages – capacitance scaling
- Stage 1.5 bit architecture with digital correction – comparator requirements relaxed
- BootstrappedS/H switches



#### **Multichannel ADC ASIC readout**
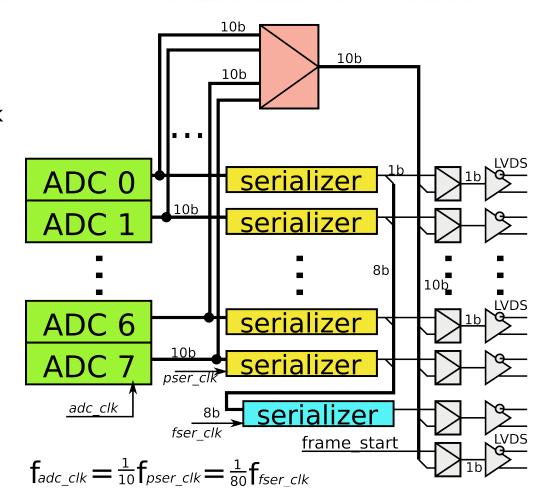
#### Three operation modes:

- Full serialization: one data link per all channels
  - up to ~250 MHz readout
  - up to ~3 Msps
- Partial serialization: one data link per channel
  - up to ~250 MHz readout
  - up to ~25 Msps
- **Test**: single channel output
  - up to ∼50 Msps





0

-1

-0.75

-0.5

-0.25

0

ADC Output Code [LSB]

0.25

0.5


0.75

#### **Multichannel ADC - Static measurements**

Transfer curves for 8 ADC channels (left)
•Good uniformity of offset and gain


1024 896 768 c7 640 q0:496.74 00:504.77 512 g1:496.66 01:507.45 02:507.63 g2:497.15 384 q3:497.07 03:505.86 g4:495.94 04:510.66 256 g5:496.51 05:504.78 q6:496.96 06:510.45 128 g7:497.04 07:510.15 INL and DNL measured for ASIC at 25MS/s:


- INL < 0.7 LSB
- DNL < 0.6 LSB

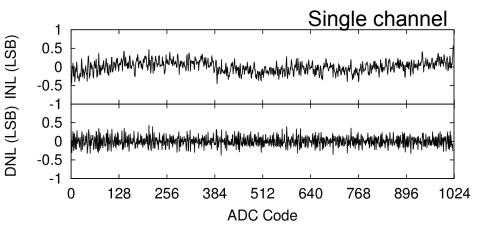


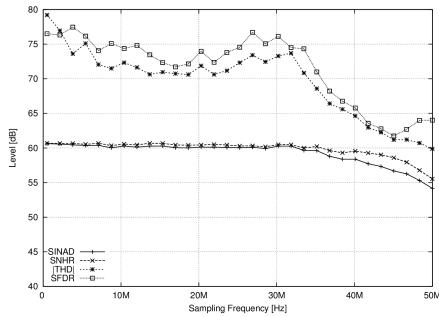
#### **Multichannel ADC - Dynamic measurements**




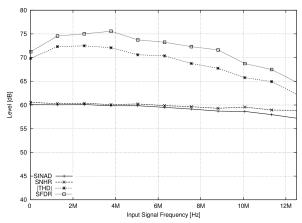

- Dynamic parameters vs sampling frequency (top) and vs input frequency (bottom)
- SINAD ~60 dB corresponding to ENOB ~ 9.7 bits for sampling rates below 35 MS/s
- In test mode ADC works up to ~50 MS/s but in multichannel system two practical configurations are:
  - serialization/channel up to ~25 MS/s
  - serialization/chip up to ~3 MS/s


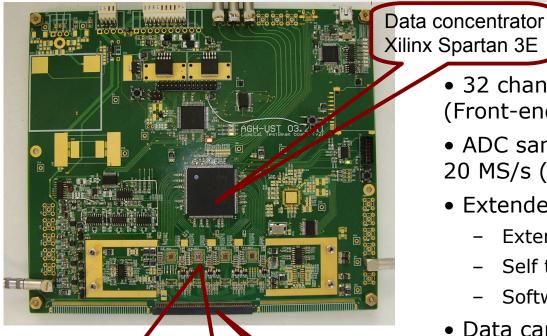
#### 32 channels readout module Final readout based on AMS 0.35um ASICs



Xilinx Spartan 3E

- 32 channels fully equipped channels (Front-end +ADC)
- ADC sampling rate is up to 20 MS/s (6.4 Gbps)
- Extended trigger mechanism
  - External CMOS / LVDS
  - Self triggering on ADC values
  - Software
- Data can be transferred using USB
- ADC Clock source
  - Internal (asynchronous with beam operation)
  - External (beam clock usec for synchronization) ILC mode





sensor connector



# LumiCal detector readout module (ASICs in AMS 0.35um)



4 pairs of Front-end + ADC

- LumiCal detector module with 32 fully equipped channels (Front-end +ADC ASICs) plus FPGA data concentrator is regularly used during testbeams
- Good performance of detector module verified on 2 testbeams in 2011
- Power pulsing: 1ms ON then
   199ms OFF ASICs Power
   ON/OFF >30
- Using deconvolution, tests for CLIC are performed with asynchronous readout


Sensor (IFJ PAN)



# Readout module is used for BeamCal and LumiCal detectors



LumiCal in testbeam 2011

 




- Present readout system for LumiCal and BeamCal detectors
  - Front-end electronics
  - 10b multichannel ADC
  - Detector module
- New ASIC developments for BeamCal
- New ASIC developments for LumiCal
- Conclusions



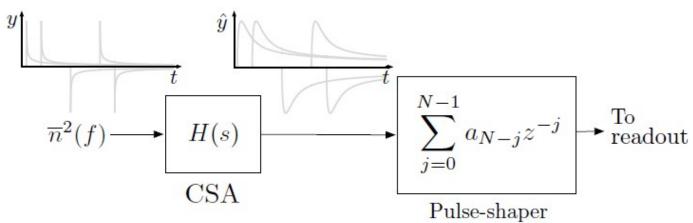
#### Noise analysis and optimization in front-end

- Aims to understand and test how different weights in multiple sampling affects signal-tonoise ratio
- and therefore, how to optimize the weights
- Switched capacitor implementation is being designed






#### **BeamCal SAR ADC architecture**

 

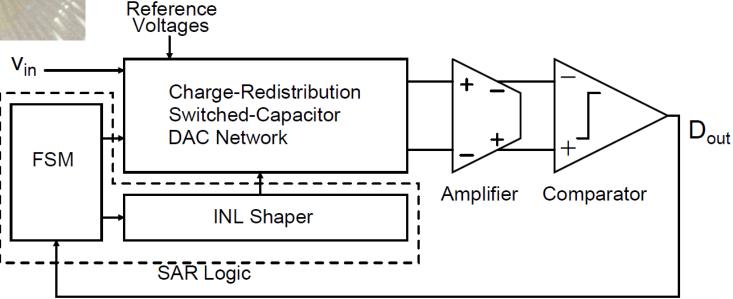
- ADC uses systematic process mismatch (radial gradients in array) to correct nonlinearity
- Test structures already produced





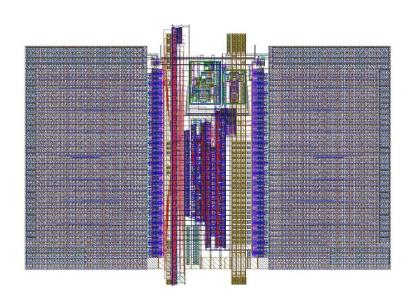
#### **SAR ADC linearity correction**

- Recently tested in a 180 nm process
- INL can be shaped to correct nonlinearity of signal path



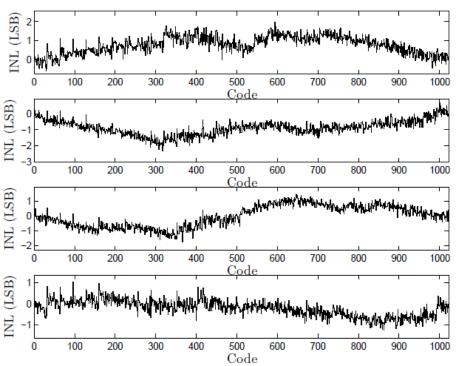





- Present readout system for LumiCal and BeamCal detectors
  - Front-end electronics
  - 10b multichannel ADC
  - Detector module
- New ASIC developments for BeamCal
- New ASIC developments for LumiCal
- Conclusions



#### Front-end: Preamplifier & Shaper

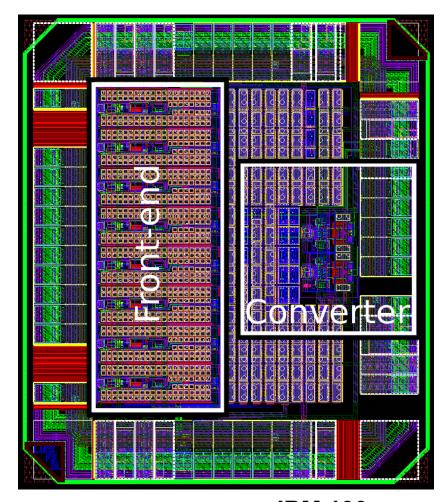

**IBM 130 nm** 

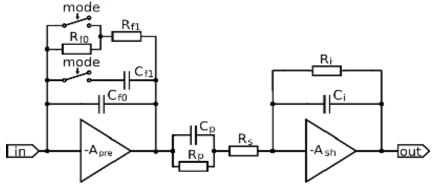

#### **Design specs:**

- 8 channels
- Cdet  $\approx 5 \div 50pF$
- 1st order shaper (Tpeak ≈ 50 ns)
- Variable gain:
  - calibration mode MIP sensitivity
  - physics mode input charge up to ~6 pC
- Power pulsing implemented
- Simulated power consumption ~1.5 mW/channel 20




#### **Design of 10-bit SAR ADC**

#### **Designs of 10-bit ADC**


- Architecture: SAR ADC with segmented/split DAC
- Sampling frequency up to ~50 MS/s
- Power consumption scales with sampling frequency
- Asynchronous SAR logic no fast clock

SAR channel 600um x 146um

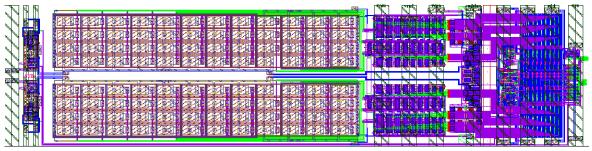

**IBM 130 nm** 

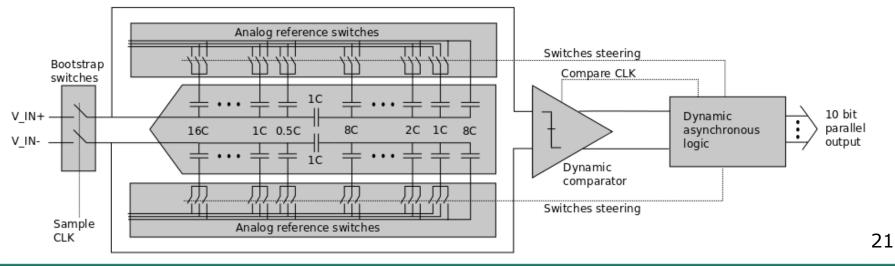- 1-2 mW at 40 MS/s
- 146um pitch
- Fabricated in 2012 (2 prototypes)





#### Layout of 8 channel 10-bit SAR ADC

#### IBM 130 nm

# DIGITAL

2200um x 2000um


#### **ASIC** comprising

- 8 channels of 10-bit SAR ADC
- PLL for data serialization
  - Systematic tests are just starting
- PLL output clock signal was observed with scope
- High speed SLVS interface
  - No dedicated tests of SLVS interface done yet
- PLL differential outputs it was veryfied that SLVS driver operates at least up to 700 MHz.

Design submitted and fabricated in 2012



 
#### 10-bit SAR ADC - Static measurements



- ADC works in the whole input signal range
- There are some codes with worse linearity (under investigation...)


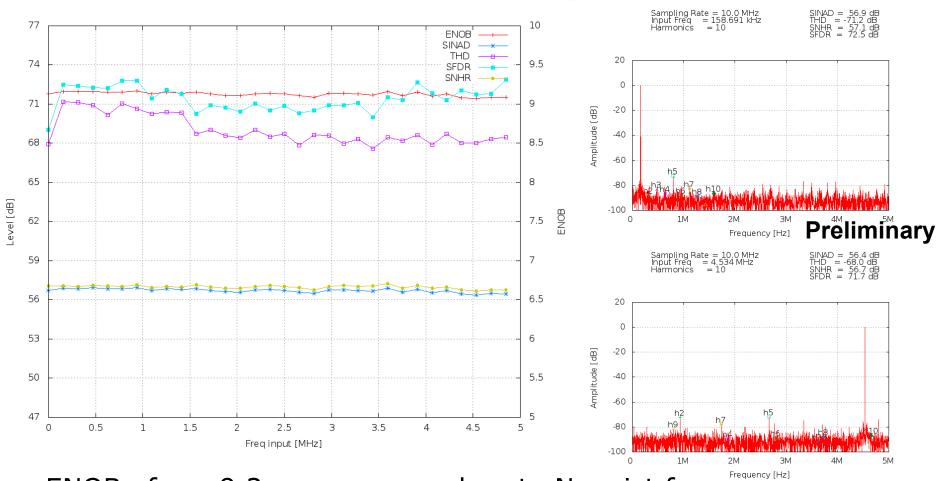
#### 10-bit SAR ADC - Dynamic measurements



• ENOB of >= 9.2 was measured up to Nyquist frequency after improving test setup – more improvement needed?



#### **Summary and Plans**


- Presently FCAL uses in test-beams the readout modules based on developed at AGH-UST ASICs in CMOS AMS 0.35um
- Development of new ASICs for BeamCal readout in 180 nm in progress – next front-end submission planned at the end of 2013
- Development of new ASICs for LumiCal readout in IBM 130 nm in progress:
  - First prototype of front-end electronics submitted and should be available in June 2013
  - First prototypes of 10-bit SAR ADC, PLL, SLVS already produced and presently under test:
    - 10-bit SAR ADC: first results show its functionality, the effective resolution slightly less than simulated quantitative measurements in progress..
    - PLL tests just started...
    - SLVS interface works well
  - Depending on test progress and results we plan next submission at the turn of 2013/2014



### **Backup slides**


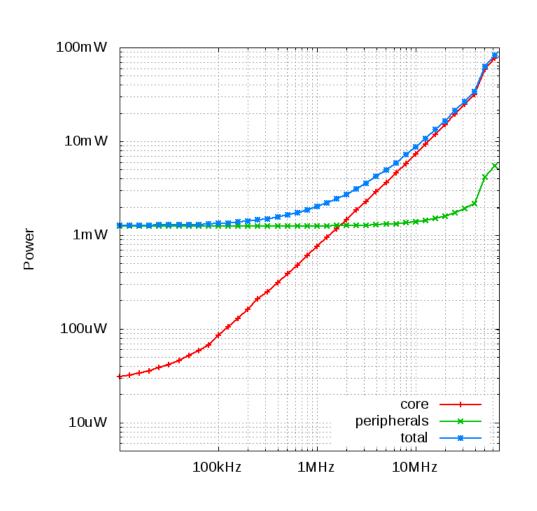
#### Developments in AMS CMOS 0.35um Power consumption in pipeline ADC




- Power scales lineary in frequency range 3 kHz – 10 MHz:
  - ADC (core) –0.8 mW/channel/MHz
  - serializer in partialserialization mode –0.35 mW/channel/MHz
  - serializer in fullserialization mode –0.85 mW/channel/MHz


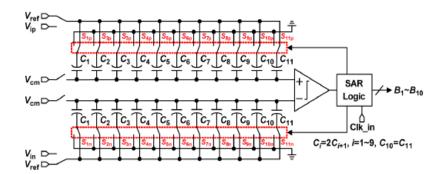
# Developments in IBM CMOS 130nm SAR ADC: General features & design considerations


- Power and area-efficient architecture
- the same circuitry is used N-times (for N-bit ADC) to approximate the input voltage
- Only one comparator, two DACs and SAR logic needed – fits well to modern digital CMOS
- Limited sampling rates but with modern CMOS technology (~100nm) up to ~100MSps 10-bit ADCs were reported
  - next conversion cannot be started before completion of previous one
  - sampling time adds to conversion time (not like in pipeline)



- Comparator the only analog block
- DAC network serves as sampling capacitance
- Simple digital logic
- Fully differential implementation increases the resistance to disturbances


 
#### <u>Preliminary measurements</u> 10-bit SAR ADC - Dynamic measurements different channels




- Results for different channels (only one channel ON during measurements) are similar
- $\bullet$  It was suspected that ENOB decrease with  $f_{in}$  is partially/mainly due to setup



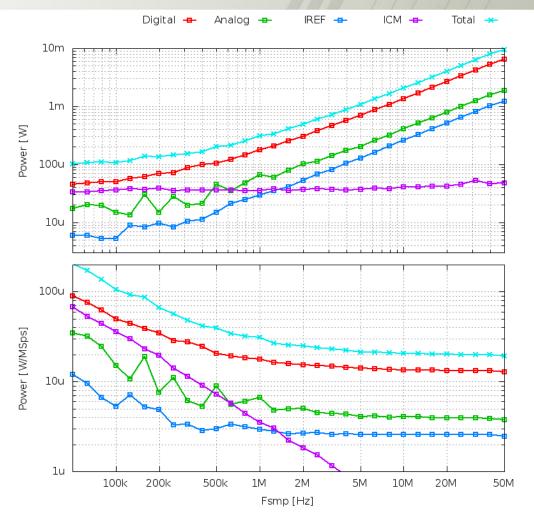
# Preliminary measurements 10-bit SAR ADC - Power consumption vs sampling frequency

- Power measured for 8 ADC channels
- At 40MS/s power consumption is about 1 mW per channel in agreement with simulations





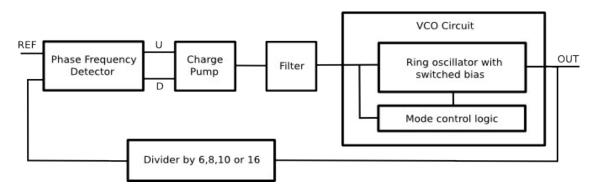
# **Developments in IBM CMOS 130nm Design of PLL for data serialization**


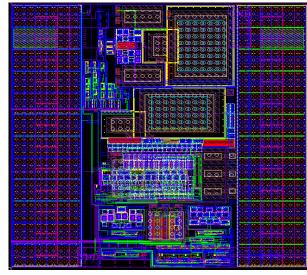
#### **Design specs:**

- Architecture: type II PLL with 2<sup>nd</sup> order filter
- Scalable frequency & power
- Automatically switched VCO freq. range
- VCO frequency range 8MHz 3GHz,
- VCO frequency division by 6, 8, 10 or 16
- Power consumption <2mW at 3GHz
- Submitted and fabricated in 2012, the tests have just started...




300 x 300 um



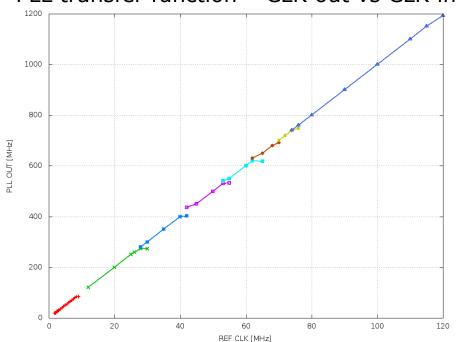
#### <u>Preliminary measurements</u> PLL – Transfer function, power consumption





#### Power consumption measurements

 


- PLL measurements have just started (~ 2 days) and are in progress...
- PLL output CLK in frequency range 15MHz-1.2GHz already observed
- There are some gaps between frequency ranges...
- Automatic mode detection looks promising
- SLVS driver works at least up to 1.2 GHz (used for PLL output)



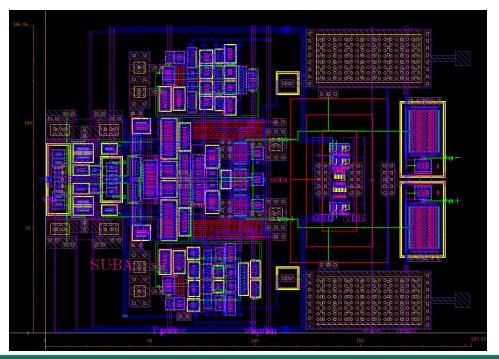
#### <u>Developments in IBM CMOS 130nm</u> Single Ended-to-Differential converter

Single Ended to Differential converter (in front-end ASIC)

- Dynamic input range ~600 mV
- Differential output range ~1.2V
- Maximum frequency ~ 50 MHz




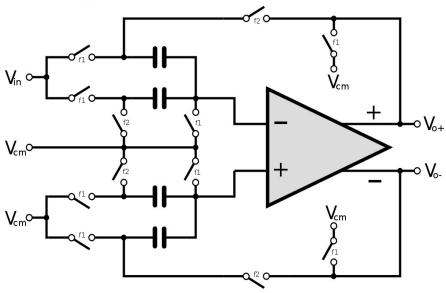

Design submitted February 2013



#### Old BeamCal readout ASIC

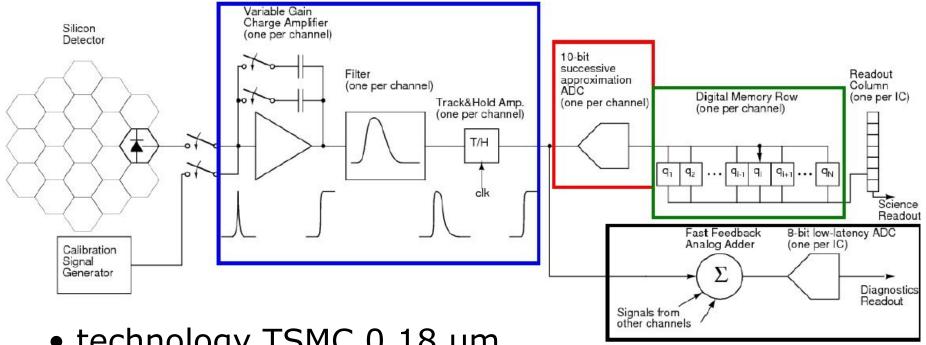

- technology TSMC 0.18 um
- 32 channels
- memory: 2820 words (10 bits + parity) per channel
- analog addition of 32 channels for fast feedback



#### **Pair monitor**

- First readout ASIC
  - CMOS process: 0.25 μm TSMC
- Chip size : 4 x 4 mm<sup>2</sup>, **6 x 6** pixels (36)
- Test setup based on KEK-VME 6U module was prepared
- Sensor needs to be bound bonded
- Silicon On Insulator (SOI) technology first readout prototype
  - The sensor and readout electronics are integrated in the SOI substrate. (monolithic)
  - **SOI 0.2 μm** CMOS process
  - Chip size: 2.5 x 2.5 mm², 3 x 3 pixels (9) (only readout)
  - The noise level (260 e<sup>-</sup>+130 e<sup>-</sup>/pF) is much smaller than typical signal level (20000 e<sup>-</sup>)
  - All the ASIC components work correctly.

