

# SPADIC – Self-triggered charge pulse processing ASIC

Tim Armbruster, Peter Fischer, *Michael Krieger*, Ivan Peric

ZITI, Universität Heidelberg

`michael.krieger@ziti.uni-heidelberg.de`

TPC Workshop, Bonn


28.02.2013

# Introduction


- Self-triggered Pulse Amplification and Digitization ASiC
- main application: TRD subsystem of CBM (FAIR/GSI)



# Concept


 


# Channel overview

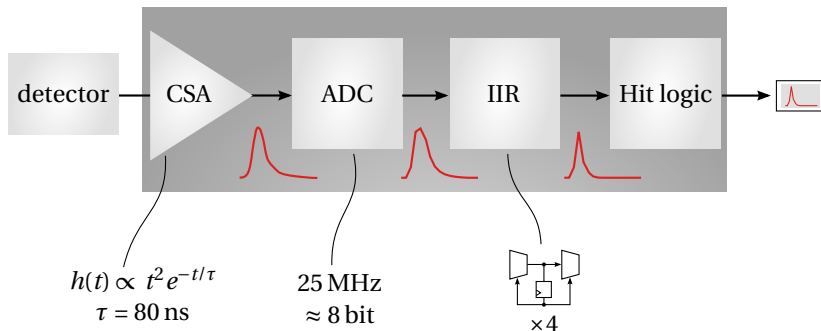



# Charge amplifier

  


two amplifiers per channel selectable:

- input range: 75 fC
- shaping time: 80 ns
- noise: 800  $e^-$  @ 30 pF
- positive polarity (4 mW)
- negative polarity (10 mW, not optimized)


layout & schematics: modular, scalable

## ADC

 


- current mode pipelined design
- 25 MHz sample rate, continuously running
- 9 bit nominal output
- resolution  $\approx 8$  bits
- 4.8 mW, rad-hard layout,  $400 \times 300 \mu\text{m}^2$

# IIR Filter

 

 - 16 bit internal resolution
- 6 bit coefficients
- freely programmable ( $\frac{-32, \dots, 31}{32}$ )
- instability excluded



# IIR Filter

purpose: “tail cancellation”

shorten pulses → reduce pileup/help hit logic



- model signal as sum of exponential terms:

$$x_n \propto \sum w_i q_i^n$$


- recursion:  $y_n = x_n + b x_{n-1} + a y_{n-1}$

- each filter stage shifts relative weights:


$$w'_i = \frac{q_i + b}{q_i - a} w_i$$

  


# IIR filter: examples (simulation)

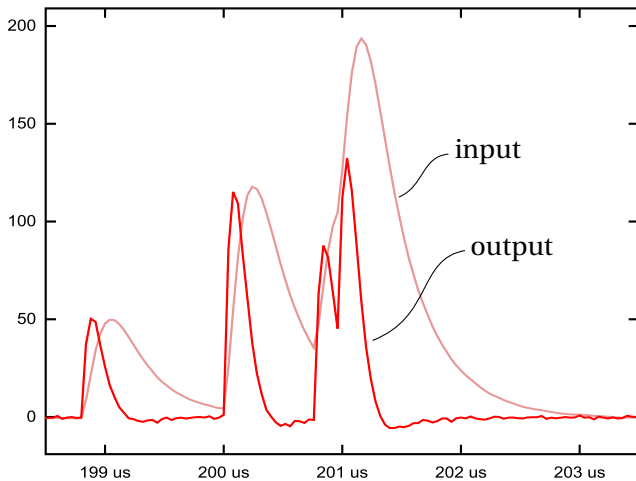


# IIR filter: examples (simulation)

 

# Hit logic

 


# Message format

 


- every word has a preamble (4 or 1 bit)
- easy recovery of message stream



# Message output multiplexing

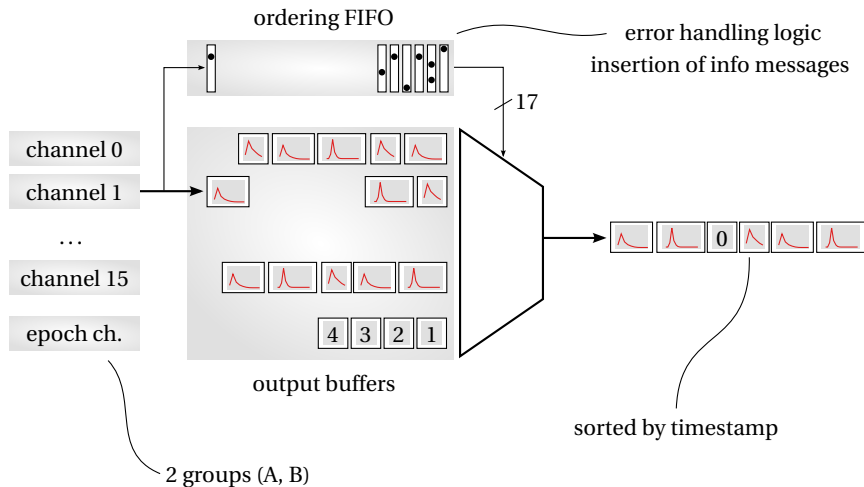


# DAQ interface (CBMnet)

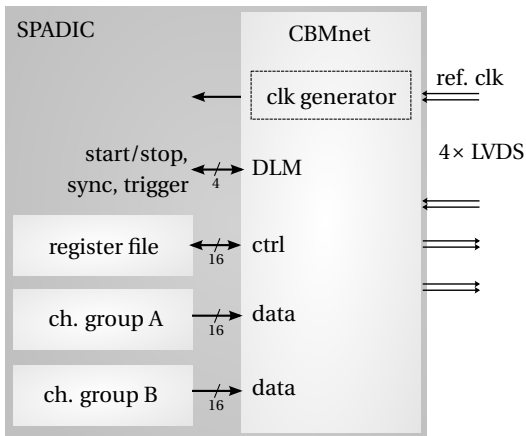


- error checking, retransmission
- *deterministic latency messages (DLM)*
- different traffic classes share single serial link
- 500 Mbit/s (DDR), 8b/10b encoded, LVDS (1 input, 2 outputs)

# Layout view

 


- UMC 180 nm
- overall size:  $5 \times 5 \text{ mm}^2$
- digital part:
  - $3.5 \times 4.5 \text{ mm}^2$
  - home-made standard cell library
  - 2.5 million transistors, 23k FF, 81k gates
  - 44 Faraday SRAMs
  - total wire length: 14.4 m
  - Power (200 MHz): 600 mW

# Test setup

 

 
# First results

ADC curve: taken at 20 MHz sample rate, preliminary bias settings



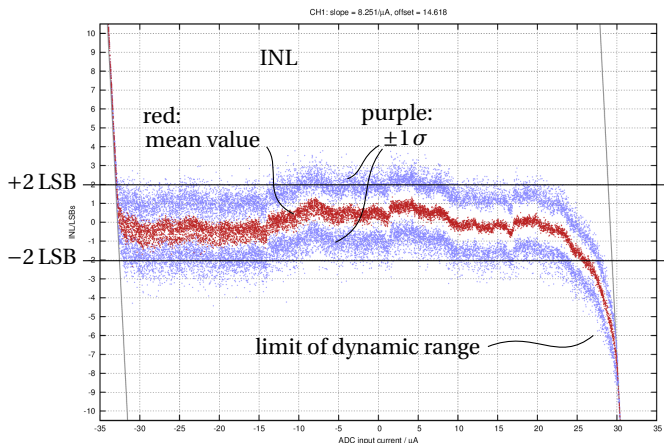
# First results

ADC curve: taken at 20 MHz sample rate, preliminary bias settings



# First results

measured pulses (20 MHz sample rate)

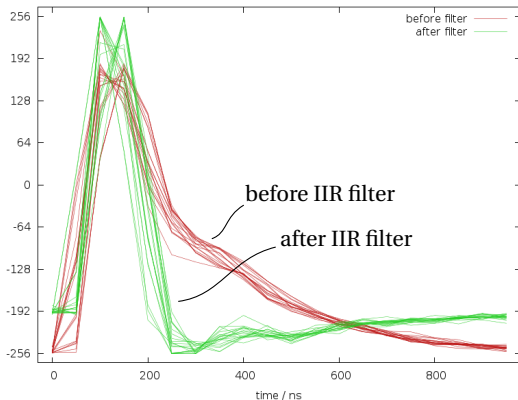


CSA → ADC → IIR Filter → hit logic → message building ✓

# First results

CBM beamtime October 2012 @ CERN: first time CBMnet readout

TRD prototype

 



# Development status & lookout


- shown measurements done using auxiliary readout (bypassing CBMnet, limited capabilities)
- no major bugs discovered, everything so far tested works
- lab setup not yet CBMnet compatible → in progress
- full characterization (CSA, ADC) to be done, optimal settings to be found

# Summary
 
## SPADIC

complete system for charge pulse readout

- 32 channels
- self-triggered recording of whole pulse shapes (programmable selection mask)
- neighbor trigger, global trigger
- flexible digital signal processing
- time-sorted output message stream with notification of error conditions
- CBMnet: built-in DAQ connection with reliable data transmission and synchronization features using 4 LVDS pairs



# SPADIC

Self triggered Pulse Amplification and Digitization asIC

<http://spadic.uni-hd.de>