

#### Status and Future of the Transient Recorder Chip

#### **Development of the HitDetection ASIC @ GSI**

Bonn – 28.02.2013 Peter Wieczorek, GSI

FAIR






- FAIR @ GSI
- Motivation for the HitDetection ASIC
- ASIC Architecture
- Crucial Design Points
- First Results
- Summary and Outlook




### **FAIR Facility**

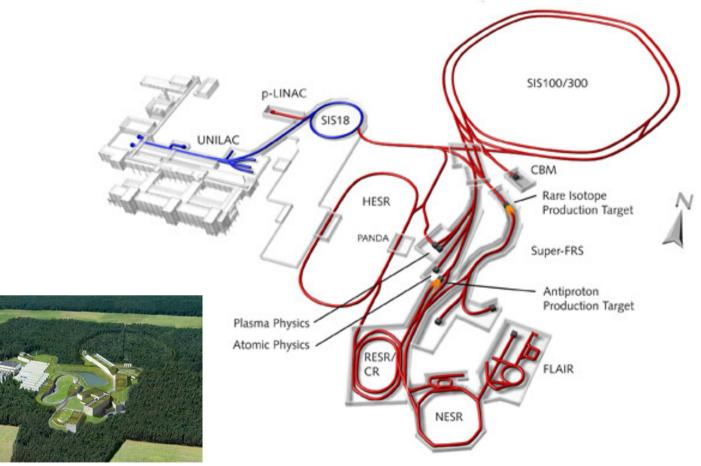

**Projected Facility** 

— 6 5 ľ

#### **PANDA Experiment**

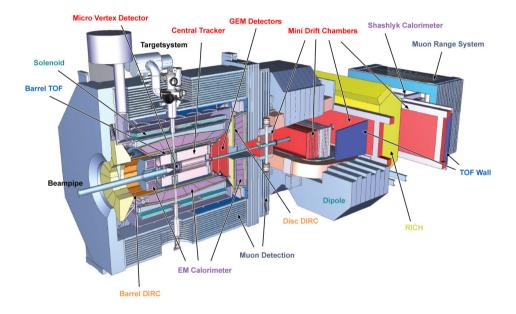


- Several sub detector systems in a very compact design
- PANDA experiment: Trigger – less data taking
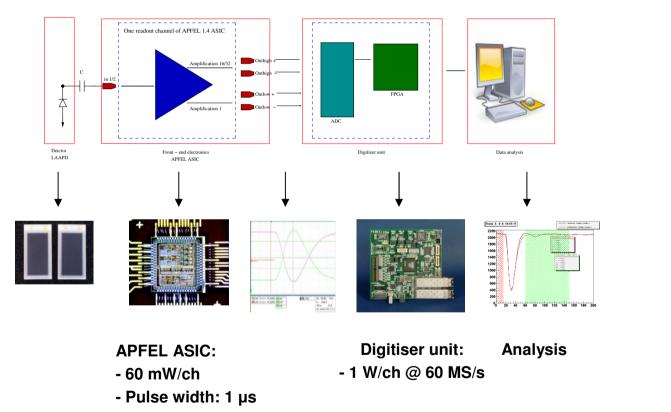
#### **PANDA EMC:** Þ

- 11000 lead tungstate crystals
- Event rate up to 300 kHz/per crystal
- Operation temperature  $T = -25 \ ^{\circ}C$







- Readout chain
  - Detector
  - Front end electronics
  - Digitiser unit
  - Analysis




#### **Motivation**

- Concept of HitDetection ASIC by Igor Konorov
- Multi purpose transient recorder ASIC
- Less external components
  - Higher reliability (limited access to sub detector volume)
  - Lower power consumption (100 mW/ch?)
  - Lower number of supply voltages (1 or 2)
  - Cost reduction

Radiation tolerance

SEUs in FPGA configuration SRAM

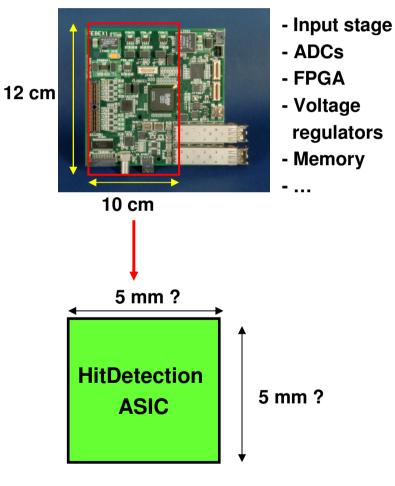


# **Features of the HitDetection ASIC**

- Self triggered transient recorder
- Configurable sampling rate (Detector specific configurable)
- Analogue signal storage and derandomisation
- ► On chip ADC
- ► Time stamping




# **Block Schematic HitDetection ASIC**

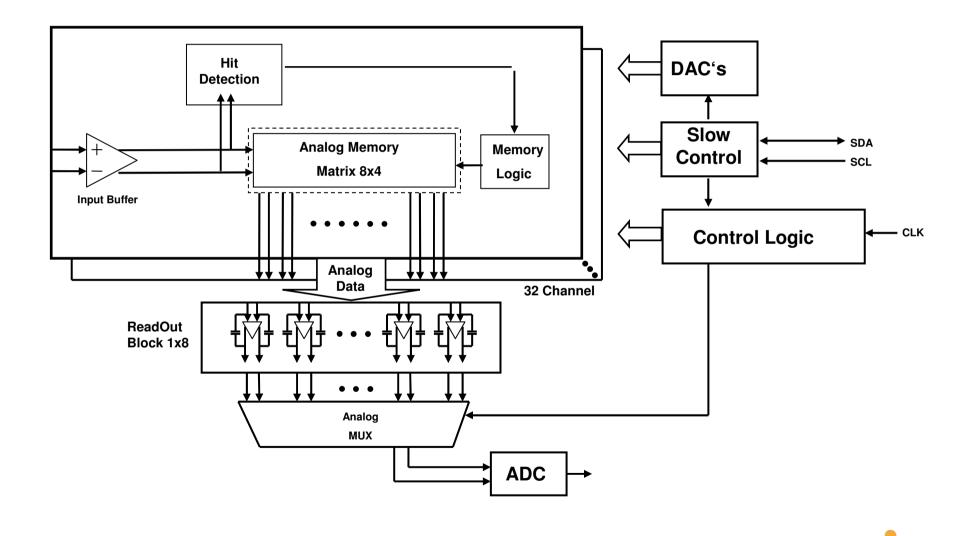

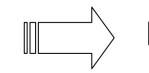
#### **HitDetection ASIC Integration Level**

- Number of input pads (differential = 2 pads/channel)
  - Proposal 32 channels:
    - Pad pitch <u>140 μm</u> chip width: 4500 μm + 500 μm ( max. chip size 5000 μm (MPW run))
  - Proposal 64 channels:
    - Pad pitch <u>100 μm</u>
       chip width: 6400 μm + 500 μm
    - Pad pitch <u>80 μm</u> chip width: 5120 μm + 500 μm
- Space limitation from block size (analogue memory differential)
  - MIM cap option @ 1 pF: Cell size : 20 μm x 100 μm
  - Channel width 4 x 20 μm + routing: <u>100 μm</u>
- Data rate assuming 200 kHz/channel, 8 samples/event, 12 bit ADC, 20 bit timestamp
  - ▶ 32 channels: 3.2 mm; Data rate: 768 Mbit/s
  - 64 channels: 6.4 mm; Data rate: 1.54 Gbit/s
- Which integration level is reasonable for the detector?



#### Final: 32 channel solution

### **Block Schematic HitDetMEM 1.0**

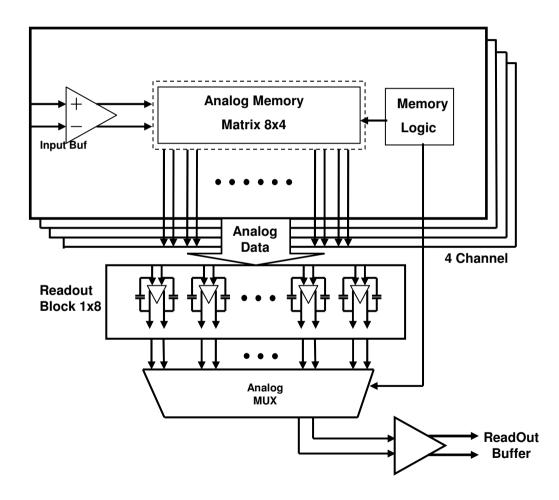


- HitDetMEM 1.0 includes:
  - Differential input buffer
  - External trigger for readout
  - Analogue memory with
     MIM cap option
  - Differential integrator
  - Analogue multiplexer
- UMC 180 nm CMOS
- Chip size:

 $3240~\mu m$  x  $1525~\mu m$ 
 
## **Differential Input Stage**


- **Requirements for the input stage:** 
  - Fully differential operation
  - Input DC range: 0 3 V Þ
  - Pulse heights: about ± 1 V  $\triangleright$
  - Output Vcm fix at 0.9 V Þ
  - High linearity and slew rate (SR: 2 V / 5 ns)
  - Low noise / low power consumption



Test different input stage based on a folded cascode architecture




# **Channel Memory Matrix 8x4**

 

Parallel readout

 
#### **Analogue Signal Storage and Derandomisation**

- Capacitor array used as analogue memory
- Analogue memory is divided into blocks with configurable size
- Signals from input receiver are sampled and stored at the position of write pointer
- Write pointer circles inside of one block


 
#### **Analogue Signal Storage and Derandomisation**


- Signals from particle energy deposits are detected by the hit detection unit
- Write pointer switches to the next memory block
- Signal transient is stored in previous block
- Analogue readout when shared ADC is available
- Block is available again for signal storage


 
## **Differential Integrator**


Requirements for the integrator stage:


- Fully differential operation
- Input DC range: 0 1.5 V
- Pulse heights: about ± 1 V
- High linearity and slew rate
- Low noise and low power



- Use a fast integrator architecture without CMFB:
  - Differential input (n mos)
  - Auto zero circuit
  - Output buffer
 
#### Functional Tests on HitDetMEM 1.0 (1)




 


1 Differential input buffer	=>	works
2 Analog MIM- cap memory	=>	works
Out 3 Differential integrator	=>	works
4 Analogue multiplexer	=>	works
5 Output buffer	=>	works



# Functional Test of HitDetMEM 1.0 (2)

 

#### **Results: HitDetMEM 1.0**

 

- Input stage: to slow for our application
- Memory cell: reach the range: ± 1 V Þ
- Sampling frequency: up to 100 MHz
- Integrator stage: fulfill the design requirements



#### HitDetMEM 1.0 vs HitDetMEM 2.0

- HitDetMEM 1.0:
  - Input stage (rail to rail design):
    - Works in the expected range
    - <u>But</u>: to slow for our application
  - Memory cell:
    - Reach the expected range of ± 1 V
  - Integrator:
    - Works as expected
  - Multiplexer:
    - Not connected to power
    - <u>But</u>: function test was possible

- HitDetMEM 2.0:
  - Input stage:
    - 4 new different input stage concepts are implemented
  - Memory cell:
    - Same as in preversion
  - Integrator:
    - Same as in preversion
  - Multiplexer:
    - Same multiplexer with power connection

#### Status HitDetMEM 2.0: Delivered at GSI end of January

G



- Measurements of the first HitDetMEM 1.0 ASIC are finished
- ► A 2<sup>nd</sup> test ASIC HitDetMEM 2.0 was submitted with several test structures
- Preliminary results of second submission are expected in march 2013



#### Outlook

- Hit Detection unit (Filter)
  - In the proposal of Igor Konorov: FIR filter (Fine Impulse Respond)
    - A continuous level, discrete time filter
  - FIR filter should be able to detect hits in a pile up situation
  - Open question:
    - FIR filter necessary?
    - Which order of this filter?
    - A free configurable filter coefficient or fixed one?
- Slow control and control logic
- ADC development
  - 12 bit
  - ADC speed?
- First full HitDetection ASIC submission (maybe 2013/2014)