FPGAs for ps Timing

Michael Traxler, GS

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

FPGAs for ps Timing Why Time measurements, Why to use FPGAs, FPGAs as TDC in running experiments

Michael Traxler, GSI

2019-03-14

▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q @

Outline

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

1 Time Measurement

2 FPGA TDCs

3 Hardware: TRB Platform

Experiences and Limits

5 Summary

・ロト ・ 母 ト ・ ヨ ト ・ ヨ ・ つへぐ

Time Measurements in Particle Physics: Why?

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

Time of Flight (ToF) applications for particle identification



"Live" plot of the currently running HADES measurement campaign @GSI.

Other "trivial" applications of time measurements

- Arrivial time to separate events (free running data acquisition)
- Pile-up (>1 reaction in integration time of detectors) rejection

Conclusion: Time measurements are used in every experiment.

▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q @

Time Measurements: How?

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

- Hardware: TRB Platform
- Experiences and Limits

Summary

How to obtain the time measurement

- Oscilloscope (ADC) gives the best representation of the original signal and best possibilities for offline processing and correction
- ADCs draw a lot of power, are expensive and additional massive data processing necessary → heat, price, space
- possible to use efficiently if time interval is short (selective trigger)

Typical photomultiplier signals on oscilloscope



Time Measurements with TDC

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

- If the number of channels increase and a very good time precision is needed
 - Signal discrimination (threshold) and time difference measurement is a feasible and effective option
- Amplitude measurement: direct Time over Threshold (ToT)
 - not linear and limited dynamic range
- Time measurement can also be used for precise charge measurement

Consequence: Use time measurement for all detectors in the system

- Many different methods of "direct" time measurement are possible
- A very flexible, precise, low power, small and cheap Time to Digital (TDC) converter is needed

Motivation for building TDCs with an FPGA

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

- To be independent from not easy to acquire ASICs from the community.
 - should be easily available, industrial quality in design, package and documentation
 - vendor independent (not really easy!)
 - based on FPGAs (TDC, DAQ, FEE-Discriminator) and other parts with a second source
 - We "misuse" digital FPGAs in the asynchronous and analoge domain
 - $\bullet\,$ an FPGA is more than a digital device $\rightarrow\,$ go deep in FPGA architecture
 - use intrinsic delays for time measurements, pulse stretching and signal delays
 - use LVDS-input buffers for signal discrimination
- To be flexible in functionality
 - Add and change functionality nobody thought of when the TDC was build

Basic Operation of an FPGA-TDC

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

- Coarse & Epoch counters for long measurement range
- Tapped Delay Line for fine time interpolator
- Stretcher for measuring the traling edge in the same channel
- Decoder: thermocode \rightarrow binary
- Ring buffer for the latest hit signals



▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q @

Fine Time Interpolation



- Propagation of the start signal is sampled with the stop signal
- Suits well with the FPGA architecture
- $\bullet\,$ Carry chain for delay line $\to\,$ small bin width
- $\bullet~\mbox{Clock signal}$ as common stop signal $\rightarrow~\mbox{minimal skew}$
- Coarse & Epoch counters $\rightarrow \sim$ 45 minutes measurement range

▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● ○ ○ ○

FPGA-TDC: Further improvements



- $\bullet~$ Non-uniform intrinsic delays $\rightarrow~$ Ultra wide bins
- the precision of the TDC is reduced
- Wave Union Launcher [Jinyuan Wu]:
 - send many transitions to the delay line, when a hit signal arrives, thereby increase the number of measurements on the delay line and even out ultra wide bins (UWB)

FPGA-TDCs: Bin Width (DNL)

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

- Non-linearities caused by non-uniform intrinsic delays
- UWBs increase non-linearities
- WUL averages the locations of the transition on the delay line, thus dividing the UWBs
- Max bw: $45ps \rightarrow 35ps$
- $\bullet~\mbox{Avg}$ bw: 20ps \rightarrow 10ps
- Calibration of the TDC further decreases the non-linearity



DOI: 10.1109/NSSMIC.2011.6154560

Features of FPGA TDCs

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

- FPGA TDCs can be very precise time measurement devices
- trade-off between time precision and used resources
- FPGA TDCs are flexible
 - implemented features can be easily changed (trigger, windows, scalers, etc.)
 - new ideas pop up quite often



TRB Platform: Features

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

- Versatile and meanwhile technically mature platform for TDC measurements and digital readout
- consists of FPGA-firmware, DAQ- and (online-)calibration-software and hardware
- most important ingredient: the TRB team (a collaboration) behind all of it for (necessary) support [http://trb.gsi.de]
- many channels (256 single edge) on one board and as cheap as possible
- leading edge time precision: 8-12ps RMS
- hitrates <50MHz (burst)
- DAQ: 140MBytes/s via two 1GbE links

TRB Platform: TRB3 module

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary



- 4 times high speed 208-pin connector for various AddONs
- Addons available:
 - 6/8 port Hubs
 - NIM/ECL-Input
 - standard 100mil pins
 - Padiwa-Adapter

< ロ > < 同 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < 回 > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ >

• etc.

[http://trb.gsi.de]

TRB Platform: Some Hardware II



- 1/4 of TRB3 on a single card
- fits in 19" standard crate system with FPGA-connectivity in backplane

▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q @

- better DC/DC converters for higher time precision
- higher DAQ speed

FPGA-TDC: Charge Measurement



Experiences and Limits

Summary

Modified Wilkinson ADC:

- "Come-and-Kiss"-principe: Commercial of the shelf and keep it small and simple.
- Input signal is integrated with a capacitor
- Capacitor is discharged using a constant current source triggered by the input signal

□ ▶ 4 冊 ▶ 4 트 ▶ 4 트 ▶ 트 りへで

• Measured charge precision: 0.22%

Experiences and Limits

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

What did we learn?

- TRB DAQ-Systems work very well and stable also for "larger" systems
- FPGA-TDC working horse of the whole DAQ/FEE-system
- Padiwa-FEE works for many users very well
- but...



▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q @

Padiwa Timing Results



- timing measurements in the lab are very good
- "trivial": signal to noise determines timing precision

Feature and Problem at the same Time

FPGAs for ps Timing

- Michael Traxler, GSI
- Time Measurement
- Hardware: TRB Platform
- Experiences and Limits
- Summary

- The TRB platform is a stable and flexible
- Flexibility has a (high) price
 - Cables everywhere! (Fine for ~1k channels.)



Effects of Cables

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

- Mechanically this becomes a problem (densities)
 - Barrel-DIRC-beam-time clearly showed that this is more than a inconvenience
- Long cables damp the signal away



Solution

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

- Rethink mechanics/cables/connectors
- Improve on noise to the input of the FEE

▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q @

- Improve on noise immunity of FEE
- Work together in a larger team!
- Some pressure!

Team for a total of 100k channels



HAL9000: Inspiration

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary

• Stanley Kubrick solved this problem in 1968 :-)



イロト 不得 トイヨト イヨト

ъ

Backplane Granularity and Dimensions: Long and Tedious Optimization



DiRICH concept



DiRICH Requirements and Design Consequences

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

- FEE module for 32 channels
- Amplification, Discrimination, TDC + DAQ
- "no" cables
- analog input signals and digital output signals (serial transmission) over the same connector
- low power consumption
- only possible with newest FPGAs (price/performance) and very high pin-count connectors
- galvanically isolate PMT from FEE with transformers
 - reduces issues with HV-power-supply GND connection

DiRICH: Amplifier Schematics



• BFU760F: fast transistor (40 GHz transition freq.)

э

- low power consumption: 12mW
- high gain: \sim 30
- simple (no specific higher order shaping)

DiRICH: Put to Reality

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement FPGA TDC

Hardware: TRB Platform

Experiences and Limits



- 47mm x 100mm area, 300μ m x 600μ m components, 0201
- transformer, gain 30 amps, 16bit-DAC, discriminator, high precision TDC, DAQ + TrbNet (2Gbit/s SERDES), slow-control and voltage-regulation

DiRICH: Backplane

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

Hardware: TRB Platform

Experiences and Limits



- Backplane with 12 DiRICH, 6 MA-PMTs (384 channels)
- real challenge in layout, 14 layers with stacked microvias.

DiRICH: Concentrator



Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary



• Concentrator module: aggregates 12 TrbNet links to 1 TrbNet link

DiRICH: Power



Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits

Summary



Power module (both, DC/DC and Linear) + HV + Clock
+ Trigger-Distribution

DiRICH: System

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

FPGA TDCs

Hardware: TRB Platform

Experiences and Limits



- All DiRICH photos by Gabi Otto @GSI
- All fits in :-) How does it perform ?

Timing Performance in the Lab



HADES RICH Detector

FPGAs for ps Timing

Michael Traxler, GSI

Time Measurement

Hardware: TRB Platform

Experiences and Limits

Summary



ъ



FPGAs for ps Timing

- Michael Traxler, GSI
- Time Measurement
- FPGA TDCs
- Hardware: TRB Platform
- Experiences and Limits
- Summary

- The TRB (with its associated FPGA-TDC + DAQ) is a mature platform (hardware and software) useful for many applications
 - Collaboration takes care of constant development and maintenance
- based on the "come-and-kiss" principle
 - no hard to acquire ASICs used
 - due to modern commercial components (small, less power) now closer to the ASIC domain
- limitations for larger systems
 - cable-hell and noise
- larger application specific systems: need to optimize
 - hard and software is "easy" to adapt to special applications

◆□▶ ◆□▶ ◆□▶ ◆□▶ → □ ・ つくぐ

• MA-PMT and MCP-PMT applications are quite common and we can share the achievements and effort

Summary II

FPGAs for ps Timing

- Michael Traxler, GSI
- Time Measurement
- FPGA TDCs
- Hardware: TRB Platform
- Experiences and Limits
- Summary



• The HADES detector uses only TDCs for analog to digital conversion. Including the Electromagnetic Calorimeter.

Thank you for your attention!

FPGAs for
ps Timing
Michael
Traxler. GSI
Time Mea-
Hardware:
Platform
Summary

◆□▶ ◆□▶ ◆ □▶ ◆ □ ● ● ● ●